

UNIT-II


phase controlled Rectifiers

Rectifier:- A rectifier is also known as ac-de converter

Applications:-

- Steel-rolling mills, paper mills
- Traction system working on dc
- Electrochemical & electrometallurgical processes
- Magnet power supplies
- Portable hand tool drives
- High-voltage dc transmission

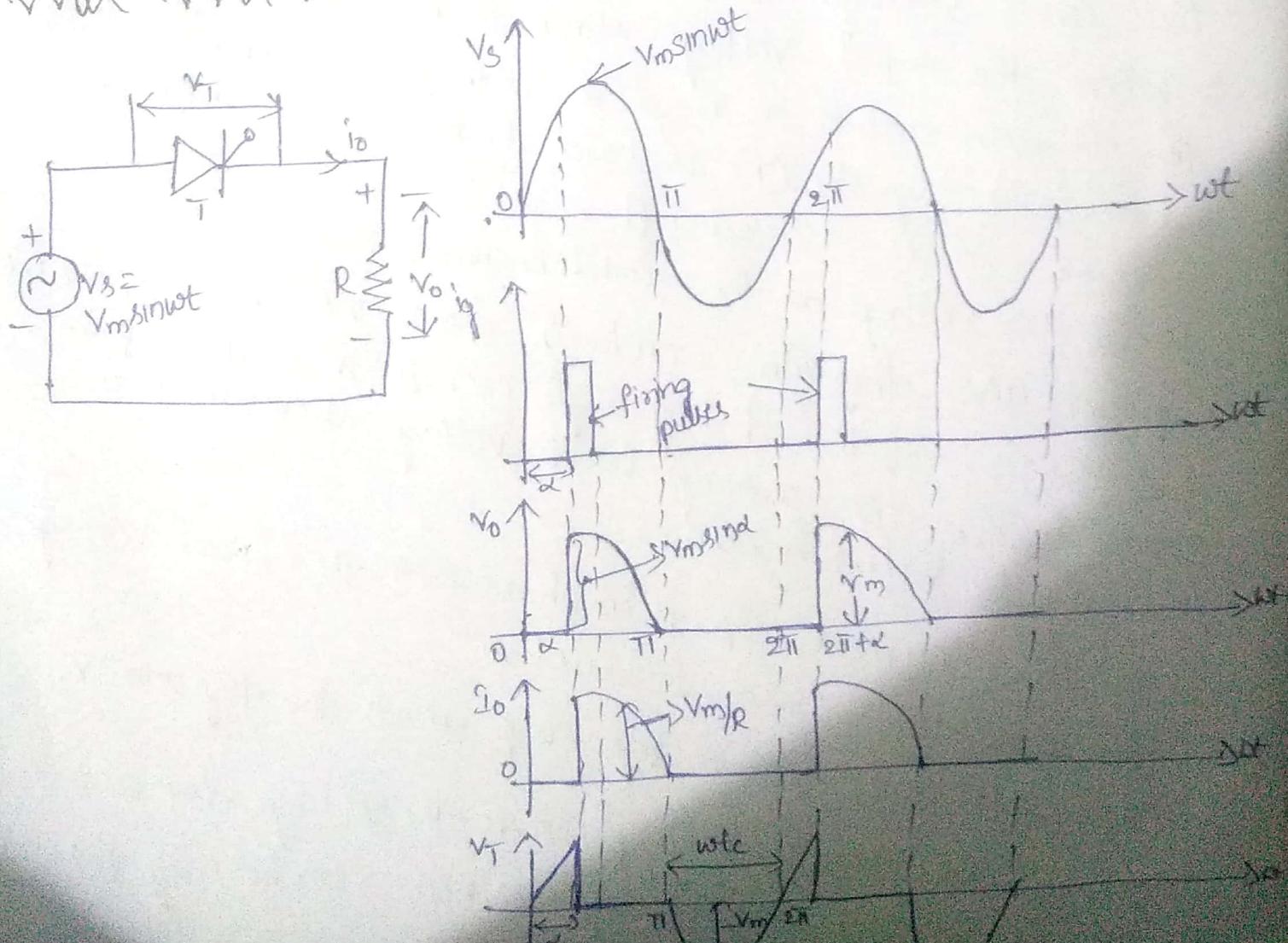Single phase half wave circuit with R-load



→ fig. shows the 1-Ø half wave controlled converter using resistive load. It consists of a single thyristor feeding DC power to resistive load

→ let us consider a source voltage $V_s = V_m \sin \omega t$ is impressed to the circuit

→ During the positive half cycle of input voltage, the thyristor anode is positive with respect to its cathode hence the thyristor is said to be forward biased.

→ When the thyristor is triggered at some delay angle $\omega t = \alpha$, then thyristor starts conducting and full voltage appears across the load as V_o .

→ At the instant of delay angle (α) firing angle α ,

the load voltage V_o rises from zero to $V_m \sin \alpha$.

→ When the input voltage starts to be negative at $\omega t = \pi$, the thyristor anode is negative with respect to its cathode causes the thyristor (T) is said to be reversed biased therefore, it is turned off.

Hence the voltage at the load becomes zero

→ From, the thyristor conducts from $\omega t = \alpha$ to π , $\alpha + \frac{\pi}{2}$ and soon. If the firing angle (α) is increased from zero to π , the average load voltage decreases from the largest value to zero

→ The load current, i_o is in phase with the load voltage V_o because the load is resistive

→ The waveform of voltage drop across the thyristor V_T

→ During the conducting periods the voltage drop across the thyristor is zero and during the non-conducting period

the voltage drop in the thyristor is appeared and is represented as the waveform

→ The thyristor is reverse biased for π radians, the clt turn-off time is given by

$$t_c = \frac{\pi}{\omega} \text{ sec}$$

where $\omega = 2\pi f$ and f is the supply frequency in Hz

→ the circuit turn-off time t_c must be more than the SCR turn-off time t_{av} as specified by the manufacturers

→ Average voltage V_o across load R .
for the 1-Ø half wave clt in terms of firing angle α is given by

$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$= \frac{V_m}{2\pi} (1 + \cos \alpha)$$

where α - firing angle

Maximun output voltage, V_o occurs at $\alpha = 0^\circ$

$$V_{o,\max} = \frac{V_m}{2\pi} \cdot 2 = \frac{V_m}{\pi}$$

Normalizing output voltage, $V_o = \frac{V_{o,\max}}{2} (1 + \cos \alpha)$

Average load current, $i_o = \frac{V_o}{R} = \frac{V_{o,\max}}{2\pi R} (1 + \cos \alpha)$

in some types of loads, one may be interested in rms value of load voltage V_{rms} . ex. of such loads are electric heating and incandescent lamps.

→ RMS voltage V_{rms} in such case is given by

$$V_{rms} = \left[\frac{1}{2\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{1/2}$$

$$= \frac{V_m}{2\sqrt{\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

→ The value of rms current I_{rms} is

$$I_{rms} = \frac{V_{rms}}{R}$$

power delivered to resistive load = $(V_{rms}) \times (I_{rms})$

$$= \frac{V_{rms}}{R} = I_{rms}^2 \cdot R$$

Input volt-amps = $\frac{V_s}{\sqrt{2}}$ (total rms line current)



$$= V_s \cdot I_{rms} = \frac{\sqrt{2} V_s}{2R\sqrt{\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

input power factor = $\frac{\text{power delivered to load}}{S}$

$$= \frac{V_{rms} \cdot I_{rms}}{V_s \cdot I_{rms}} = \frac{V_{rms}}{V_s}$$

$$\text{input power factor} = \frac{1}{\sqrt{2}\pi} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

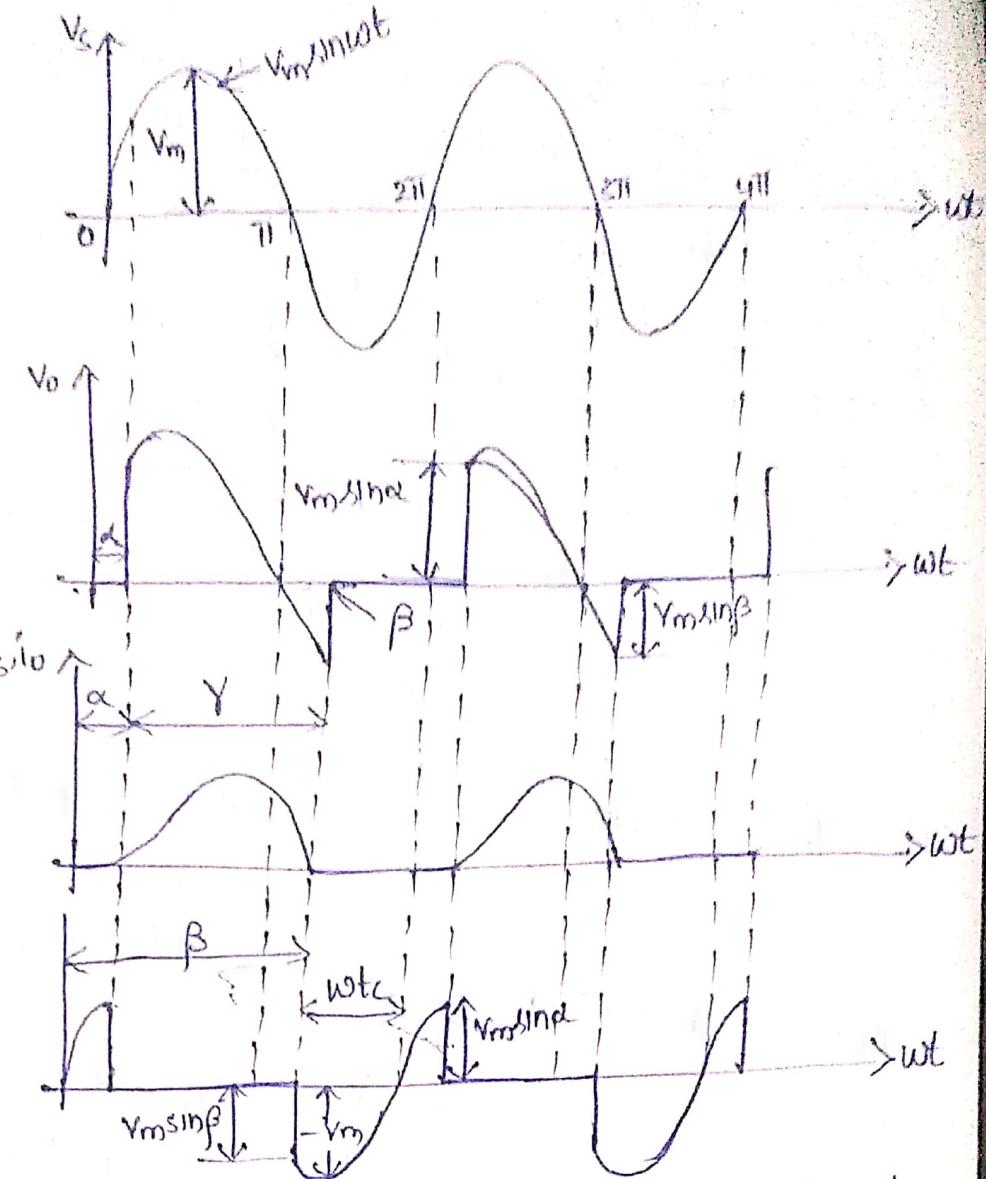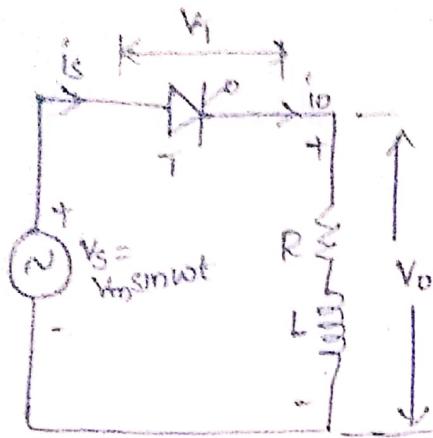⇒ Single-phase half-wave ckt with RL load:



→ A single phase half wave thyristor ckt with RL load line voltage V_s . At $\omega t = \alpha$, thyristor is turned on by gating signal.

→ The line voltage V_o at once becomes equal to source voltage V_s .

→ But the inductance L forces the load, or output, current i_o

→ to rise gradually. After sometime, i_o reaches maximum value and then begins to decrease.

→ At $\omega t = \pi$, V_o is zero, but i_o is not zero because of the load inductance L .

→ After $\omega t = \pi$, SCR is subjected to reverse anode voltage but it will not be turned off as load current i_o is

the magnetic energy stored in the inductor.

not less than the holding current. At some angle $\beta > \alpha$, it reduces to zero and SCR is turned off as it is already reverse biased.

- At $wt = \beta$, $v_o = 0$ and $i_o = 0$. At $wt = 2\pi + \alpha$, SCR is triggered again. v_o is applied to the load and load current develops as before.
- Angle β is called the extinction angle and $(\beta - \alpha) = \gamma$ is called conduction angle.
- The waveform of voltage across thyristor V_T reveals that when $wt = \alpha$, $V_T = V_m \sin \alpha$, from $wt = \alpha + \beta$, $V_T = 0$ and at $wt = \beta$, $V_T = V_m \sin \beta$.
- As $\beta > \alpha$, V_T is negative at $wt = \beta$, \therefore thyristor is reverse biased from $wt = \beta$ to 2π .

Thus, the ckt. turn-off time,

$$t_c = \frac{2\pi - \beta}{\omega} \text{ sec}$$

The voltage eqn for the ckt, when T is on,

$$V_m \sin wt = R i_o + L \frac{di_o}{dt}$$

- The load current i_o consists of two components one steady-state component is and the other transient component it, here i_o is given by

$$i_s = \frac{V_m}{\sqrt{R^2 + X^2}} \sin(wt - \phi)$$

where $\phi = \tan^{-1} \frac{X}{R}$ and $X = \omega L$

The transient component, it can be obtained from
force-free eqn

$$Ri_t + L \frac{di_t}{dt} = 0$$

it solution gives, $i_t = Ae^{-(RL)t}$

$$i_0 = i_s + i_t = \frac{V_m}{Z} \sin(\omega t - \phi) + A e^{-RLt} \rightarrow ①$$

$$\text{where } Z = \sqrt{R^2 + X^2}$$

constant A can be obtained from the boundary condition
at $\omega t = \alpha$

$$\text{At this time } t = \frac{\alpha}{\omega}, i_0 = 0$$

$$\text{then, } 0 = \frac{V_m}{Z} \sin(\alpha - \phi) + A \cdot e^{-R\alpha/\omega}$$

$$A = -\frac{V_m}{Z} \sin(\alpha - \phi) e^{R\alpha/\omega}$$

sub 'A' in eqn ①

$$i_0 = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{V_m}{Z} \sin(\alpha - \phi) \exp\left\{-\frac{R}{\omega L}(wt - \alpha)\right\} \rightarrow ②$$

for $\alpha < \omega t < \beta$

it also seen from the wave-form of i_0

when $\omega t = \beta$, load current $i_0 = 0$, substituting this

$$\sin(\beta - \phi) = \sin(\alpha - \phi) \cdot \exp\left\{-\frac{R}{\omega L}(\beta - \alpha)\right\}$$

The transcendental eqn can be solved the value of extinction angle β , average load voltage V_0 is given by


$$V_0 = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \cdot d(\omega t) = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

$$\text{Avg. load current, } I_0 = \frac{V_m}{2\pi R} (\cos \alpha - \cos \beta)$$

$$\text{RMS load voltage, } V_{0\text{rms}} = \left[\frac{1}{2\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{1/2}$$
$$= \frac{V_m}{2\sqrt{\pi}} \left[(\beta - \alpha) - \frac{1}{2} (\sin 2\beta - \sin 2\alpha) \right]^{1/2}$$

Single phase halfwave ckt with RL load & free wheeling diode

- 1-φ half wave ckt with RL load, the wave form of load current is not continuous and due to this the operating power factor of the system becomes very poor which may give rise to poor performance of the ckt.
- In order to improve the wave form of load current & and power factor of the ckt a diode is connected across the load is called free wheeling diode. It is also called by-pass (or) commutating diode.

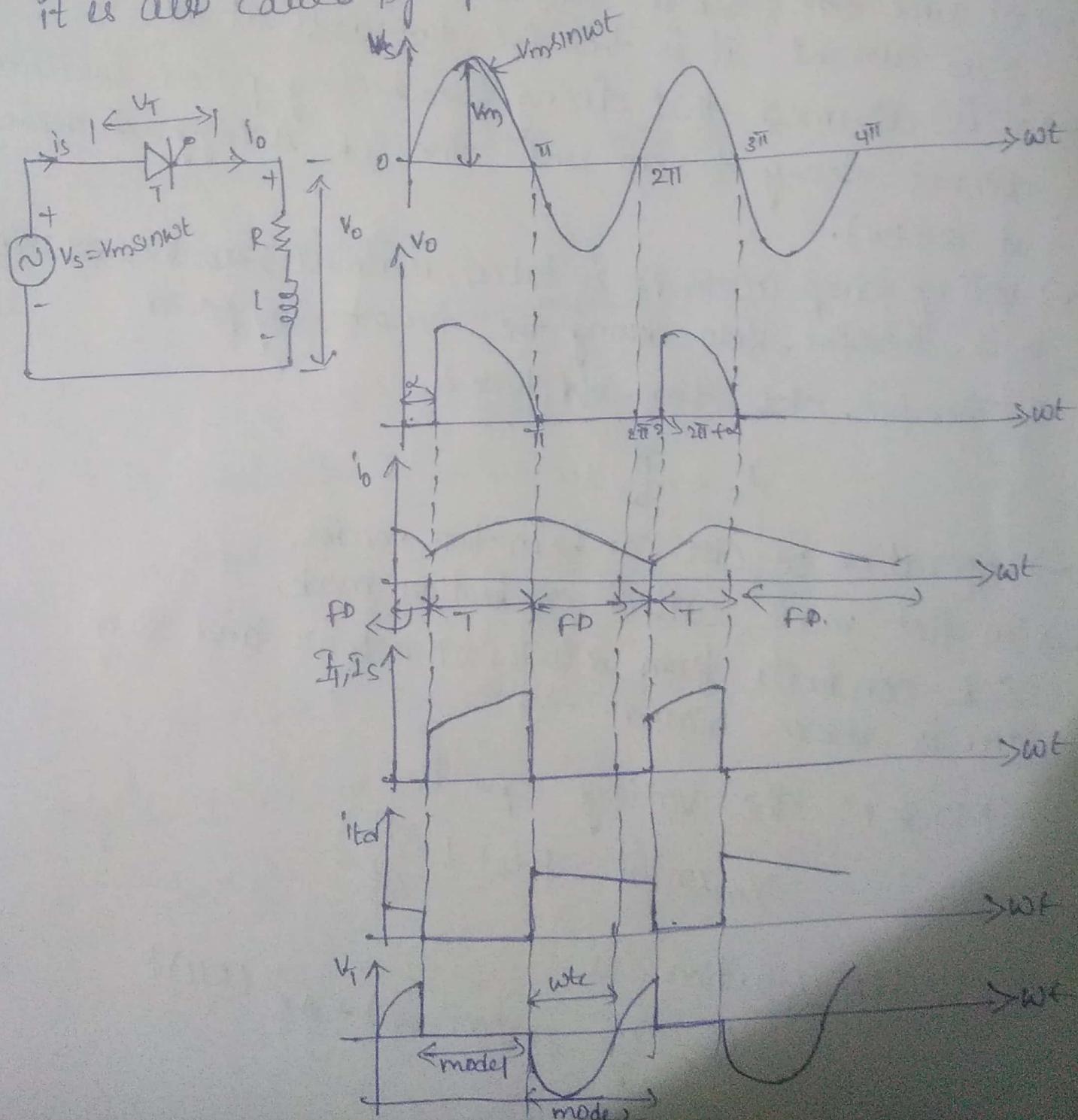

- At $\omega t = 0$, source voltage is becoming positive.
- At some delay angle α , forward biased SCR is triggered and source voltage v_s appears across load as v_o
- At $\omega t = \pi$, source voltage v_s is zero and just after this instant, as v_s tends to reverse, freewheeling diode FD is forward biased through the conducting SCR.
- As a result, load current i_o is immediately transferred from SCR to FD as v_s tends to reverse.
- At same time, SCR is subjected to reverse voltage and zero current, it is therefore turned off at $\omega t = \pi$.
- It is assumed that during freewheeling period, load current does not decay to zero until the SCR is triggered again at $(2\pi + \alpha)$.
- Voltage drop across FD is taken as almost zero, the load voltage v_o is, therefore, zero during the free wheeling period.

Therefore, ckt turn-off time is

$$t_c = \frac{\pi}{\omega} \text{ sec.}$$

- operation of ckt can be in two modes.
- In first mode called conduction mode, SCR conducts from α to π , $2\pi + \alpha$ to 3π and so on and is reverse biased

Mode 1: the voltage eqn is

$$V_m \sin \omega t = R i_o + L \frac{d i_o}{dt}$$

its solution is

$$i_o = \frac{V_m}{R} \cdot \sin(\omega t - \phi) + A e^{-(R/L)t}$$

At $\omega t = \alpha$, $i_o = I_0$, at $t = \alpha/\omega$, $i_o = I_0$

$$\therefore A = \left[I_0 - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{R\alpha/\omega t}$$

$$\therefore i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + \left[I_0 - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{-R/L(t - \frac{\alpha}{\omega})}$$

\therefore at Mode 1, $\alpha \leq \omega t \leq \pi$

Mode 2: This mode is called free wheeling mode, extends from π to $2\pi + \alpha$, 3π to $4\pi + \alpha$ and so on. In this mode SCR is reverse biased from π to 2π , 3π to 4π as by voltage waveform V_t .

The voltage equ" for mode 2 is

$$0 = R i_o + L \frac{di_o}{dt}$$

$$\text{its solution is } i_o = A e^{-(R/L)t}$$

$$\text{At } \omega t = \pi, i_o = I_{o1}$$

$$\text{it gives } A = I_{o1} \cdot \exp\left\{-\frac{R}{L}(t - \pi/\omega)\right\}$$

\therefore At mode 2, $\pi < \omega t \leq (2\pi + \alpha)$

Avg. load voltage V_o is given by

$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t)$$
$$= \frac{V_m}{2\pi} (1 + \cos \alpha)$$


Average load current,

$$I_0 = \frac{V_0}{R} = \frac{V_m}{2\pi R} [1 + \cos \alpha]$$

The Advantages of free wheeling diode are

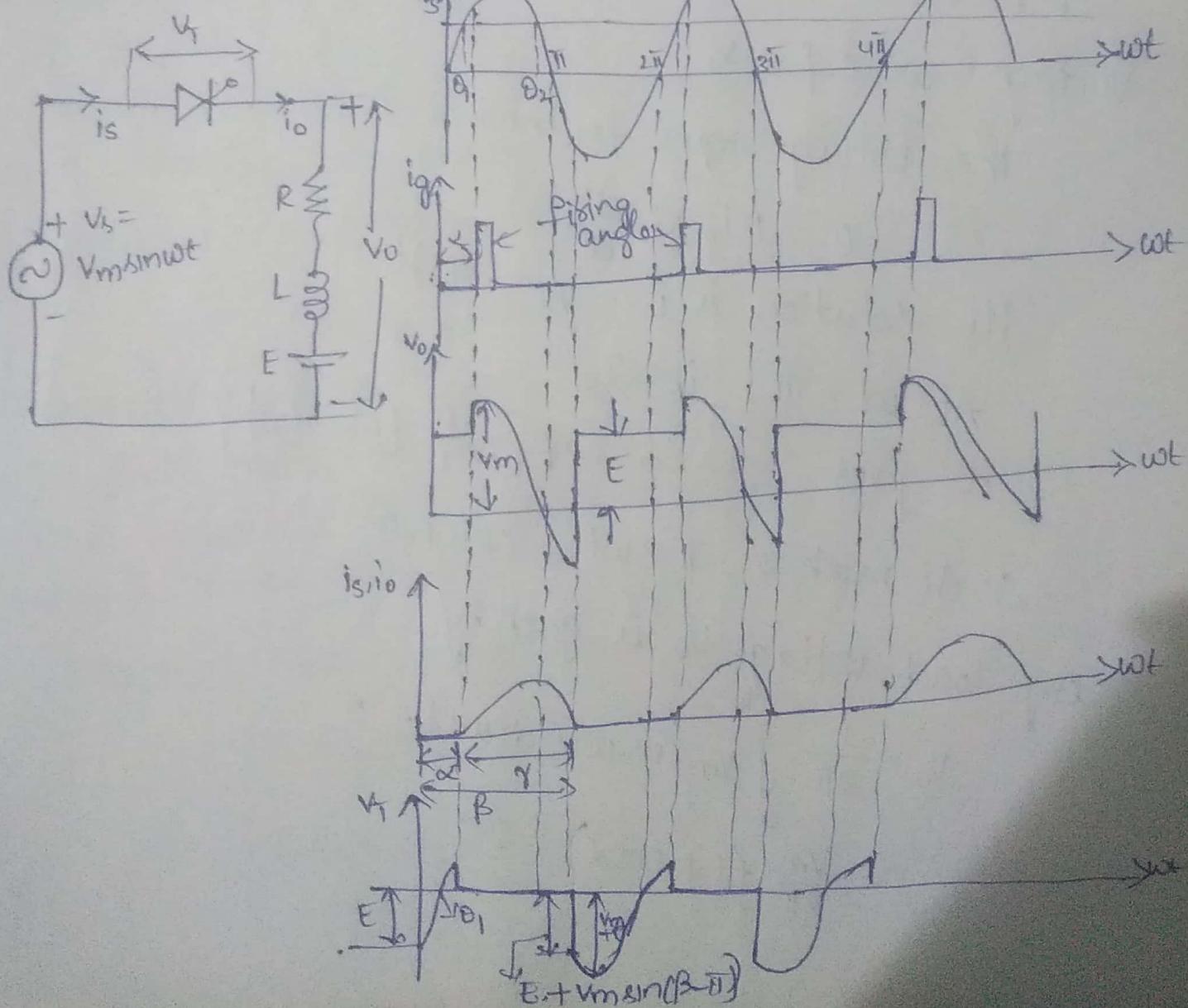- i) input p.f is improved
- ii) load current waveform is improved
- iii) load performance is better
- iv) As energy stored in L is transferred to R during the free wheeling period, overall converter efficiency improves

⇒ Single phase Half wave circuit with RLE load:



A 1-φ halfwave controlled rectifier with RLE load.
 The counter emf E in the load may be due to a battery
 or dc motor. The minimum value of firing angle is obtained
 from the relation $V_m \sin \omega t = E$. This is shown to occur at
 an angle θ_1 , where

$$\theta_1 = \sin^{-1}(E/V_m)$$

- At Thyristor T is fired at an angle $\alpha < \theta_1$, then $E > V_s$,
 SCR is reverse biased and therefore it will not turn on.
- Similarly, max. value of firing angle is $\theta_2 = \pi - \theta_1$
- During the interval load current i_o is zero, load voltage
 $v_o = E$ and during the time i_o is not zero, v_o follows v_m
 for the ckt with SCR Ton, KVL gives the voltage diff equ as

$$V_m \sin \omega t = R i_o + L \frac{di_o}{dt} + E$$

The solution of this eqn made up of two components

1. Steady state current component is
2. Transient current component it.

for convenience is maybe thought of as the sum of
 i_{s1} & i_{s2} where i_{s1} is the steady state current due to ac source
 i_{s2} is that due to counter emf E acting alone

i_{s1} is that due to dc counter emf E acting alone.

$$\therefore i_{s1} = \frac{V_m}{Z} \sin(\omega t + \phi)$$

if only E were present, then steady state current i_{s2} is

$$i_{s2} = -(E/R)$$

The transient current it is $it = A \cdot e^{-(R/L)t}$

Then the total current $i_o = i_{s1} + i_{s2} + it$

$$= \frac{V_m}{Z} \sin(\omega t + \phi) - \frac{E}{R} + A e^{-(R/L)t}$$

At $wt = \alpha$, $i_0 = 0$, i.e., at $t = \frac{\alpha}{\omega}$, $i_0 = 0$

$$\text{This gives } A = \left[\frac{E}{R} - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{R\alpha/L\omega}$$

$$i_0 = \frac{V_m}{Z} \left[\sin(\omega t - \phi) - \sin(\alpha - \phi) \exp\{-R/L\omega(t - \alpha)\} \right] - \frac{E}{R} \left[1 - \exp\{-R/L\omega(t - \alpha)\} \right]$$

it is applicable for $\alpha \leq wt \leq \beta$.

The extinction angle β depends upon load emf E , fixing angle α and the load impedance angle ϕ .

→ Average voltage across inductance is zero. Thus, average value of load current can be obtained by integrating $(V_m \sin \omega t - E)/R$ between α and β .

The average load current i_0 is given by

$$i_0 = \frac{1}{2\pi R} \left[\int_{\alpha}^{\beta} V_m \sin \omega t - E dt \right]$$

$$= \frac{1}{2\pi R} [V_m (\cos \alpha - \cos \beta) - E(\beta - \alpha)]$$

Here conduction angle $\gamma = \beta - \alpha$, putting $B = \gamma + \alpha$ gives

$$i_0 = \frac{1}{2\pi R} [V_m (\cos \alpha - \cos(\gamma + \alpha)) - E \cdot \gamma]$$

using the trigonometric equ"

$$\cos x - \cos y = 2 \sin \frac{x+y}{2} \cdot \sin \frac{y-x}{2}$$

$$\text{Then } i_0 = \frac{1}{2\pi R} \left[2V_m \sin \left(\alpha + \frac{\gamma}{2} \right) \sin \frac{\gamma}{2} - E \cdot \gamma \right]$$

Average load voltage is given by

$$V_0 = E + i_0 \cdot R = E + \frac{1}{2\pi} \left[2V_m \sin \left(\alpha + \frac{\gamma}{2} \right) \sin \frac{\gamma}{2} - \gamma \cdot E \right]$$

$$= E \left(1 - \frac{\gamma}{2} \right) + \frac{V_m}{\pi} \sin \left(\alpha + \frac{\gamma}{2} \right) \sin \frac{\gamma}{2}$$

The above expression for the avg load voltage v_o can be for periodically α , extending from α to $(2\pi + \alpha)$, we have

$$v_o = \frac{1}{2\pi} \left[\int_{\alpha}^{2\pi} v_m \sin(\omega t) \cdot d(\omega t) + E(2\pi + \alpha - \beta) \right]$$

$$= \frac{1}{2\pi} [v_m (\cos \alpha - \cos \beta) + E(2\pi + \alpha - \beta)]$$

If load inductance L is zero, the extinction angle β would be equal to $\theta_2 = \pi - \theta_1$. Now β would be less than π then $\beta = \pi - \theta$.

∴ Avg load current i_o is

$$i_o = \frac{1}{2\pi R} [v_m (\cos \alpha - \cos(\pi - \theta_1)) - E(\pi - \theta_1 - \alpha)]$$

$$= \frac{1}{2\pi R} [v_m (\cos \alpha + \cos \theta_1) - E(\pi - (\theta_1 + \alpha))]$$

RMS value of load current,

$$i_{rms}^2 = \frac{1}{2\pi} \int_{\alpha}^{\beta} \left(\frac{v_m \sin \omega t - E}{R} \right)^2 d(\omega t)$$

$$= \frac{1}{2\pi R^2} \int_{\alpha}^{\beta} (v_m^2 \sin^2 \omega t + E^2 - 2v_m E \sin \omega t) d(\omega t)$$

its amplification gives

$$i_{rms} = \left[\frac{1}{2\pi R^2} \left\{ (v_s^2 + E^2)(\beta - \alpha) - \frac{v_s^2}{2} (\sin 2\beta - 2 \sin 2\alpha) - 2v_m E (\cos \alpha - \cos \beta) \right\} \right]^{1/2}$$

power delivered to load, $P = i_{rms}^2 \cdot R + i_o \cdot E$


$$\text{Supply power factor} = \frac{i_{rms} \cdot R + i_o \cdot E}{V_s \cdot i_{rms}}$$

The cpt turnoff time $t_c = \frac{2\pi + \theta_1 - \beta}{\omega}$ sec


Full wave Rectifiers :-

In 1- ϕ half wave controlled rectifiers produce only one pulse of load current during one cycle of source voltage, these can therefore be termed as single phase single pulse converter.


- The disadvantages of 1- ϕ half wave, or single phase one-pulse rectifiers, are minimised by the use of 1- ϕ full wave, or 1- ϕ two pulse rectifiers.
 - There are two basic configurations for full wave controlled converters.
 - One configuration uses an input transformer with two windings for each input phase winding. This is called mid-point converter.
1. A single phase two pulse mid point SCR rectifier
 2. A three phase six pulse mid point converter

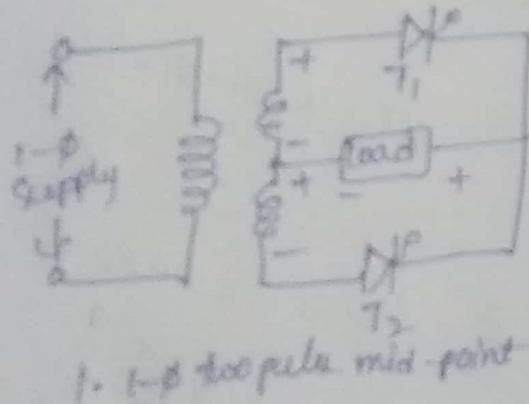

1. 1- ϕ two-pulse mid-point

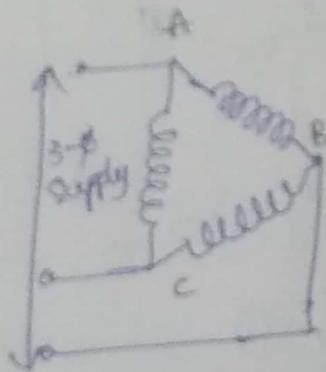


1. 3- ϕ three-pulse mid-point

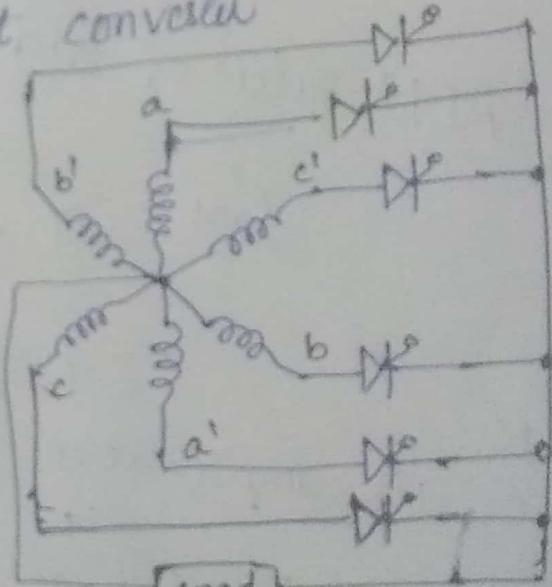


2. 3- ϕ 6 pulse mid point

- Second configuration uses SCRs in the form of bridge circuit.

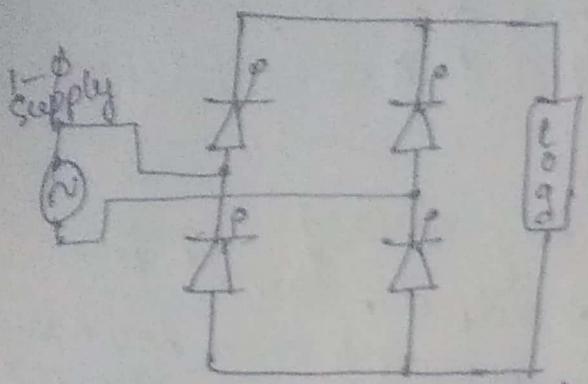1. 1- ϕ full wave, or two-pulse, bridge converter using four SCRs
2. A 3- ϕ six-pulse bridge converter using six SCRs




1. 1- ϕ two pulse bridge Rectifier


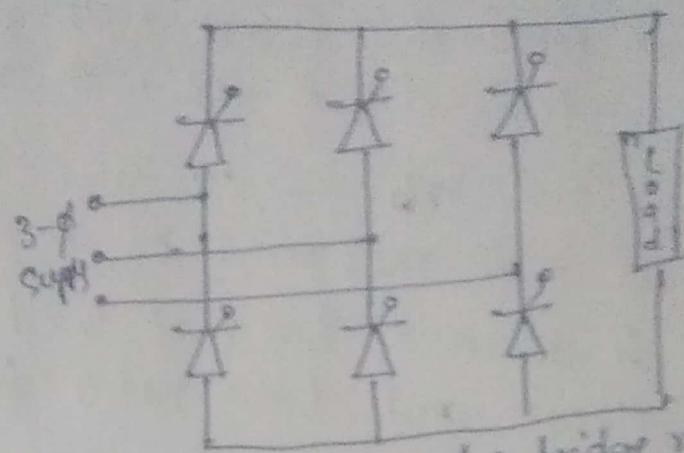


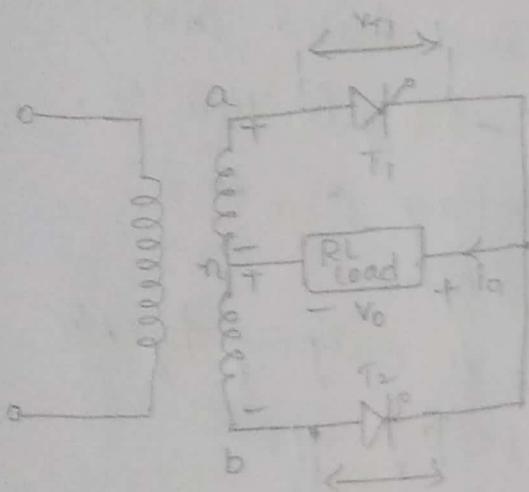2. 3- ϕ six pulse bridge rectifier

Single phase full wave Rectifier :- (midpoint converter)



a) circuit diagram

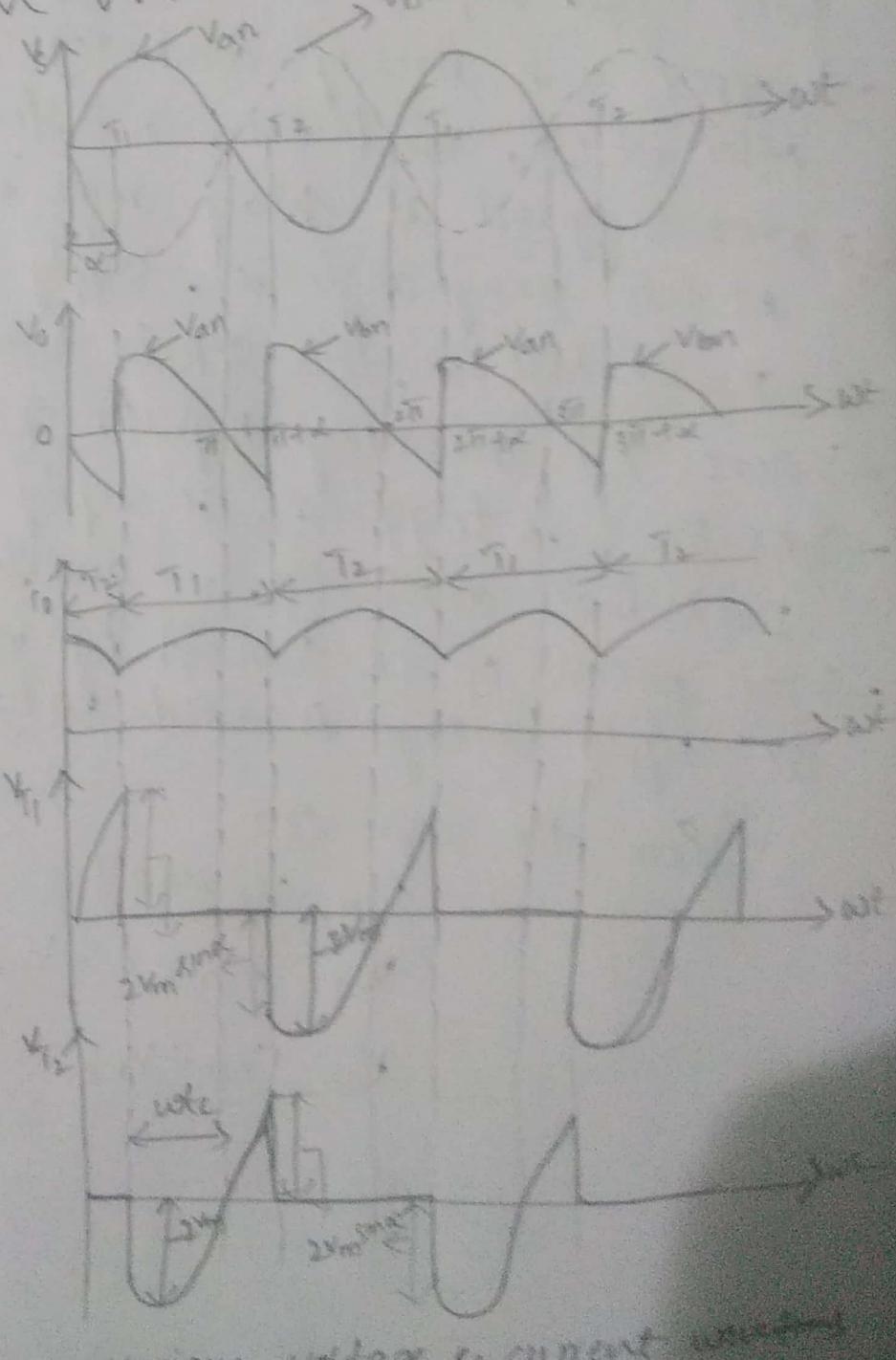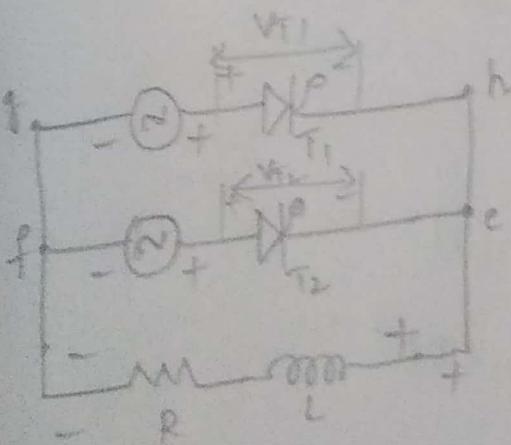

→ 1-φ full wave rectifier using a center-tapped tf

→ when terminal A is +ve with respect to n,
terminal N is +ve with respect to b.

$$\therefore V_{an} = V_{nb} \Rightarrow (or) V_{an} = -V_{bn}$$

as 'n' is mid point of secondary winding.

→ it is assumed here that load or output current is continuous and turns ratio from primary to each secondary is unity

→ Thyristors T_1 & T_2 are forward biased during +ve and -ve half cycles respec. they are triggered accordingly.

→ Suppose T_2 is already conducting.

After $\omega t = 0$, V_{an} is +ve, T_1 is forward biased and

→ when triggered at delay angle ' α ' $\rightarrow T_1$ gets turn on.
At this firing angle ' α ', supply voltage $> V_m \sin \alpha$
reverse bias T_2 , this SCR is turned off.

→ Here T_1 is incoming thyristor & T_2 is outgoing thyristor

→ As the T_1 is triggered, ac supply voltage applies
reverse bias across the T_2 and its turns off

→ This process of SCR turnoff by natural reversal of
ac supply voltage is called natural (or) line commutation

from the equⁿ ckt

$$V_{an} = V_m \sin \omega t$$

$$V_{bn} = -V_{nb} = -V_m \sin \omega t$$

$$V_{ab} = V_{an} + V_{nb} = 2V_m \sin \omega t$$

→ when $\omega t = \alpha$, T_1 is triggered, SCR T_2 is reverse voltage $V_{ab} = 2V_m \sin \alpha$, current transferred from T_2 to T_1 & T_2 is turned off

→ The magnitude of reverse voltage across T_2 can also be obtained by applying KVL to the loop $efghe$ at the instant T_1 triggered, thus

$$: V_{T_2} - V_{bn} + V_{an} - V_{T_1} = 0$$

$$V_{T_2} = V_{bn} - V_{an} + V_{T_1}$$

with T_1 conducting, $V_{T_1} = 0$, \therefore the voltage across T_2

$$V_{T_2} = -V_{bn} - V_{an}$$

$$= -2V_m \sin \alpha$$

As the above exp ' T_2 ' is reverse biased by voltage $2V_m \sin \alpha$ and it is turns off.

→ Thyristor T_1 conducts from α to $\pi + \alpha$

→ After $\omega t = \pi$, T_1 is reverse biased, but it will continue

conducting as the forward biased SCR T_2

→ At $\omega t = \pi + \alpha$, T_2 is triggered, T_1 is reverse biased by voltage

of magnitude $2V_m \sin \alpha$;

current transferred from T_1 to T_2 , T_1 is turned off

→ The turn off time provided by the circuit to SCR T_2 is

$t_c = \frac{\pi - \alpha}{\omega}$ sec
 At T_2 is turns off
 & reverse biased from
 $\omega t = \alpha$ to π

→ Thyristor T_1 is turned off at $\omega t = \pi + \alpha$ & reverse voltage from $\omega t = \pi + \alpha$ to $\omega t = 2\pi$

$$t_c = \frac{2\pi - (\pi + \alpha)}{\omega} = \frac{\pi - \alpha}{\omega}$$

The average value of output voltage is

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\alpha+\pi} V_m \sin \omega t \cdot d(\omega t)$$
$$= \frac{2V_m}{\pi} \cos \alpha$$

\Rightarrow for mid-point rectifier observations are


1. when commutation of an SCR is desired, it must be reversed biased and the incoming SCR must be forward biased
2. when incoming SCR is on, current is transferred from outgoing SCR to incoming SCR.
3. The circuit turn-off time is greater than the SCR turn off time

\Rightarrow Single phase full-bridge Rectifiers

\rightarrow 1-Ø full converters
are primarily three types.

they are

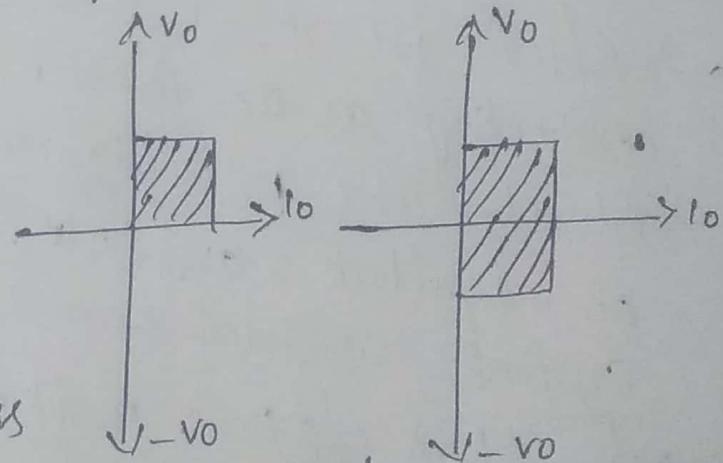1. uncontrolled converters
2. half controlled converters
3. fully controlled converters



a) one quadrant

b) two quadrant

\rightarrow An uncontrolled converter uses only diodes and the level of dc op voltage cannot be controlled



\rightarrow A half controlled converter uses a mixture of diodes & thyristors and there is a limited control over the level of dc output voltage.

- A fully controlled converter uses thyristors only & there is a wider control over the level of dc output voltage.
- A semi converter is a one quadrant converter. it has one polarity of dc op voltage and current at its output terminals.
- A two quadrant converter is one in which voltage polarity can reverse but current direction cannot reverse because of the unidirectional nature of thyristors

Single phase fullwave Bridge converter :-

- Generally for fullwave rectifier we will take it as a two mode
1. continuous conduction mode
 2. Discontinuous conduction mode
- ⇒ Continuous conduction mode means inductance L is large
Angle ' α ' is small
- ⇒ Discontinuous conduction mode means inductance L is small
Angle α is large

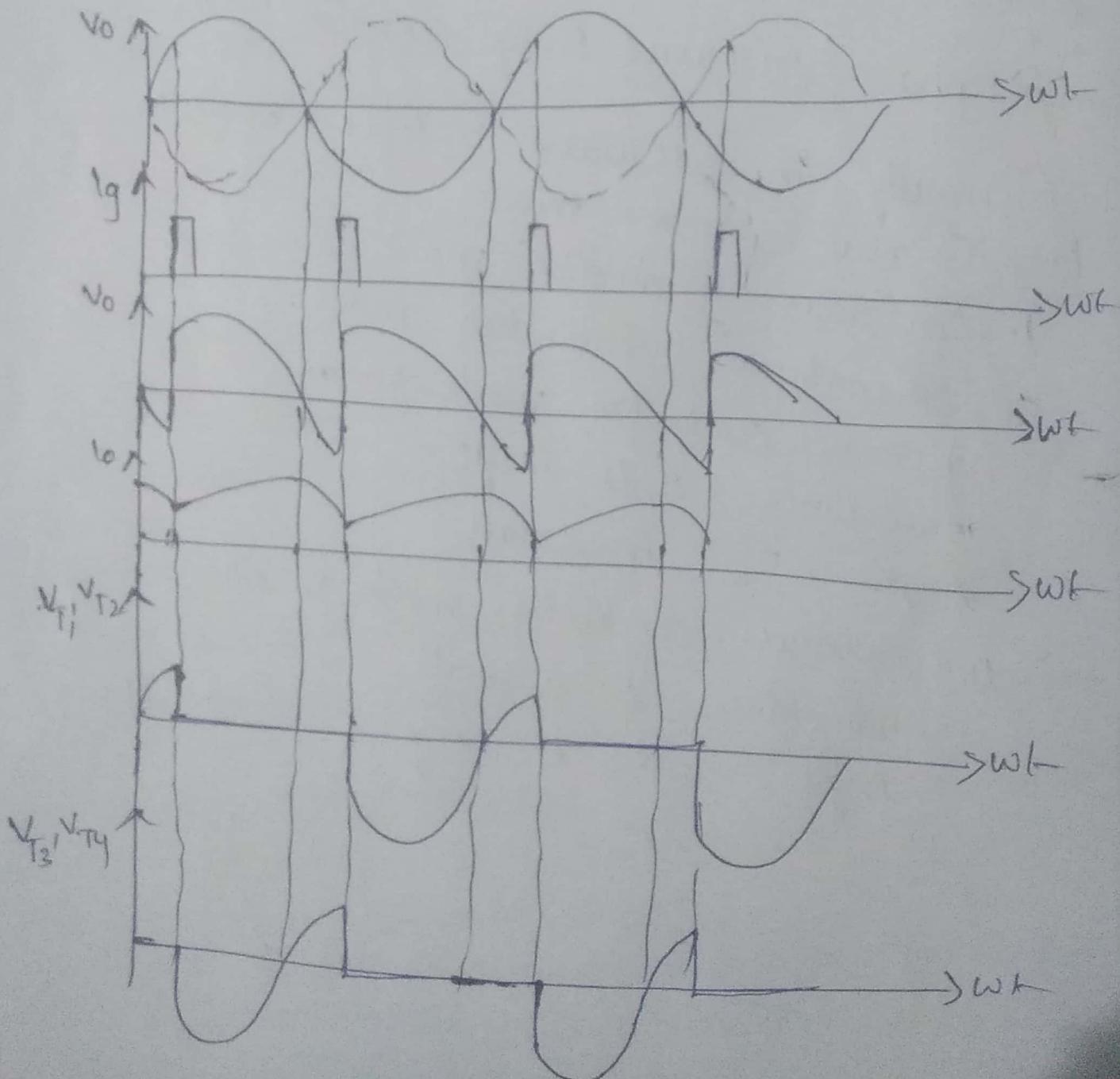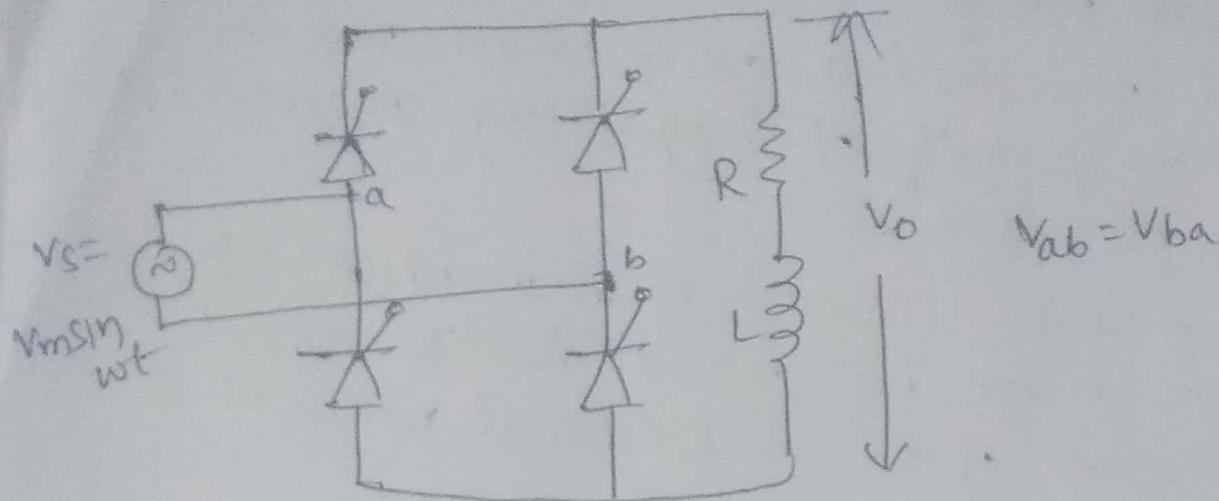1-φ full controller bridge rectifier with RL load



- The ckt consists of Thyristors T_1, ST_2, T_3, ST_4
- Voltage source V_S , ϵ RL load
- The o/p waveforms for 1-φ fullwave bridge rectifier with RL load
- ϵ firing angle α
- inductance 'L' is large, angle ' α ' is small
operation is continuous conduction mode
- inductance 'L' is small, angle α is large
operation is discontinuous conduction mode
- consider $\alpha = 30^\circ$, during the +ve halfcycle of the i/p voltage, T_1, ST_2 are forward biased, it does not conduct until gate signal is applied to them
- when gate pulse is applied T_1, ST_2 at $\alpha = 30^\circ$, it gets turns on ϵ begins to conduct.
- when i/p voltage applied to the load at $wt = \alpha$, the current through the load I_c will increase slowly because of L presence $\therefore I_c$ increases slowly ϵ reaches max. during +ve halfcycle i.e., at $wt = \pi - \alpha$ T_3, ST_4 are forward, T_1, ST_2 are reverse biased current at $T_1, ST_2 \neq 0$ \therefore If does not turns off
- conducts small in -ve half cycle, when $wt = \pi + \alpha$ gate pulse all T_3, ST_4, T_1, ST_2 are turns on the load current I_c shifts path from T_1, ST_2 to T_3, ST_4 , then T_1, ST_2 turns off at $wt = \pi + \alpha$
- from T_1, ST_2 is off state, T_3, ST_4 are appearing when $\pi + \alpha$, voltage appears
- V_{B, T_4} is in not appearing as in off state, appearing at T_1, ST_2

$$V = \frac{\text{area}}{\text{base}}$$

Avg voltage

$$V_{avg} = \int_{\alpha}^{\pi+\alpha} \frac{V_m \sin \omega t \cdot d(\omega t)}{\pi}$$

$$= \frac{V_m}{\pi} \int_{\alpha}^{\pi+\alpha} \sin \omega t \cdot d(\omega t)$$

$$= \frac{V_m}{\pi} \left[-\cos \omega t \right]_{\alpha}^{\pi+\alpha} = \frac{-V_m}{\pi} [\cos(\pi+\alpha) - \cos \alpha]$$

$$\therefore \cos(\pi+\alpha) = -\cos \alpha$$

$$= -\frac{V_m}{\pi} (-\cos \alpha - \cos \alpha)$$

$$V_{avg} = -\frac{V_m}{\pi} \times -2 \cos \alpha = \frac{V_m}{\pi} 2 \cos \alpha = \frac{2V_m}{\pi} \cos \alpha$$

$$V_{rms} = \sqrt{\int_{\alpha}^{\pi+\alpha} \frac{V_m^2 \sin^2 \omega t \cdot d(\omega t)}{\pi}} = \frac{V_m}{\sqrt{\pi}} \sqrt{\int_{\alpha}^{\pi+\alpha} \frac{1 - \cos 2\omega t}{2} d(\omega t)}$$

$$= \frac{V_m}{\sqrt{\pi/2}} \sqrt{\int_{\alpha}^{\pi+\alpha} (1 - \cos 2\omega t) d(\omega t)} = \frac{V_m}{\sqrt{\pi}} \sqrt{\int_{\alpha}^{\pi+\alpha} (\omega t)^2 \frac{d(\omega t)}{\pi} - \left(\frac{\sin 2\omega t}{2} \right)_{\alpha}^{\pi+\alpha}}$$

$$= \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi+\alpha - \alpha) - \frac{1}{2} [\sin 2(\pi+\alpha) - \sin 2\alpha]}$$

$$= \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \frac{1}{2} [\sin(2\pi+2\alpha) - \sin 2\alpha]}$$

$$= \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \frac{1}{2} (\sin 2\alpha - \sin 2\alpha)} = \frac{V_m}{\sqrt{2} \times \sqrt{\pi}} \times \sqrt{\pi}$$



$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

- 1- ϕ fully controlled bridge rectifier with RL load
(with DIS continuous conduction)
- Suppose $\alpha = 90^\circ$, during the +ve half cycle, thyristors T_1, T_2 are forward biased, T_3, T_4 are reverse biased at $\alpha = 90^\circ$, we are giving at gate pulses to T_1, T_2 for the supply voltage V_s across the RL load
- During the +ve half cycle T_1, T_2 conducts so the o/p current increases slowly at $wt = \pi$ due to the presence of inductor L, the current slowly reaches the zero value
so, a small -ve voltage appears across the ~~load~~
So, a small -ve voltage appears across the ~~load~~
- During the -ve half cycle, T_1, T_2 are reverse biased T_3, T_4 are forward biased at $wt = \pi + \alpha$ firing pulses are given to T_3, T_4 so this voltage V_{ba} appearing across the load,
- here also load increases slowly at $wt = 2\pi$ due to the presence of inductor output current decreases slowly to zero. So a -ve voltage appears across the load (T_3, T_4), so here the load current I_c is DIS continuous.
- By referring o/p. voltage we can draw $v_{T_1}, v_{T_2}, v_{T_3} \& v_{T_4}$



$$V_{oavg} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d\omega t$$

$$V_{oms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t)}$$

Ckt & waveforms

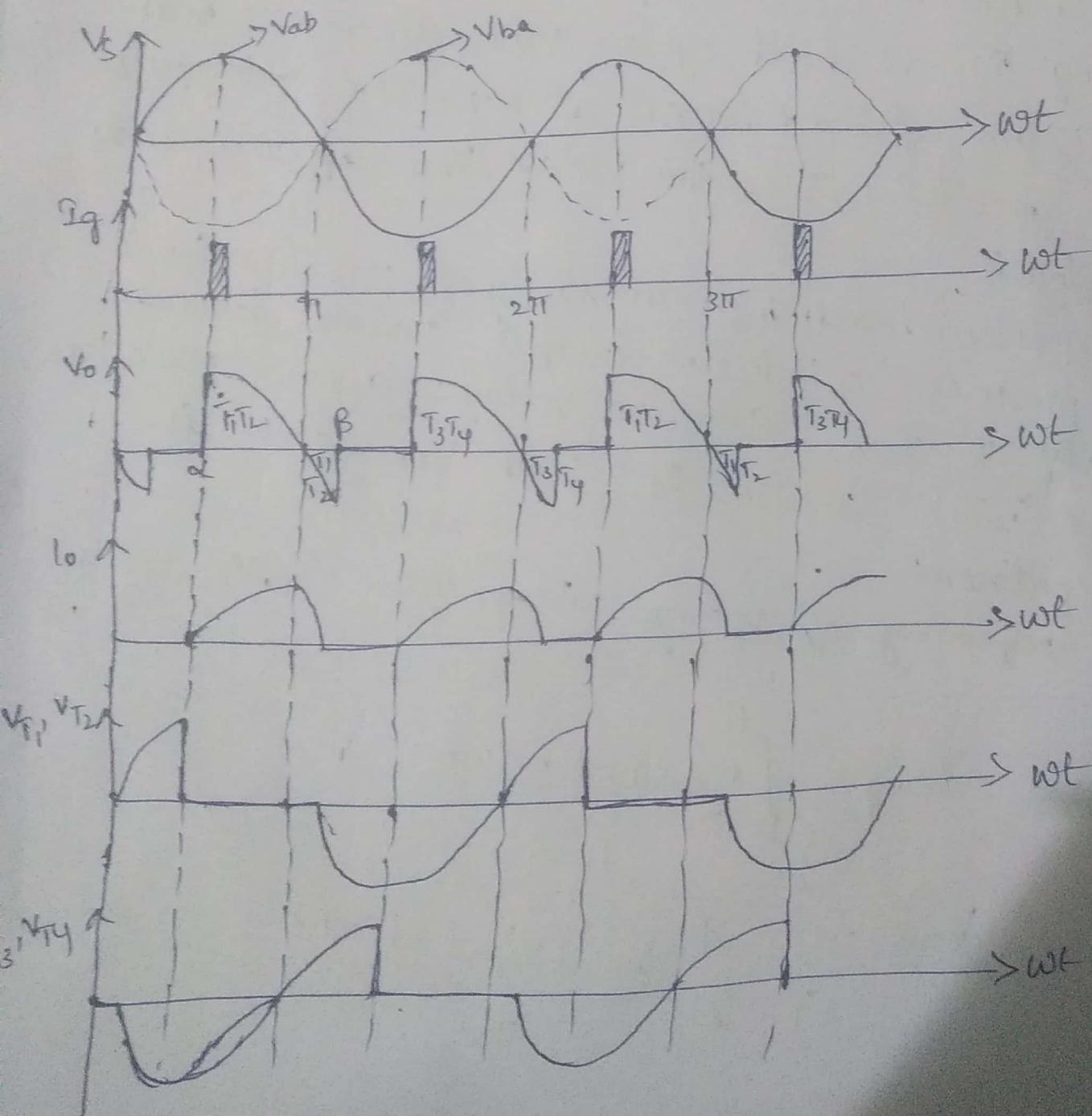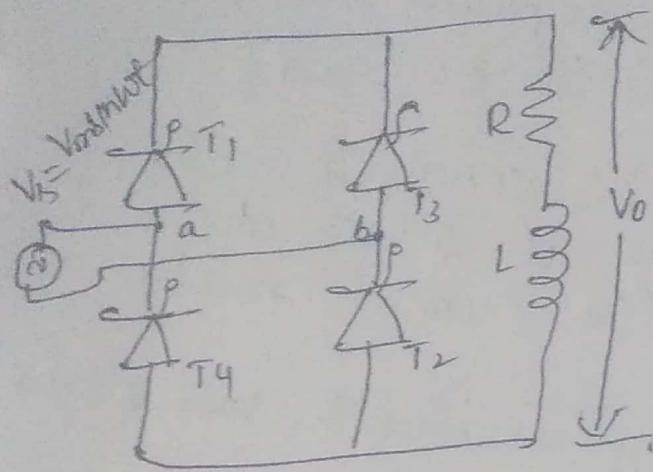

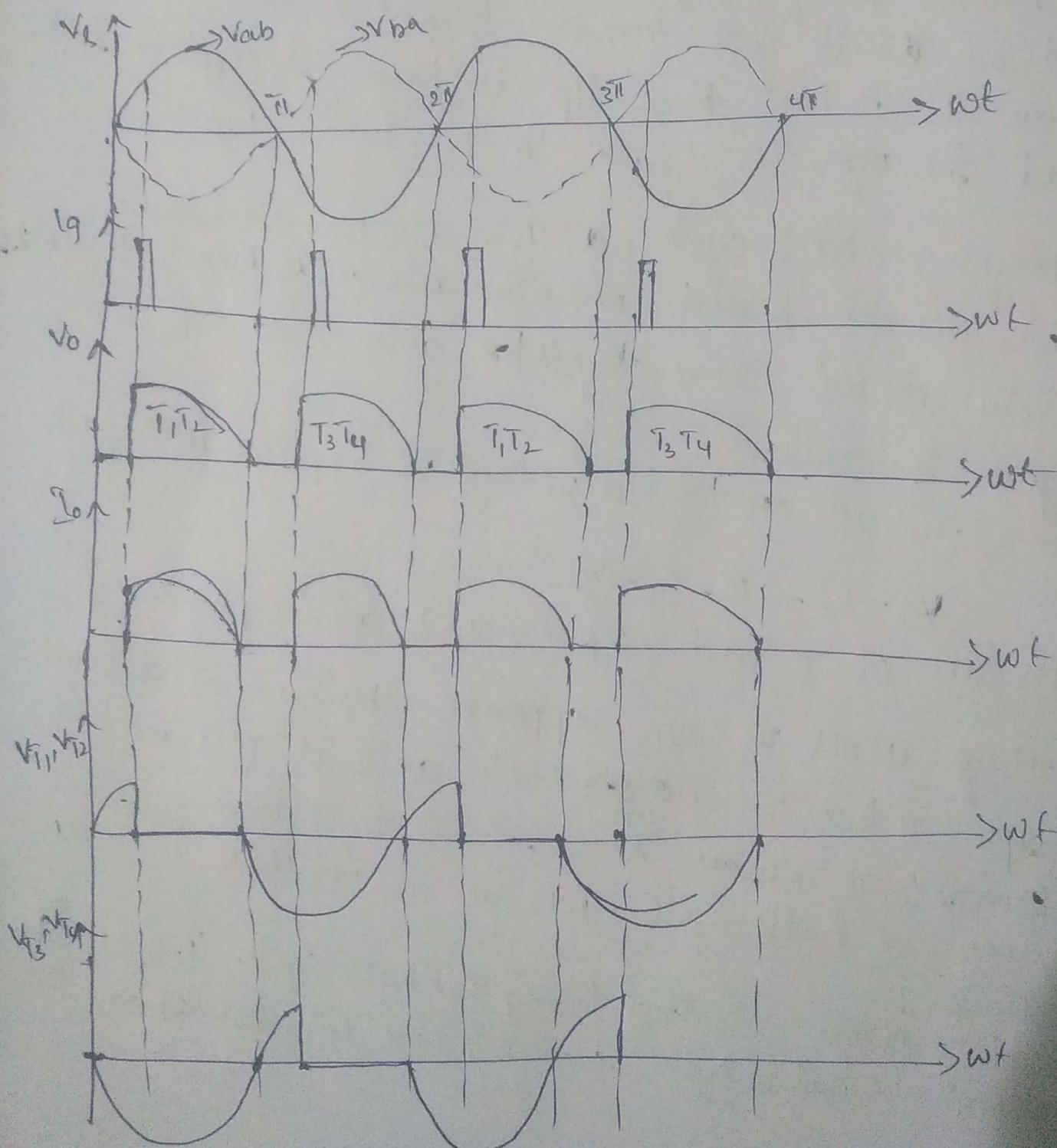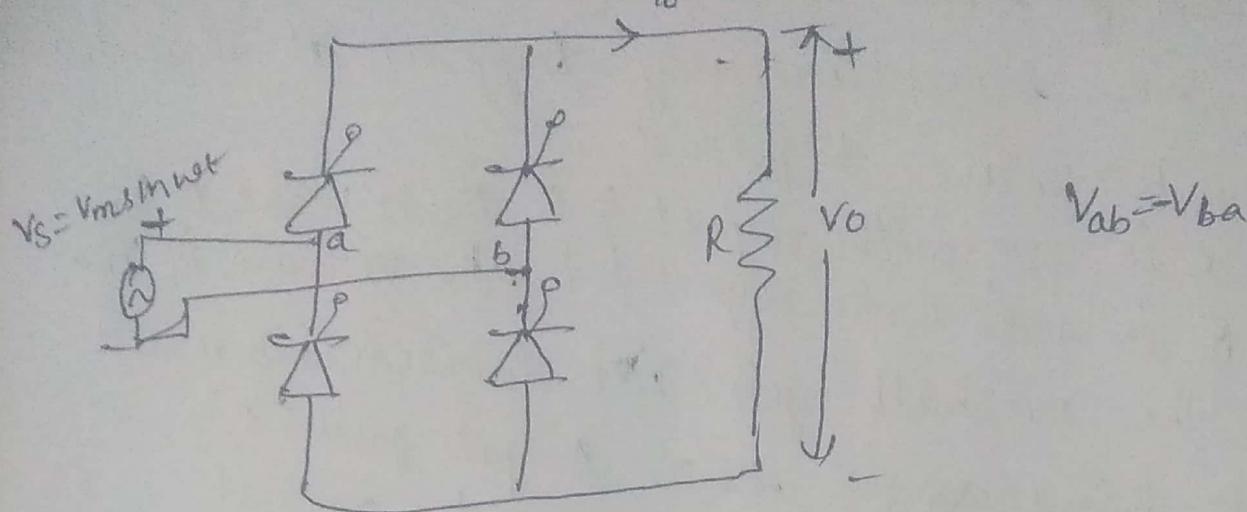1-Ø fully controlled bridge rectifier with R-load :-



- CKts consists of 4 thyristors T_1, T_2, T_3 & T_4 at a voltage source V_s and resistive load R
- T_1, T_2 are simultaneously triggered at π radians later, T_3, T_4 are triggered
- when 'a' is +ve with respect to b the V_s wave is V_{ab}
b is +ve with respect to a the V_s wave is V_{ba}
- During the +ve half cycle T_1 is forward biased, T_3, T_4 is reverse consider fixing angle $\alpha = 30^\circ$ for gate pulses T_1, T_2
- at $wt = \alpha$ it gets turn on begins to conduct when T_1, T_2 is on this i/p voltage is applied to the load through the path $V_s - T_1 - \text{load} - T_2 - V_s$
- During -ve half cycle, T_3, T_4 are forward biased T_1, T_2 reverse biased when the gate pulse given to thyristors T_3, T_4 at $wt = \pi + \alpha$ thyristors gets turns on and begins to conduct when T_3, T_4 are on the i/p voltage V_s applied to the path $V_s - T_3 - R - T_4 - V_s$
- In case of R load o/p V_s & o/p I are in phase.
- Voltage across V_1, V_2 appears during +ve half cycle upto $0 \leq \alpha, T_1, T_2$ in ~~on~~ state acts as open switch from α to π T_1, T_2 are $S:C$, so zero voltage
- During -ve half cycle T_1, T_2 are in off state in reverse voltage
- Voltage across V_3, V_4 during +ve half cycle T_3, T_4 are ~~on~~ off during -ve half cycle from π to $\pi + \alpha$ T_3, T_4 are ~~off~~ on

$$\begin{aligned}
 V_{avg} &= \int_{\alpha}^{\pi} \frac{V_m \sin \omega t \, d(\omega t)}{\pi} \\
 &= \frac{V_m}{\pi} \int_{\alpha}^{\pi} \sin \omega t \cdot d(\omega t) \\
 &= \frac{V_m}{\pi} \left[-\cos \omega t \right]_{\alpha}^{\pi} \\
 &= -\frac{V_m}{\pi} [\cos \pi - \cos \alpha] \\
 &= -\frac{V_m}{\pi} [-1 - \cos \alpha] = \frac{V_m}{\pi} [1 + \cos \alpha]
 \end{aligned}$$


$$I_{avg} = \frac{V_{avg}}{R}$$

$$\begin{aligned}
 V_{rms} &= \sqrt{\frac{\int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t)}{\pi}} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t)} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{\int_{\alpha}^{\pi} (1 - \cos 2\omega t) \cdot d(\omega t)} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{(2\omega t)_{\alpha}^{\pi} - \left(\frac{\sin 2\omega t}{2} \right)_{\alpha}^{\pi}} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) - \frac{1}{2} \{ \sin 2\pi - \sin 2\alpha \}} \quad \therefore \sin 2\pi = 0 \\
 V_{rms} &= \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{2}}
 \end{aligned}$$

$$I_{rms} = \frac{V_{rms}}{R}$$


1-Φ fully controlled bridge Rectifier with RLB load

continuous conduction

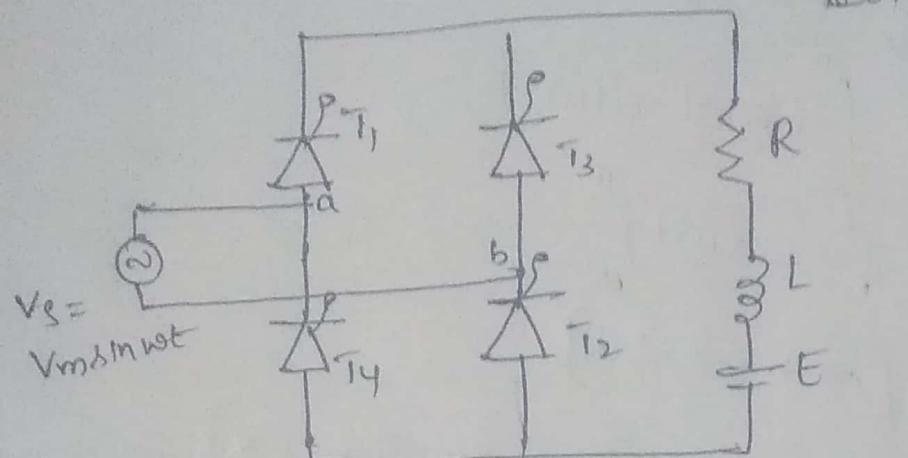

$$V_m \sin \omega t > E$$

$$V_{ab} = -V_{ba}$$

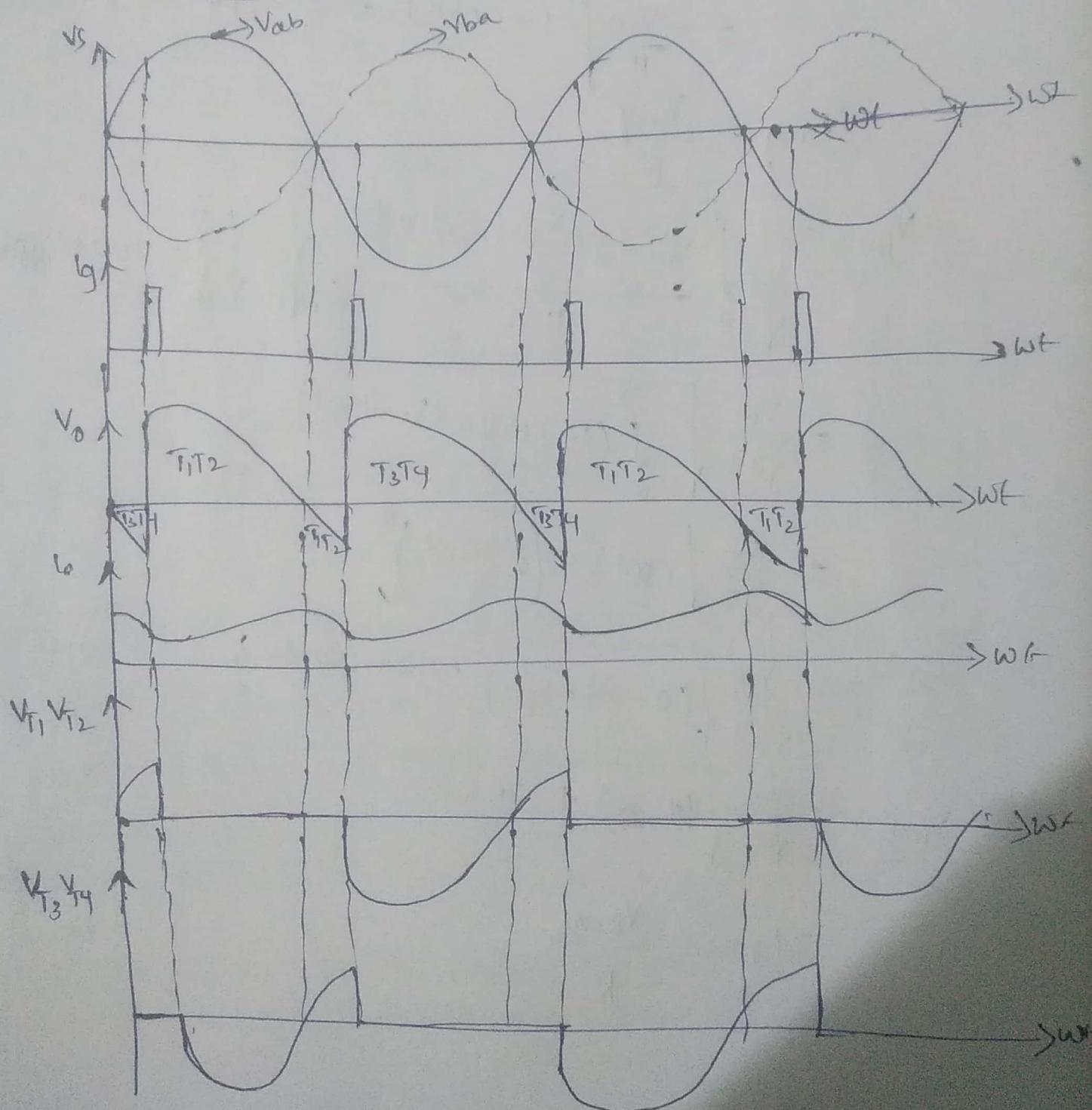

- During positive half cycle the thyristors T_1, T_2 are forward biased, T_3, T_4 are reverse biased
 - at $\omega t = 30^\circ$, firing pulses are applying at T_1, T_2
 $\therefore \omega t = \alpha$ T_1, T_2 are turned on. and the i/p voltage v_s is applied to the load.
And here current gradually increases
 - at $\omega t = \pi$ i.e., during the -ve half cycle
 T_3, T_4 are forward bias, T_1, T_2 are reverse biased
but the current at the thyristors T_1, T_2 are not zero during the presence of inductor L due
 - π to $\pi + \alpha$ the current through the inductor L begins to $V_k \neq 0$ and T_1, T_2 conducts for a small duration of -ve half cycle
 - $\omega t = \pi + \alpha$ firing pulses are given to T_3, T_4
 T_3, T_4 are turns on, so the load current shifted to T_3, T_4 from T_1, T_2 ,
current increases gradually.
 - when α to π , T_1, T_2 are off, then V_{T_1}, V_{T_2} are appearing across the thyristors.
From α to $\pi + \alpha$ T_1, T_2 are ON, so, V_{T_1}, V_{T_2} are zero
from $\pi + \alpha$ to $2\pi + \alpha$ T_1, T_2 are in OFF state
 - when α to π T_3, T_4 are ON, $\therefore V_{T_3}, V_{T_4}$ are zero
 α to $\pi + \alpha$ T_3, T_4 are OFF, V_{T_3}, V_{T_4} are reverse
- ~~$\pi + \alpha$ to $2\pi + \alpha$~~

$$\begin{aligned}
 V_{avg} &= \frac{1}{\pi} \int_{-\alpha}^{\pi+\alpha} V_m \sin \omega t \cdot d(\omega t) \\
 &= \frac{V_m}{\pi} \int_{-\infty}^{\pi+\alpha} \sin \omega t \cdot d(\omega t) \\
 &= \frac{V_m}{\pi} [-\cos \omega t]_{-\alpha}^{\pi+\alpha} = -\frac{V_m}{\pi} [\cos(\pi + \alpha) - \cos \alpha] \\
 &= -\frac{V_m}{\pi} [-\cos \alpha - \cos \alpha] = \frac{2V_m}{\pi} \cos \alpha
 \end{aligned}$$

$$V_{avg} = \frac{2V_m}{\pi} \cos \alpha$$

$$I_{avg} = \frac{V_{avg}}{R}$$



$$\begin{aligned}
 V_{rms} &= \sqrt{\frac{1}{\pi} \int_{-\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t \cdot d(\omega t)} = \frac{V_m}{\sqrt{\pi}} \sqrt{\int_{-\alpha}^{\pi+\alpha} \left(\frac{1 - \cos 2\omega t}{2} \right) d(\omega t)} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{\int_{-\infty}^{\pi+\alpha} (1 - \cos 2\omega t) \cdot d(\omega t)} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\left[(\omega t) \right]_{-\alpha}^{\pi+\alpha} - \left[\frac{\sin 2\omega t}{2} \right]_{-\alpha}^{\pi+\alpha}} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi + \alpha - \alpha) - \frac{1}{2} (\sin(2\pi + 2\alpha) - \sin 2\alpha)} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \frac{1}{2} (\sin 2\alpha - \sin 2\alpha)} = \frac{V_m}{\sqrt{2\pi}} \times \sqrt{\pi} - \frac{V_m}{\sqrt{2}}
 \end{aligned}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{V_{rms}}{R}$$

Discontinuous conduction

$$\alpha = 90^\circ$$

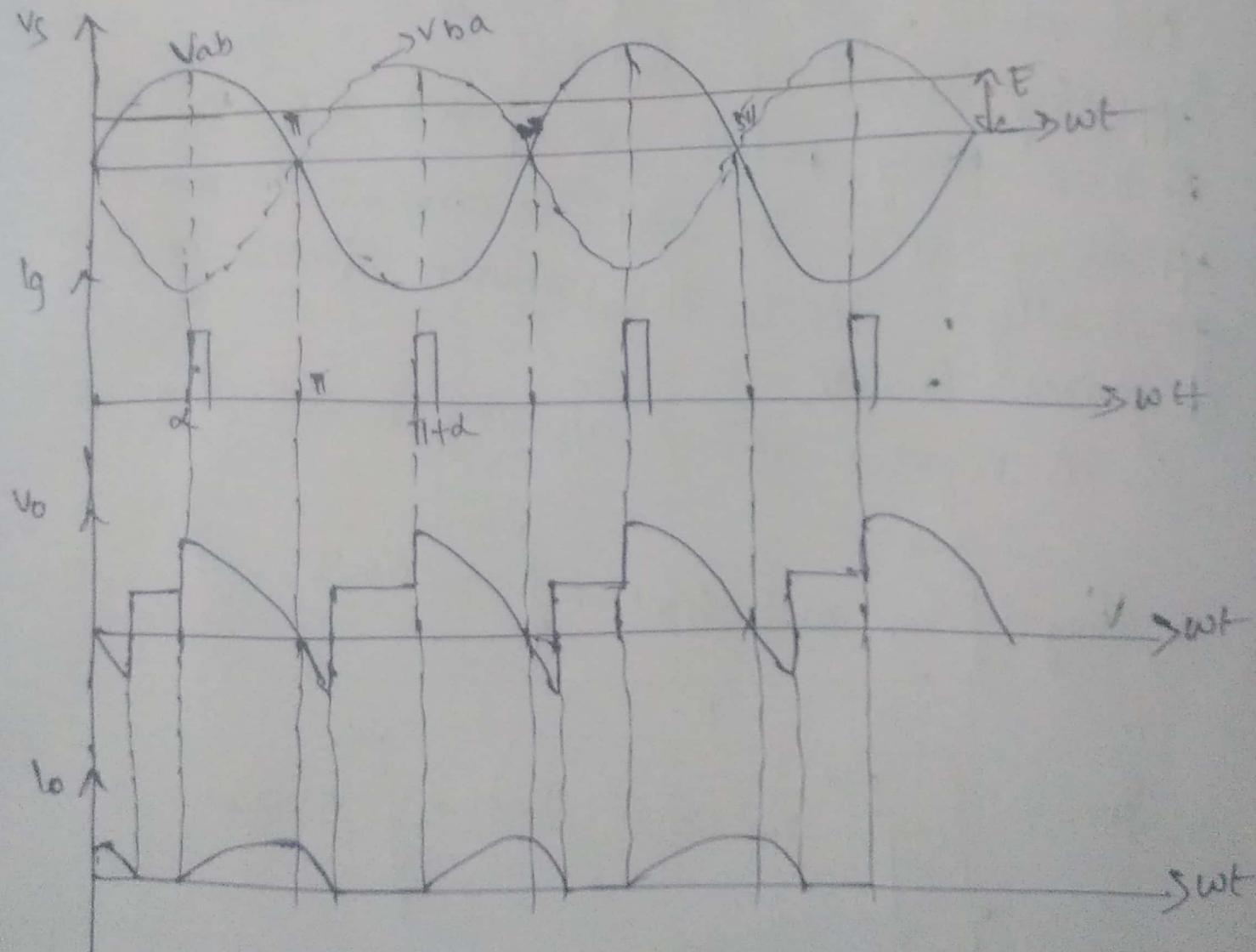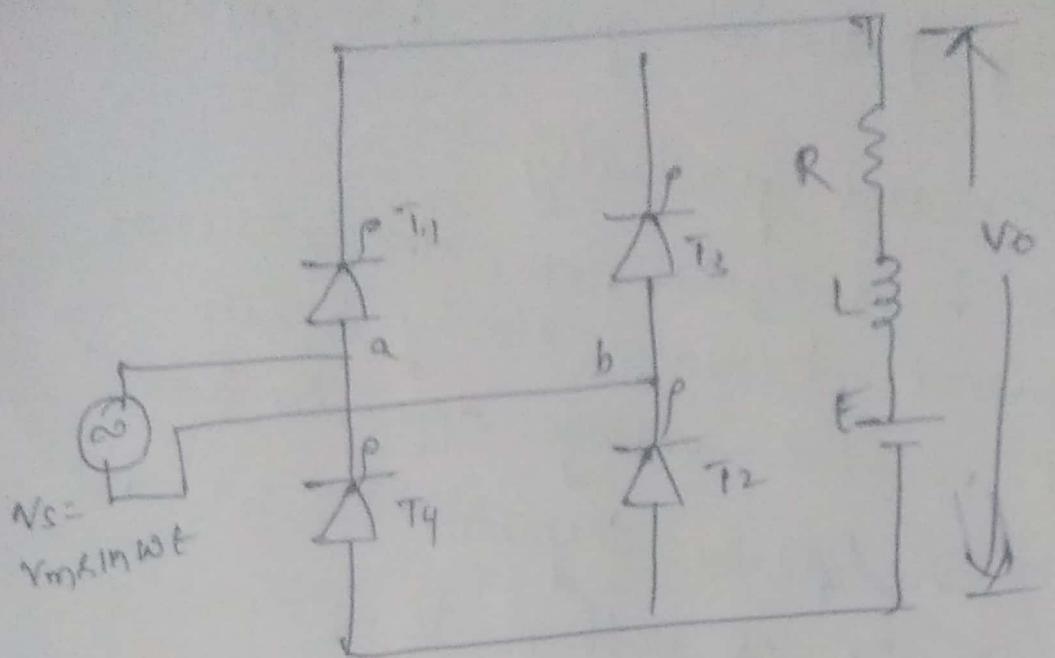


- At $\alpha = 90^\circ$, during +ve half cycle ~~T₁T₂ are forward, T₃T₄ are reverse~~
 T₁T₂ are forward, T₃T₄ are reverse
 wt = π , firing pulses are given to T₁T₂ are turns on
 across the V_s.
 current increases gradually
- during -ve half cycle, due to the presence of
 inductor current decreases slowly to zero
 \therefore A small negative voltage appears across the load
- when $\beta \leq \pi + \alpha$ All the thyristors T₁T₂T₃T₄ are
 off state. So, the op voltage V_o = E
 so, V_o appearing across the load.
- At $\pi + \alpha$ firing pulses are given to T₃T₄ so V_{ba}
 appearing across the load. So current increases
 gradually. due to the presence of inductor current
 decreases to zero.
 So, a negative voltage appearing across the load.


$$V_{avg} = \frac{\int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \cdot d(\omega t) + \int_{\pi}^{\pi+\alpha} E \cdot d(\omega t)}{\pi}$$

$$V_{rms} = \sqrt{\int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t \cdot d(\omega t) + \int_{\pi}^{\pi+\alpha} E^2 \cdot d(\omega t)}$$

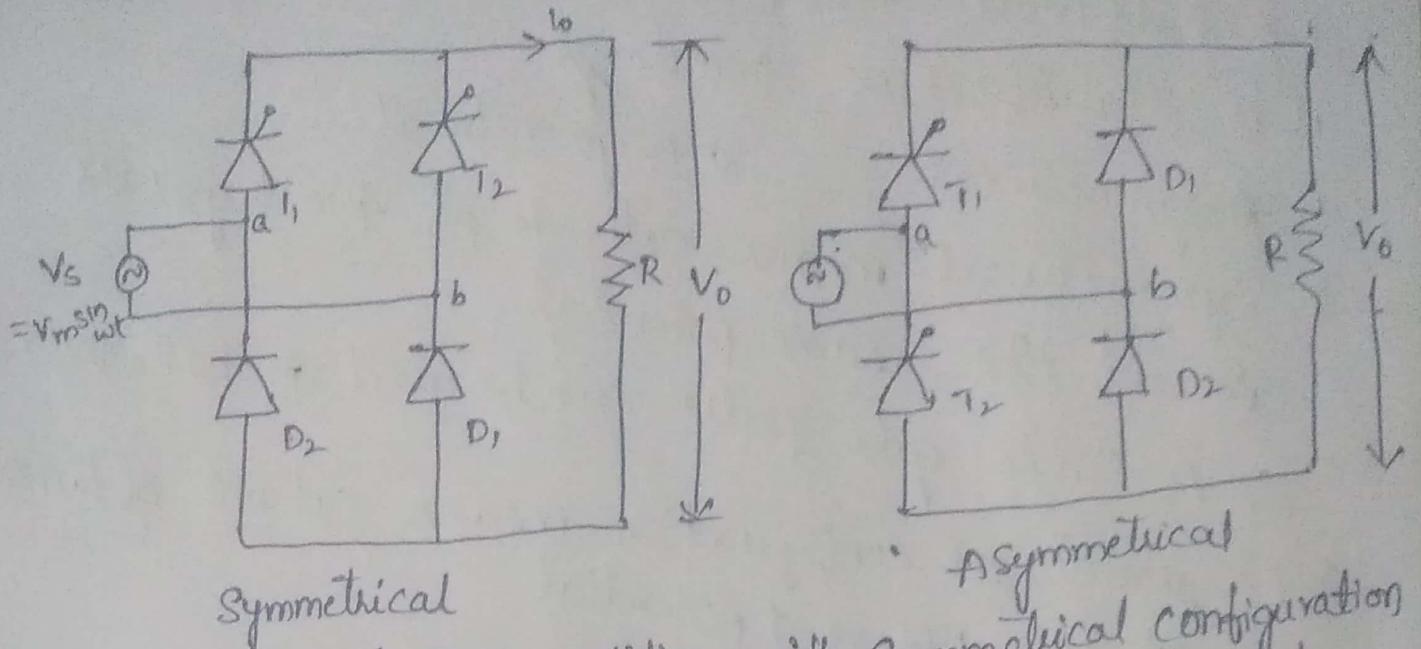→ Single phase semi-controlled Bridge Rectifier with R-load



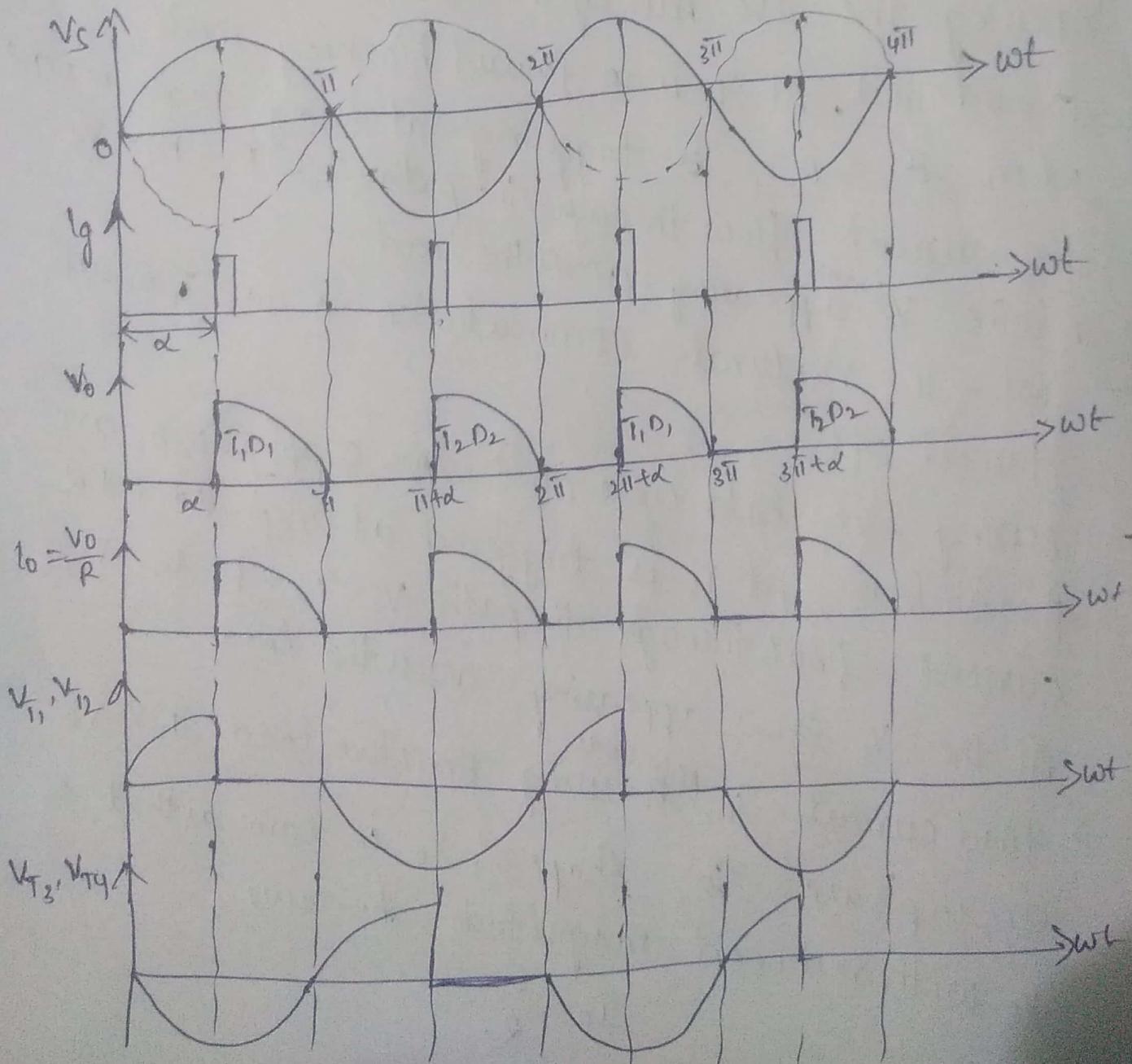1-φ semi controlled rectifier with symmetrical configuration
for R-Load



- A 1-Ø semi controlled converter is also known as half wave rectifier
 It is classified as two ways
1. Symmetrical
 2. Asymmetrical
- Symmetrical means cathode of two thyristors are at the same potential.
 ∵ A single gate pulse can be used for both the SCR's.
- A symmetrical configuration means cathode of two SCRs are at the different potential.
- During the +ve half cycle of the AC supply T_1, D_1 are forward biased. At T_1 is in forward blocking mode when SCR T_1 is triggering at firing angle $\alpha = 90^\circ$. The current flows through the path $V_s - T_1 - R - D_1 - V_s$. At the $V_s^{(evab)}$ appearing across the load commutation occurs T_1, D_1 are turned off.
- During -ve half cycle of the AC supply T_2, D_2 are forward biased. At T_2 is triggered at angle $\pi + \alpha$. Current flows through the path $V_s - T_2 - R - D_2 - V_s$. At the $V_s^{(evab)}$ appearing across the load
- Load current I_o , using Resistive load $I_o \leq V_o$ are in phase. So, shape of I_o is same as that of V_o with reduced magnitude because
- $$I_o = \frac{V_o}{R}$$



Vacross $T_1 D_1$
 \rightarrow from 0 to α $T_1 D_1$ are in off state. $\therefore V_{ab}$ appears across the switch $T_1 D_1$
 from α to π $T_1 D_1$ are S.C., i.e., no voltage appears across the switches
 from π to $2\pi + \alpha$ $T_1 D_1$ are off state. i.e., supply voltage appears across the switches $T_1 D_1$

Similarly Vacross $T_2 D_2$
 from 0 to $\pi + \alpha$ $T_2 D_2$ are in off state. $\therefore V_{ba}$ appearing across the switches

$$\begin{aligned}
 \Rightarrow V_{avg} &= \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t) \\
 &= \frac{V_m}{\pi} \int_{\alpha}^{\pi} \sin \omega t \cdot d(\omega t) = \frac{V_m}{\pi} [-\cos \omega t]_{\alpha}^{\pi} \\
 &= \frac{V_m}{\pi} [+\cos \pi - \cos \alpha] = -\frac{V_m}{\pi} [-1 - \cos \alpha]
 \end{aligned}$$

$$\begin{aligned}
 \therefore V_{avg} &= \frac{V_m}{\pi} \cos \alpha \\
 V_{Rms} &= \sqrt{\frac{1}{\pi} \int_{0}^{\pi} V_m^2 \sin^2 \omega t d(\omega t)} = \sqrt{\frac{V_m^2}{\pi} \int_{0}^{\pi} \left(1 - \frac{\cos 2\omega t}{2}\right) d(\omega t)} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{\int_{\alpha}^{\pi} (1 - \cos 2\omega t) d(\omega t)} = \frac{V_m}{\sqrt{2\pi}} \sqrt{(wt)_{\alpha}^{\pi} - \left(\frac{\sin 2\omega t}{2}\right)_{\alpha}^{\pi}} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) - \frac{1}{2} (\sin 2\pi - \sin 2\alpha)} \\
 &= \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{2}}
 \end{aligned}$$

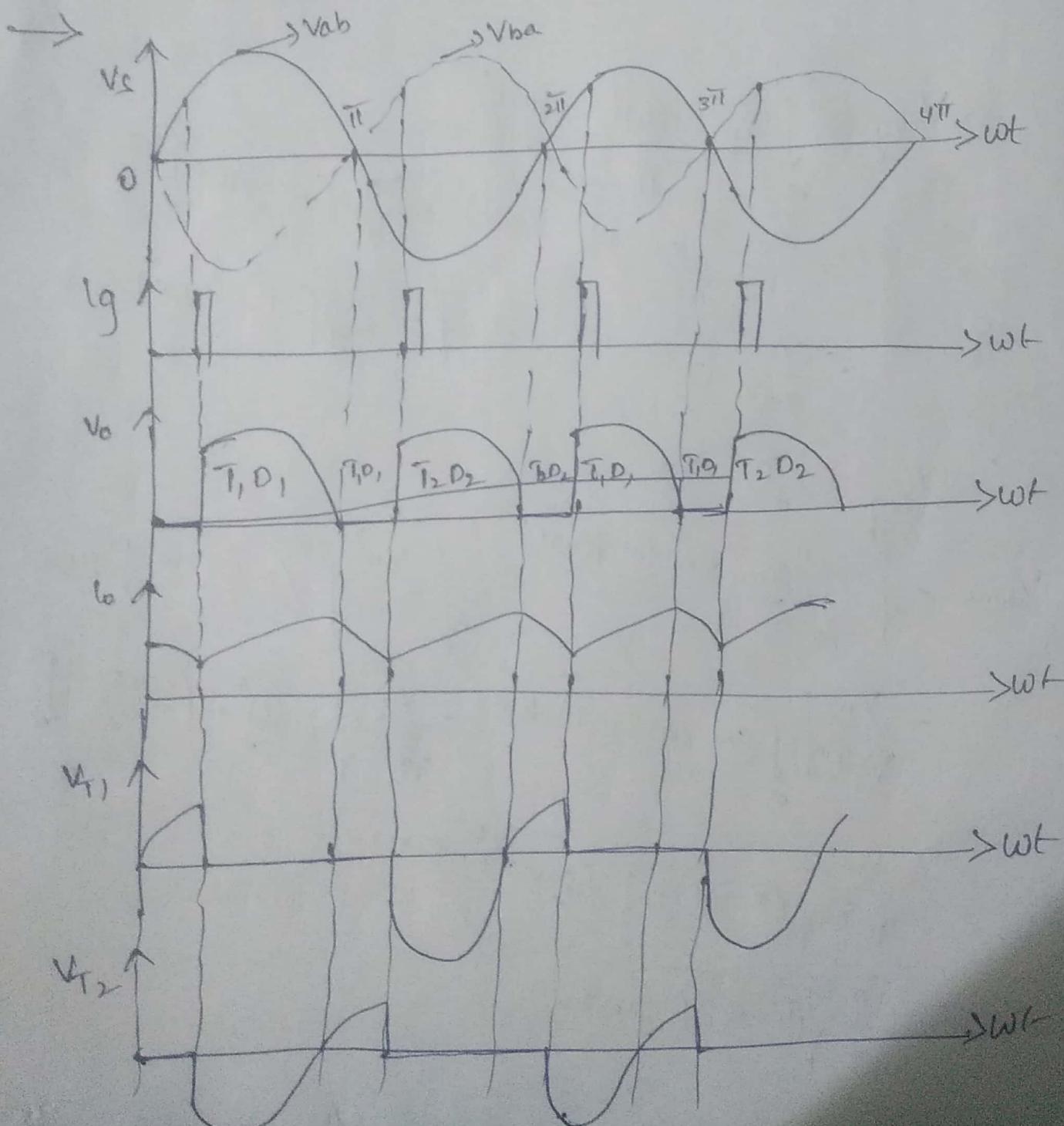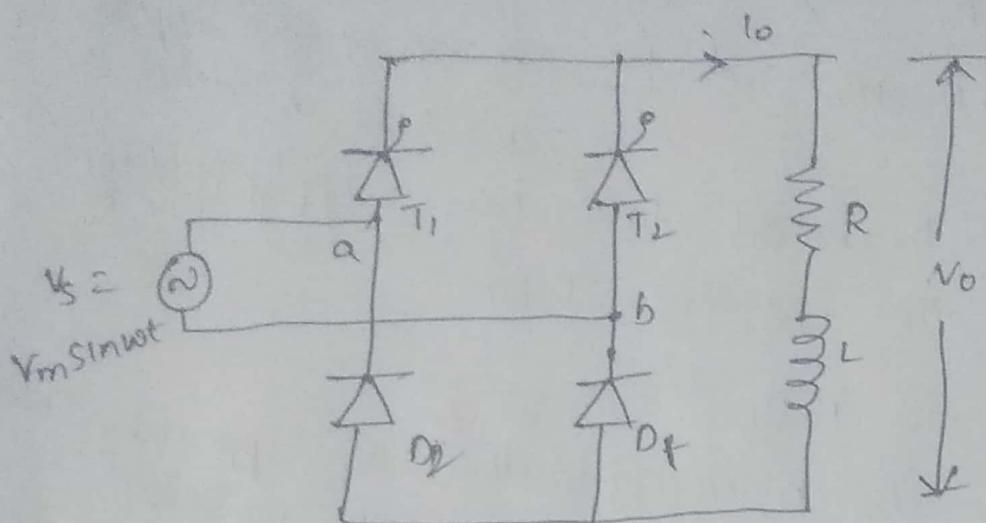\Rightarrow 1- ϕ Semi converter (symmetrical) with RL-load



→ Ckt consists of two SCRs T_1, T_2 Diodes D_1, D_2

Voltage source V_s along with RL load

→ During +ve half i/p voltage V_s the SCR T_1, D_1 are forward biased but transistor T_1 does not conduct until a gate pulse is applied to T_1 .

At $wt = \alpha = 30^\circ$, A gate pulse is given to T_1 , turns on T_1 , and begins to conduct V_s appears across the load due to the presence of 'L' the current increases gradually.

→ During -ve half cycle T_2, D_2 are forward biased due to the presence of 'L' the T_2 is forcedly in the ON state

from π to $\pi + \alpha$ T_2, D_2 conducts, so it acts as s.c ($V_o = 0$)
to shifted to (π shifted to T_2, D_2) from π to $\pi + \alpha$

so, current decreases slowly.

→ When a gate pulse is given to T_2 at $wt = \pi + \alpha$ T_2 get turned on and begins to conduct when T_2, D_2 on the voltage V_{ba} appears across the load when T_2, D_2 on current increases gradually.

T_2, D_2 on current increases gradually

→ During +ve half cycle T_1, D_1 are forward biased due to the presence of 'L' the T_1 is forcedly in the ON state

from 2π to $2\pi + \alpha$ T_1, D_1 conducts so it acts as s.c ($V_o = 0$)

(π shifted to T_1, D_1) from 2π to $2\pi + \alpha$

so, current decreases slowly.


from $0 \leq \alpha < \pi$, T_1 is in off state, V_{ab} appearing across the switch, $\pi + \alpha < 2\pi$, T_1 is in off state V_{ab} appearing across the switch, $\pi + \alpha < 2\pi$, T_2 is in off state, ~~V_{ab} appears across the open switch~~ $\alpha < \pi + \alpha < 2\pi$, T_2 is in ON state, acts as open switch


$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{avg} = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$V_{Rms} = \frac{V_m}{\sqrt{2\pi}} \sqrt{(\pi - \alpha) + \frac{\sin 2\alpha}{\alpha}}$$

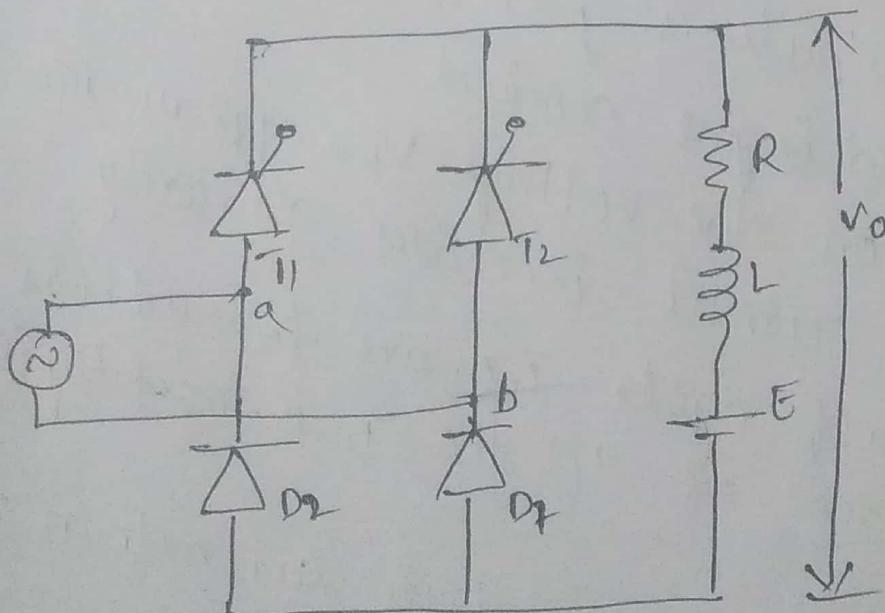\Rightarrow 1-φ semi converter (symmetrical) with RLE load



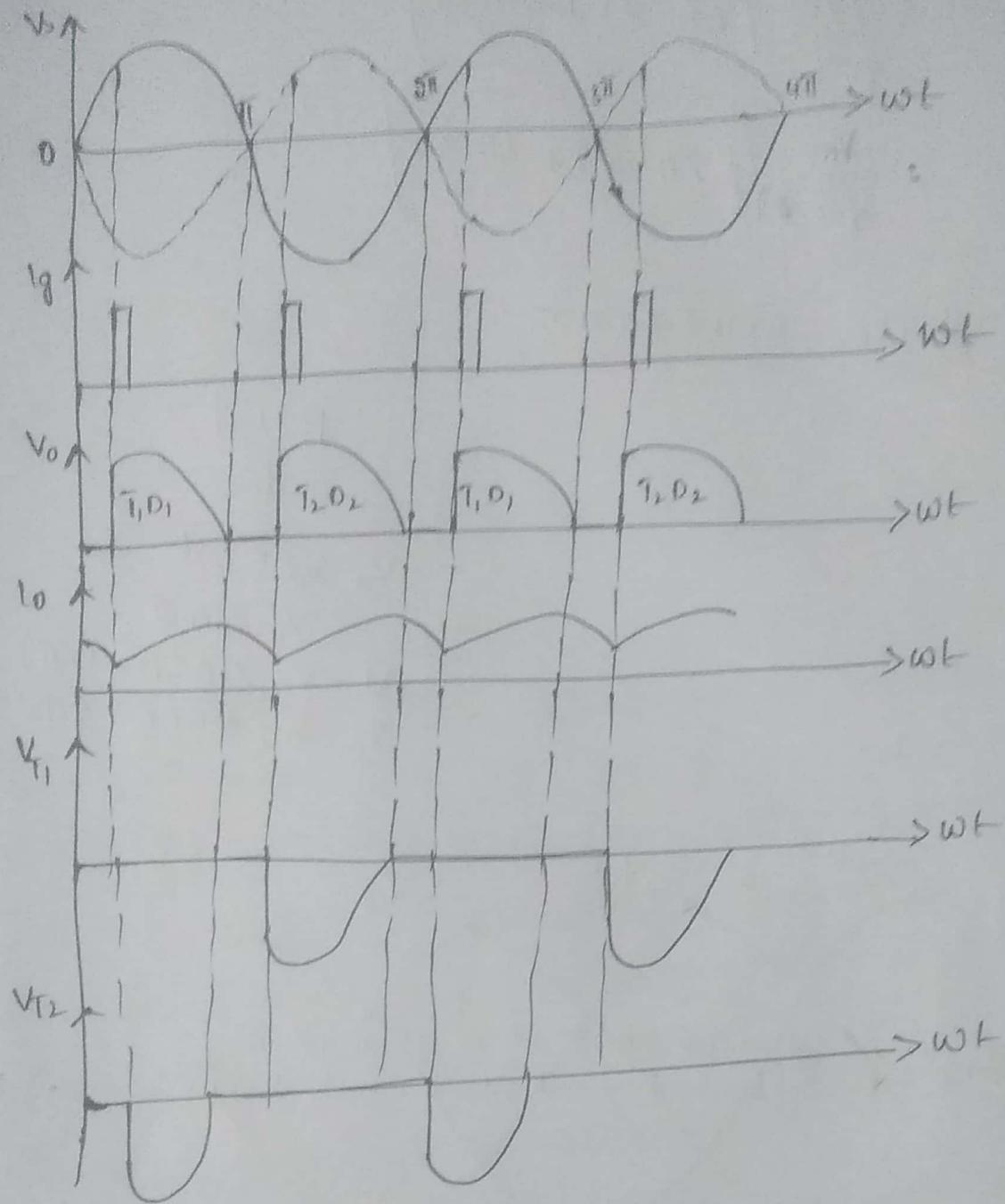

Average o/p voltage

$$V_{avg} = \frac{1}{\pi} \int_{-\pi}^{\pi} \frac{V_m \sin \omega t \cdot d(\omega t)}{\pi}$$

$$= \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$V_{rms} = \sqrt{\frac{\int_{-\pi}^{\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t)}{\pi}}$$

$$= \sqrt{\frac{V_m^2}{2\pi}} \left[\left(\omega t - \frac{\sin 2\omega t}{2} \right) \right]^{\pi}_0$$

$$= \sqrt{\frac{V_m^2}{\pi}} \left[(\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]$$

$$= \frac{V_m}{\sqrt{\pi}} \left[(\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]$$

Three phase wave-forms:-

R Y B



a' b' c'

$$V_a = V_m \sin \omega t$$


$$= V_m \sin \theta$$

$$V_b = V_m \sin(\theta - 120^\circ)$$

$$V_c = V_m \sin(\theta - 240^\circ)$$

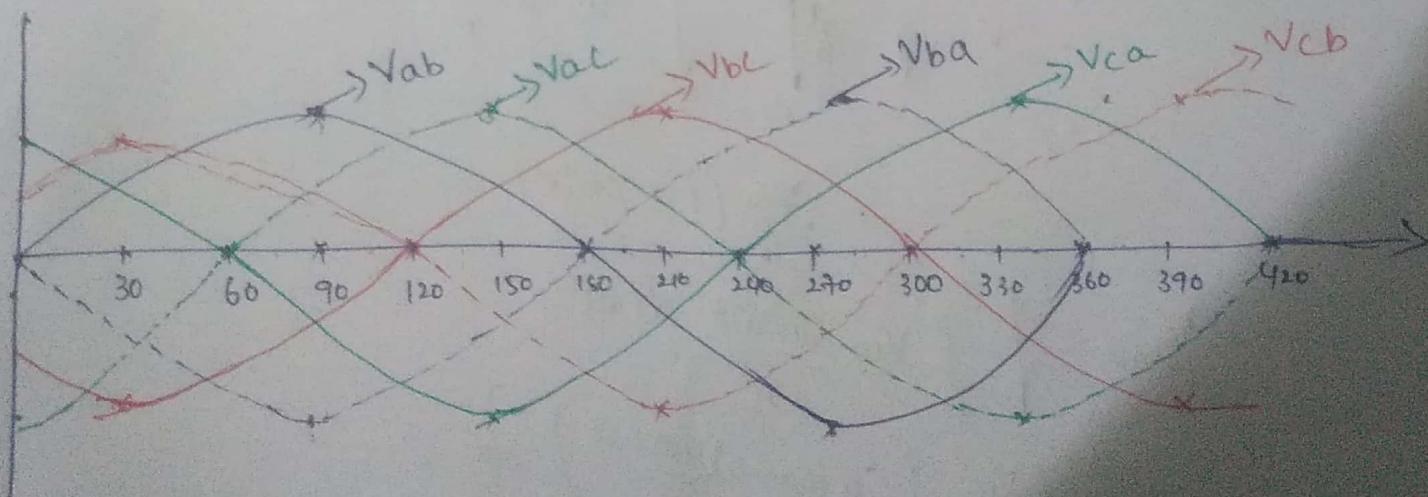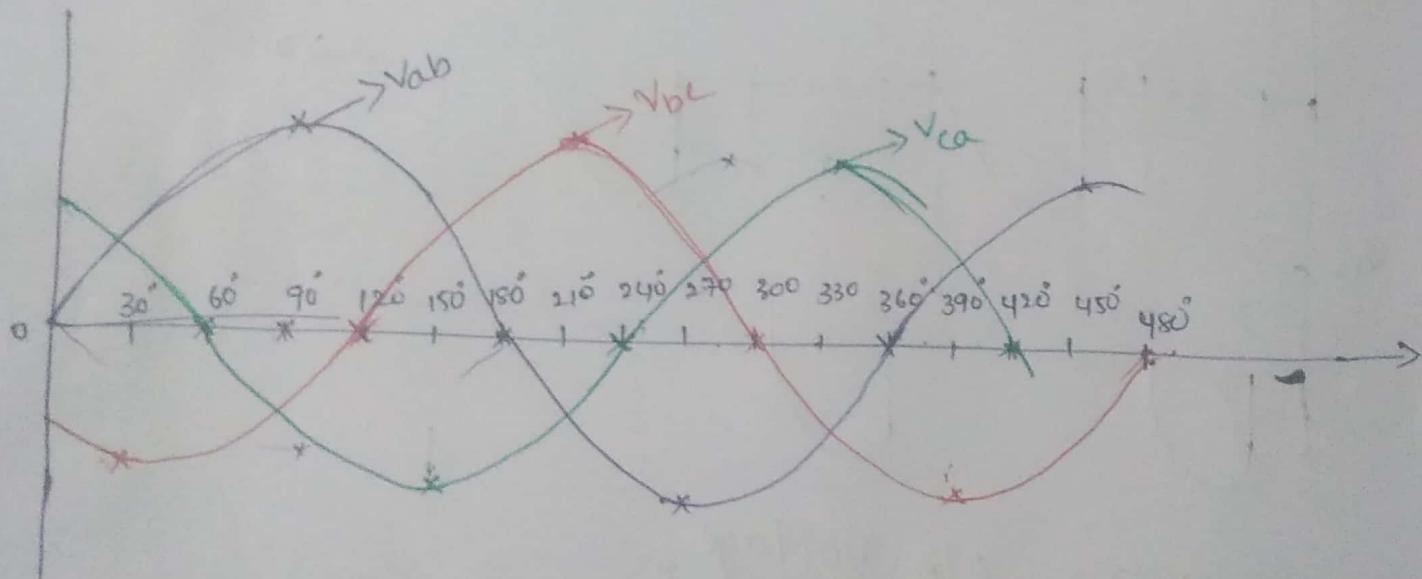

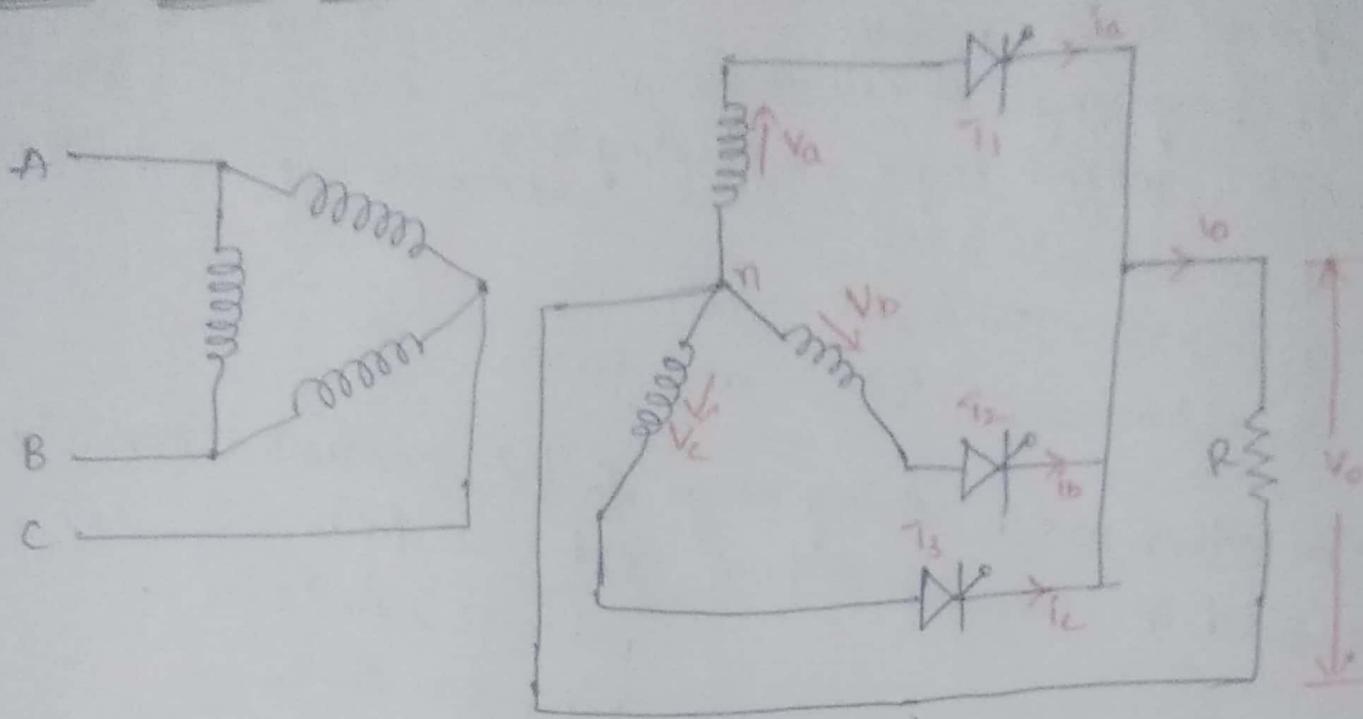3-φ half wave controlled Rectifier with R-load:



- A ckt consists of a delta-star transformer at 3-thyristors T_1, T_2, T_3 , which are connected on secondary winding star connected at a R-load
- In this ckt 3-φ power supply available the converter through 3-φ transformer with Δ-primary Y-secondary
- V_a, V_b, V_c is the phase voltage.
↳ output (or) load current
↳ output (or) load voltage
- when V_a is +ve, T_1 becomes forward biased and conducts during -ve half cycle of ~~Va~~, V_a . T_1 turns off. If T_2, T_3 conduct only during the +ve cycles of V_b & V_c respec.

→ consider 3-φ supply voltage

from 0 to 30° V_L ~~is zero~~

→ If firing angle is zero degree.

SCR T₁ would begin conducting from

T₁ → 30 to 150

T₂ → 150 to 270

T₃ → 270 to 390


T₁ → wt = 30 to 150

T₂ → wt = 150 to 270

T₃ → wt = 270 to 390 and so on.

→ In other words, firing angle for this controlled converter would be measured from
 wt = 30° for T₁,
 wt = 150° for T₂,
 wt = 270° for T₃.

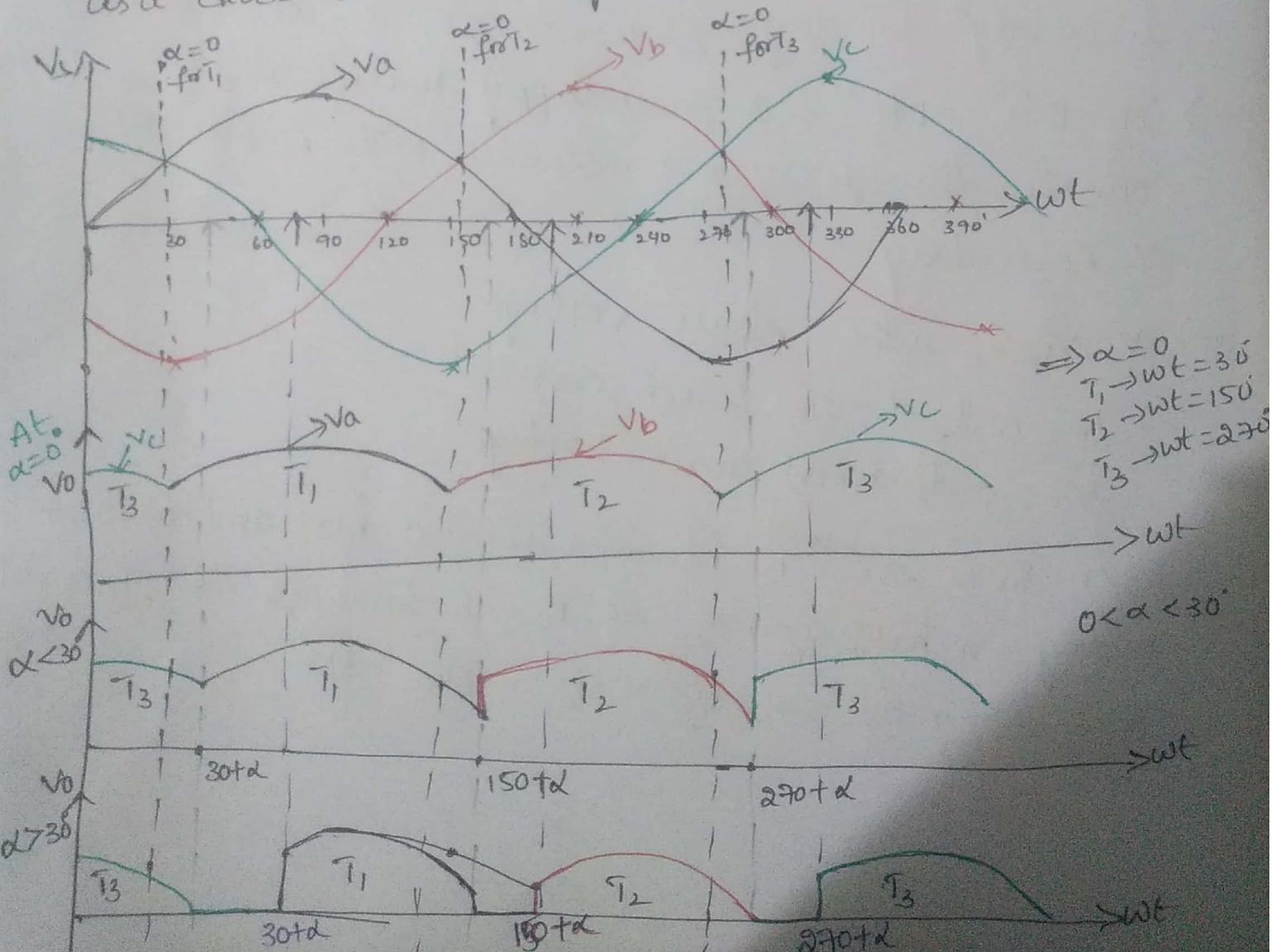→ for zero degree firing angle delay, thyristor behaves as a diode and the voltage output wave from V_O



Case i:- $\alpha < 30^\circ$.

Average value of o/p voltage,

$$\begin{aligned}
 V_o &= \frac{1}{120} \int_{30+\alpha}^{150+\alpha} V_m \sin \omega t \cdot d(\omega t) = \frac{V_m}{120} \int_{30+\alpha}^{150+\alpha} \sin \omega t \, d(\omega t) \\
 &= \frac{V_m}{2\pi/3} \left[-\cos \omega t \right]_{30+\alpha}^{150+\alpha} \\
 &= -\frac{3V_m}{2\pi} \left[\cos(150+\alpha) - \cos(30+\alpha) \right] \\
 &\approx -\frac{3V_m}{2\pi} \left[(\cos 150 \cdot \cos \alpha - \sin 150 \cdot \sin \alpha) - (\cos 30 \cdot \cos \alpha - \sin 30 \cdot \sin \alpha) \right] \\
 &\approx -\frac{3V_m}{2\pi} \left[\left(-\frac{\sqrt{3}}{2}\right) \cos \alpha - \frac{1}{2} \sin \alpha \right] - \left[\left(\frac{\sqrt{3}}{2}\right) \cos \alpha - \frac{1}{2} \sin \alpha \right] \\
 &= -\frac{3V_m}{2\pi} \left[-\frac{\sqrt{3}}{2} \cos \alpha - \frac{1}{2} \sin \alpha - \frac{\sqrt{3}}{2} \cos \alpha + \frac{1}{2} \sin \alpha \right] \\
 &= -\frac{3V_m}{2\pi} \left[-\frac{2\sqrt{3}}{2} \cos \alpha \right]
 \end{aligned}$$

$$V_o = \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha$$

In this case, the phase voltage
 V_a, V_b, V_c across the load

for line voltage

$$V_L = \sqrt{3} V_{ph}$$

$$\text{so, } V_o = \frac{3\sqrt{3}V_{mp}}{2\pi} \cos \alpha$$

$$\text{so, } V_o = \frac{3V_{ml} \cos \alpha}{2\pi}$$

$$\text{Average load current, } I_o = \frac{V_o}{R} = \frac{3V_{ml}}{2\pi R} \cos \alpha$$

Rms value of output, or load voltage is

$$V_{RMS} = \sqrt{\frac{\int_{30^\circ + \alpha}^{150^\circ + \alpha} V_m^2 \sin^2 \omega t \cdot d(\omega t)}{2\pi/3}}$$

$$= \sqrt{\frac{3V_m^2}{2\pi} \int_{30^\circ + \alpha}^{150^\circ + \alpha} \left(\frac{1 - \cos 2\omega t}{2} \right) d(\omega t)}$$

$$= \sqrt{\frac{3V_m^2}{4\pi} \int_{30^\circ + \alpha}^{150^\circ + \alpha} (1 - \cos 2\omega t) d(\omega t)}$$

$$= \sqrt{\frac{3V_m^2}{4\pi} \left\{ (\omega t) \Big|_{30^\circ + \alpha}^{150^\circ + \alpha} - \left(\frac{\sin 2\omega t}{2} \right) \Big|_{30^\circ + \alpha}^{150^\circ + \alpha} \right\}}$$

$$= \sqrt{\frac{3V_m^2}{4\pi} \left\{ \frac{2\pi}{3} - \frac{1}{2} [(\sin(300 + 2\alpha)) - \sin(60 + 2\alpha)] \right\}}$$

$$= \sqrt{\frac{3V_m^2}{4\pi} \left[\frac{2\pi}{3} - \frac{1}{2} \left\{ (\sin 300 \cdot \cos 2\alpha + \cos 300 \cdot \sin 2\alpha) - (\sin 60 \cdot \cos 2\alpha + \cos 60 \cdot \sin 2\alpha) \right\} \right]}$$

$$= \sqrt{\frac{3V_m^2}{4\pi} \left[\frac{2\pi}{3} - \frac{1}{2} \left\{ \left(\frac{\sqrt{3}}{2} \cos 2\alpha + \frac{1}{2} \sin 2\alpha \right) - \left(\frac{\sqrt{3}}{2} \cos 2\alpha - \frac{1}{2} \sin 2\alpha \right) \right\} \right]}$$

$$= \sqrt{\frac{3V_m^2}{4\pi} \left[\frac{2\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha \right]}$$

$$V_{RMS} = \sqrt{\frac{3V_m^2}{4\pi} \left[\frac{2\pi}{3} + \frac{\sqrt{3}}{2} \cos 2\alpha \right]}$$

Case ii: $\alpha > 30^\circ$

Avg. value of load voltage, $V_o = \frac{1}{120} \int_{30+\alpha}^{180} V_m \sin \omega t \cdot d(\omega t)$

$$= \frac{V_m}{2\pi/3} \int_{30+\alpha}^{180} \sin \omega t \cdot d(\omega t) = \frac{3V_m}{2\pi} [-\cos \omega t]_{30+\alpha}^{180}$$

$$= -\frac{3V_m}{2\pi} [\cos 180^\circ - \cos(30+\alpha)] = \frac{-3V_m}{2\pi} [-1 - \cos(30+\alpha)]$$

$$V_o = \frac{3V_m}{2\pi} [1 + \cos(30+\alpha)]$$

Rms value of o/p voltage, $V_{Rms} = \sqrt{\frac{1}{120} \int_{30+\alpha}^{180} V_m^2 \sin^2 \omega t \cdot d(\omega t)}$


$$= \sqrt{\frac{3V_m^2}{2\pi} \int_{30+\alpha}^{180} \left(\frac{1 - \cos 2\omega t}{2} \right) d(\omega t)} = \sqrt{\frac{3V_m^2}{4\pi} \left[(\omega t) \Big|_{30+\alpha}^{180} - \left(\frac{\sin(2\omega t)}{2} \right) \Big|_{30+\alpha}^{180} \right]}$$

$$= \sqrt{\frac{3V_m^2}{4\pi} \left[(180 - 30 - \alpha) - \frac{1}{2} (\sin(2 \times 180) - \sin 2(30 + \alpha)) \right]}$$


$$= \sqrt{\frac{3V_m^2}{4\pi} \left[(150 - \alpha) - \frac{1}{2} (\sin(360^\circ) - \sin(60 + 2\alpha)) \right]}$$

$$= \sqrt{\frac{3V_m^2}{4\pi} \left[(150 - \alpha) + \frac{1}{2} \sin(60 + 2\alpha) \right]}$$

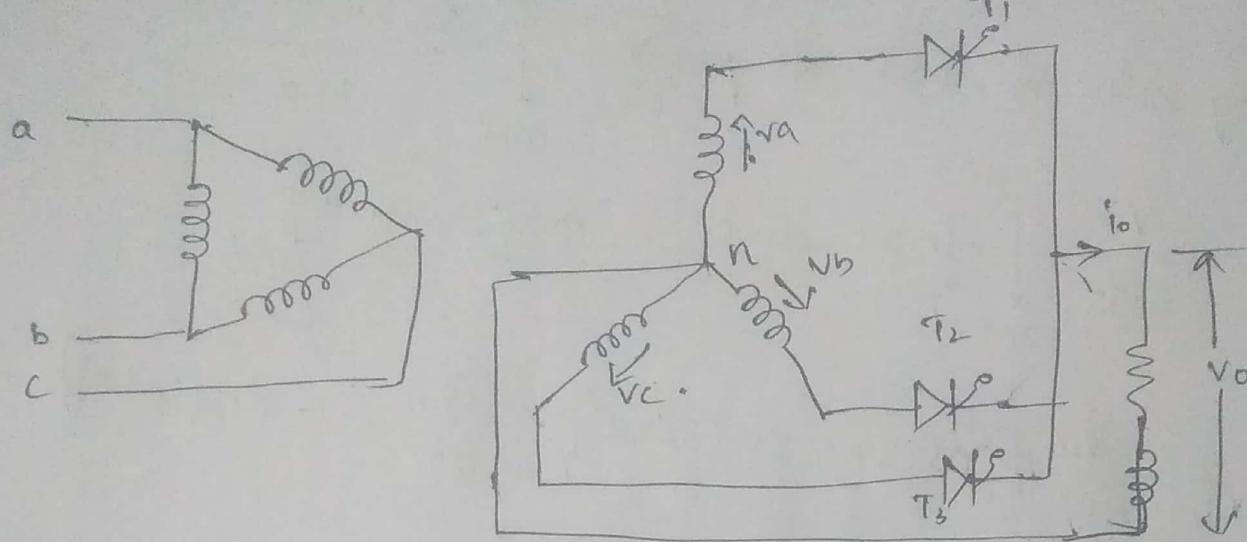3-Φ half wave controlled Rectifiers R-L load



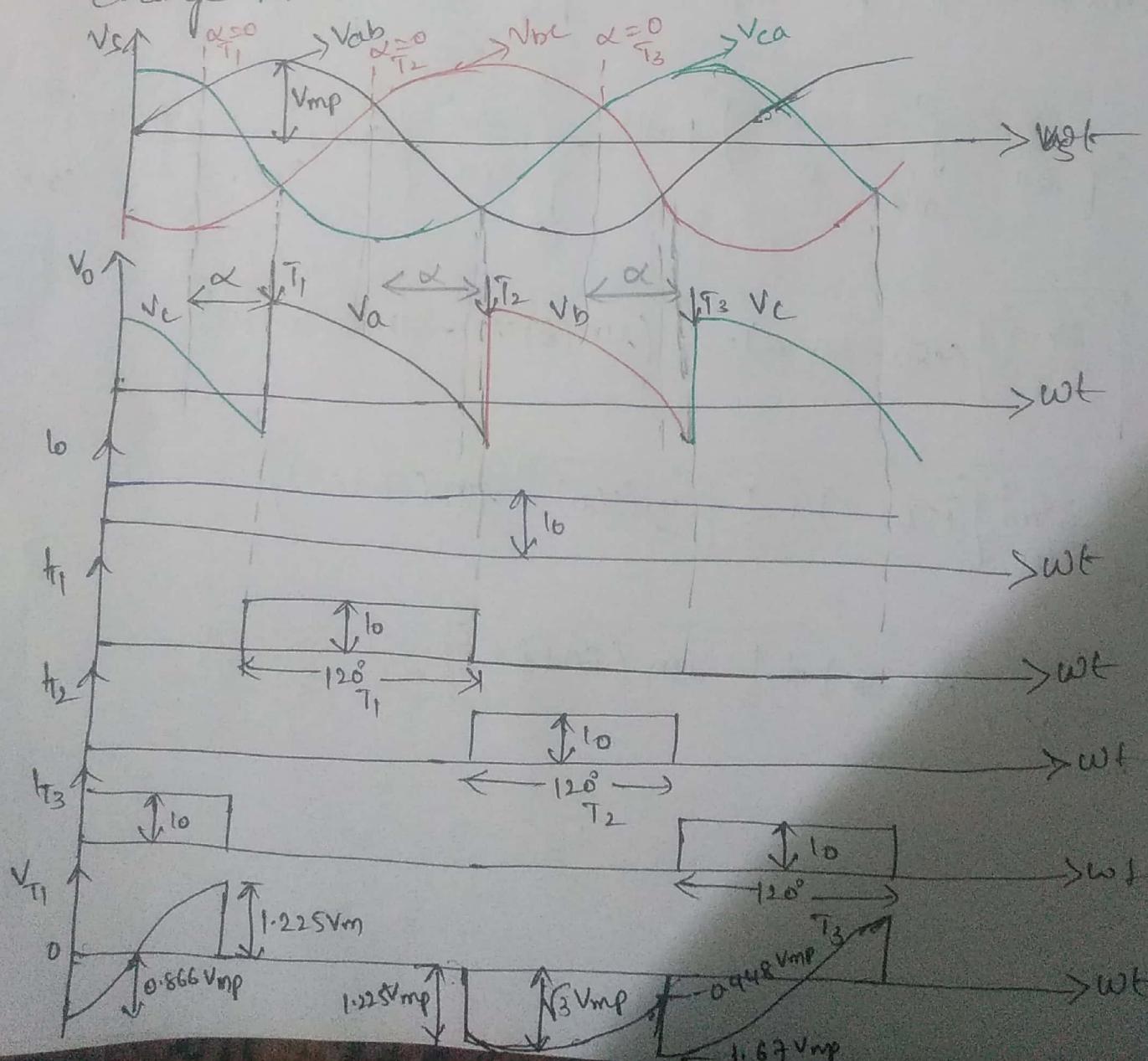→ Here we are taking inductance is very high it will not change in the current



- The load inductance L is large so, that load current is continuous and constant at I_0 .
- for firing angle range of $30^\circ < \alpha < 90^\circ$ &
 $90^\circ < \alpha < 180^\circ$.

Case I: $30^\circ < \alpha < 90^\circ$

let the firing angle be, say 45° .

Note that T_1 conducts from $30^\circ + \alpha$ to $150^\circ + \alpha$

$$\begin{array}{ccc} T_2 & \longrightarrow & 150^\circ + \alpha \text{ to } 270^\circ + \alpha \\ T_3 & \longrightarrow & 270^\circ + \alpha \text{ to } 390^\circ + \alpha \text{ & so on} \end{array}$$

At $wt = \pi$, phase voltage V_o is zero,

but i_{T_1} is not zero because of RL load.

$\therefore T_1$ would continue conducting beyond $wt = \pi$,

As $V_o = V_a$ goes negative beyond $wt = \pi$,

→ when T_2 is turned on at $wt = 150^\circ + \alpha$, load current shifts from T_1 to T_2 & a voltage

$$V_a - V_b = [V_m \sin(150^\circ + \alpha) - V_m \sin(30^\circ + \alpha)]$$

→ SCR T_2 conducts from $(150^\circ + \alpha)$ to $(270^\circ + \alpha)$ & so on.

→ The wave-form V_{T_1} for voltage across T_1 . on the fixing angle 45° , can be

when T_1 is on, $V_{T_1} = V_a - V_a = 0$ from $wt = 75^\circ$ to 195°

T_2 is on, $V_{T_1} = V_a - V_b$ from $wt = 195^\circ$ to 315°

T_3 is on $V_{T_1} = V_a - V_c$ from $wt = 315^\circ$ to 435° & so on

→ when T_2 is turned on at $\omega t = 195^\circ$,

$$V_{T_1} = V_a - V_b = -V_{mp} \sin 15^\circ - V_{mp} \sin 75^\circ \\ = -1.225 V_{mp}$$

$$\text{At } \omega t = 210^\circ, V_{T_1} = -1.5 V_{mp}$$

$$\omega t = 243^\circ \quad V_{T_1} = \sqrt{3} V_{mp}$$

$$\omega t = 270^\circ \quad V_{T_1} = -1.5 V_{mp}$$

$$\omega t = 300^\circ \quad V_{T_1} = -V_{mp} \sin 60^\circ - 0 = -0.866 V_{mp}$$

$$\omega t = 315^\circ \quad V_{T_1} = -V_{mp} \sin 45^\circ + V_{mp} \sin 15^\circ$$

$$= -0.448 V_{mp}$$

Also At $\omega t = 315^\circ, T_2$ gets turns off, whereas
 T_3 is turned on

$$V_{T_1} = V_a - V_c = -V_{mp} \sin 45^\circ + V_{mp} \sin 75^\circ \\ = -1.673 V_{mp}$$

→ At $\omega t = 315^\circ, V_{T_1}$ at once changes from $-0.448 V_{mp}$ to
 $-1.673 V_{mp}$

$$\text{At } \omega t = 330^\circ, V_{T_1} = -V_{mp} \sin 30^\circ - V_{mp} = -1.5 V_{mp}$$

$$\omega t = 360^\circ, V_{T_1} = 0 - 0.866 V_{mp} = -0.866 V_{mp}$$

$$\omega t = 390^\circ, V_{T_1} = 0.5 V_{mp} - 0.5 V_{mp} = 0$$





$$\omega t = 420^\circ, V_{T_1} = 0.866 V_{mp} - 0 = 0.866 V_{mp}$$

$$\omega t = 435^\circ, V_{T_1} = V_{mp} \sin 75^\circ + V_{mp} \sin 15^\circ = 1.225 V_{mp}$$

If also $V_{T_1} = V_a - V_a = 0$ & so on.

Avg load op voltage, $V_o = \frac{3\sqrt{3}V_{mp}}{2\pi} \cos(\alpha) \frac{3V_{mp} \cos \alpha}{2\pi}$
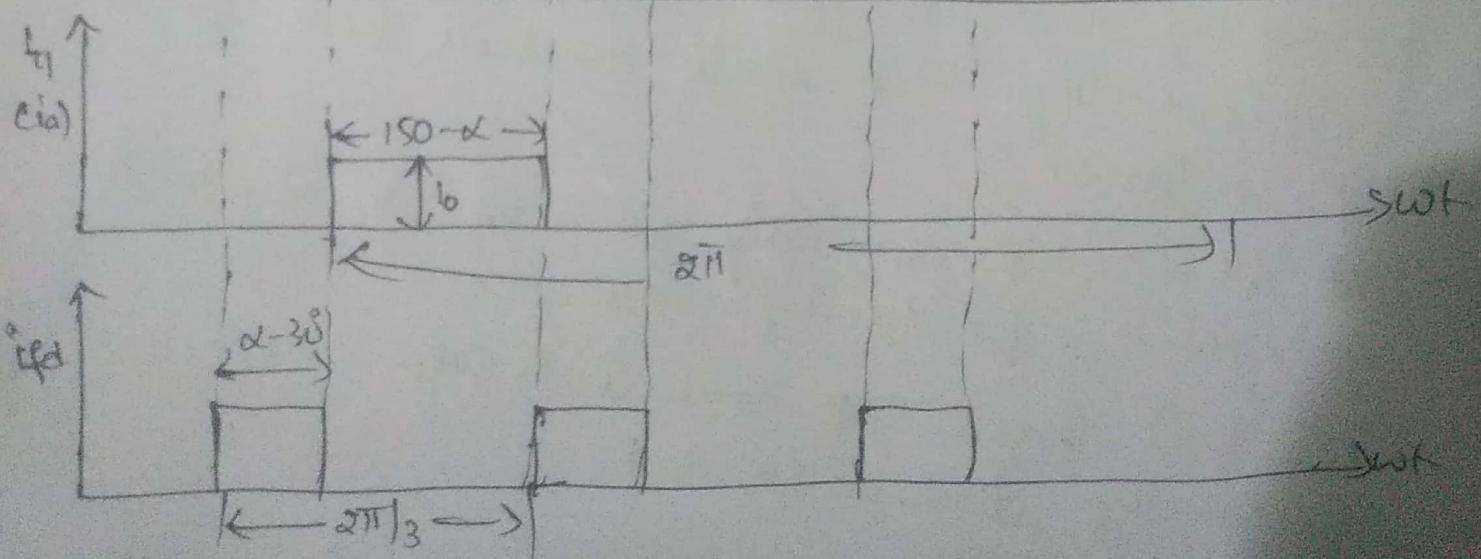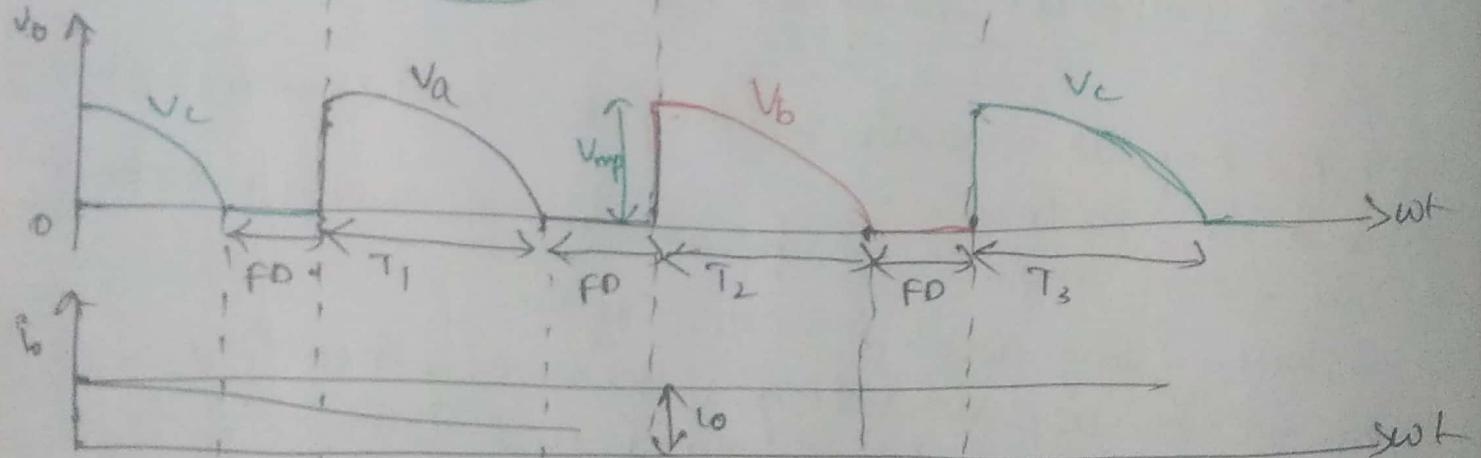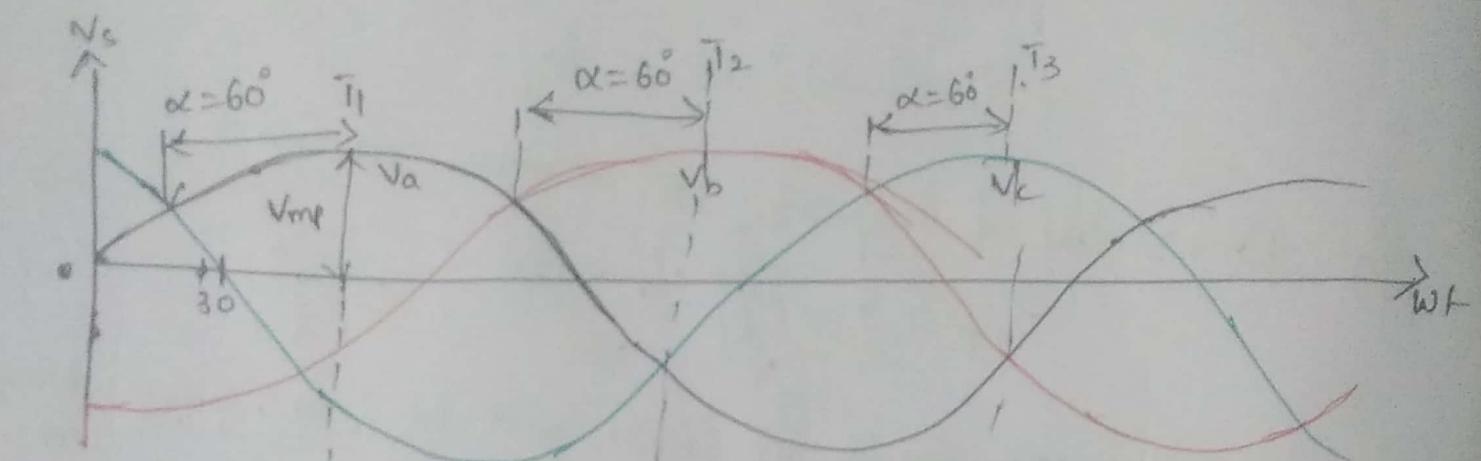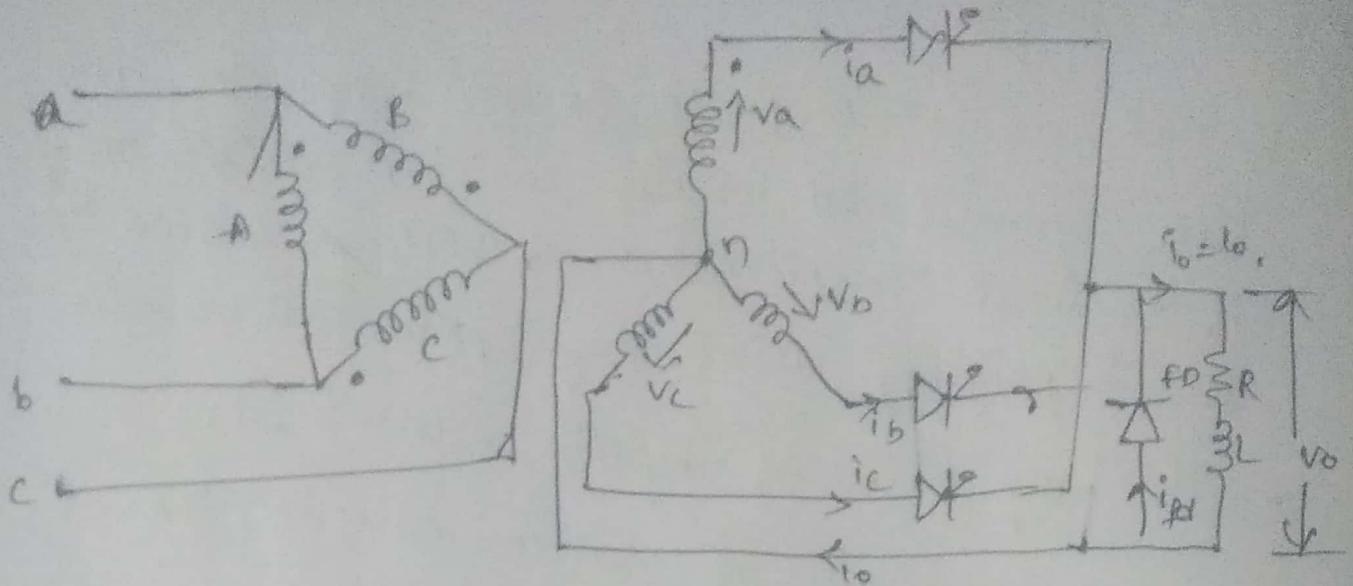
$$V_{rms} = \sqrt{\frac{3V_{mp}^2}{4\pi} \left[\frac{2\pi}{3} + \frac{\sqrt{3}}{2} \cos \alpha \right]}$$



Case II $\alpha > 90^\circ$

$V_0 = -ve \rightarrow \therefore 3\text{-}\phi 3\text{pulse converter operates as a line commutated inverter which is possible only if the load circuit has a dc voltage source of reverse polarity, as in a single-phase full converter}$

\rightarrow The avg value of thyristor current, $I_{TA} =$

avg value of source current, I_{SA}

$$= (I_0 \times 120) / 360 = I_0 / 3$$

\rightarrow Rms value of thyristor (or) source current

$$I_{TR} = I_{SR} = \sqrt{\left[\frac{\frac{1}{3} I_0^2 \times 120}{360} \right]} = \frac{I_0}{\sqrt{3}}$$

\Rightarrow 3\text{-}\phi fullwave bridge rectifier with RL load & free wheeling diode:

\rightarrow A 3\phi 3pulse converter feeding RL load & with freewheeling diode across RL load.

\rightarrow for firing angle $\alpha < 30^\circ$, freewheeling diode does not come into play.

\rightarrow so, here firing angle is taken, say 60° .

\rightarrow At $wt = \pi/2$, as phase voltage V_0 tends to go negative, freewheeling diode gets forward biased through T_1 .

\rightarrow \therefore freewheeling diode starts conducting from $wt = \pi/2$ till T_2 is turned on.

\rightarrow At $wt = 150^\circ + \alpha$. Similarly, when V_R & V_C tends to go negative, freewheeling diode comes into play.

\rightarrow Note that each SCR conducts for $(150^\circ - \alpha)$ & freewheeling diode for $(\alpha - 30^\circ)$

Avg. value of op voltage,

$$V_0 = \frac{3}{2\pi} \int_{\alpha + \pi/6}^{\pi} V_{mp} \sin(\omega t) dt$$

$$V_0 = \frac{3V_{mp}}{2\pi} [1 + \cos(\alpha + \pi/6)]$$

$$V_{rms} = \sqrt{\frac{V_{mp}}{2\pi} \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin(2\alpha + \pi/3) \right]}$$

Avg. thyristor current, $I_{TA} = \frac{I_0 \left(\frac{5\pi}{6} - \alpha \right)}{2\pi} = \frac{I_0}{2\pi} \left[\frac{5\pi}{6} - \alpha \right]$

RMS thyristor current, $I_{TR} = \sqrt{\left(\frac{I_0^2}{2\pi} \left\{ \frac{5\pi}{6} - \alpha \right\} \right)}$





$$= I_0 \sqrt{\left(\frac{1}{2\pi} \left\{ \frac{5\pi}{6} - \alpha \right\} \right)}$$

Avg value of FD current, $I_{fD,A} = \frac{I_0 (\alpha - 30^\circ)}{2\pi/3} = \frac{3I_0(\alpha - 30^\circ)}{2\pi}$

RMS value of FD current, $I_{fD,rms} = \sqrt{\left(\frac{I_0^2 (\alpha - 30^\circ)}{2\pi/3} \right)}$

$$= I_0 \sqrt{\frac{3}{2\pi} (\alpha - 30^\circ)}$$

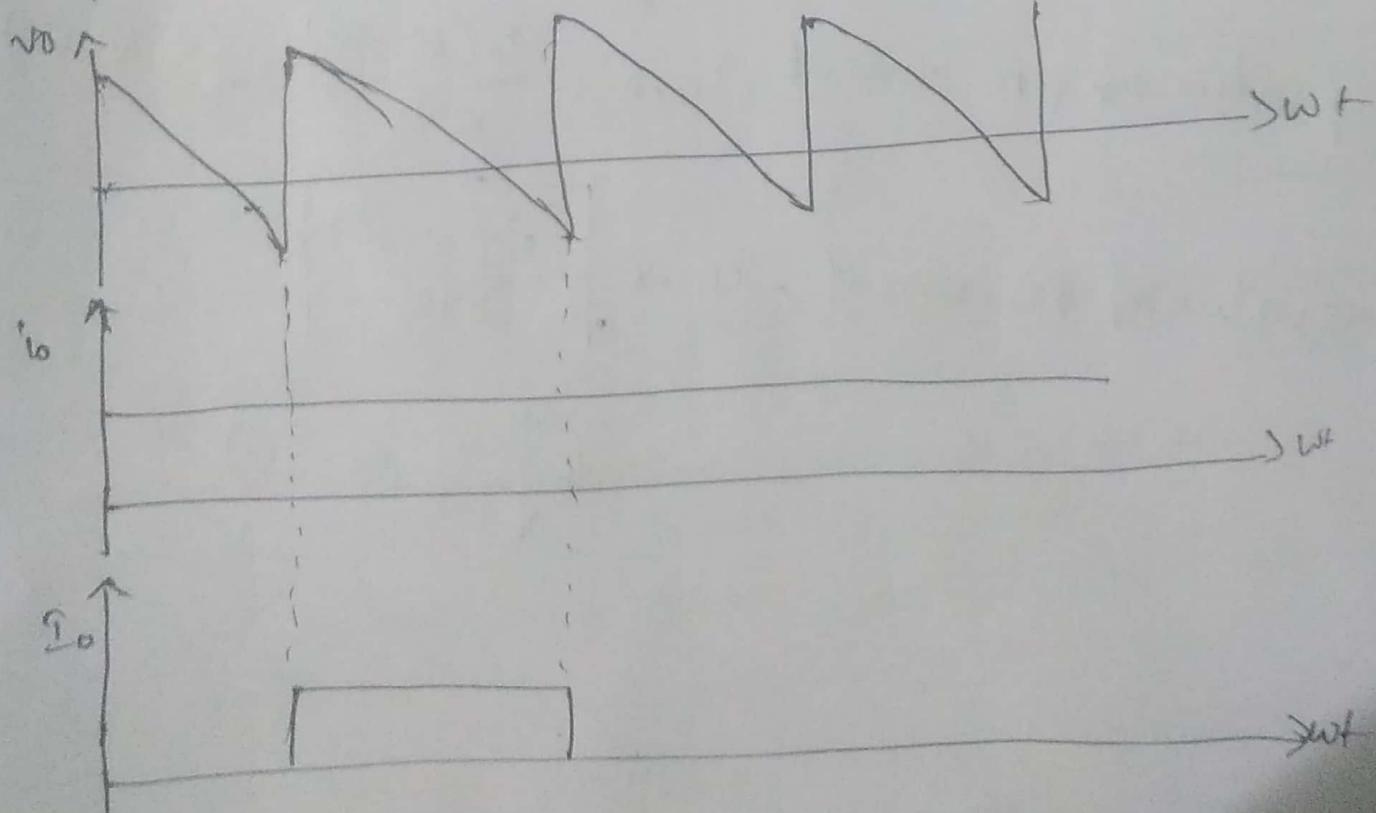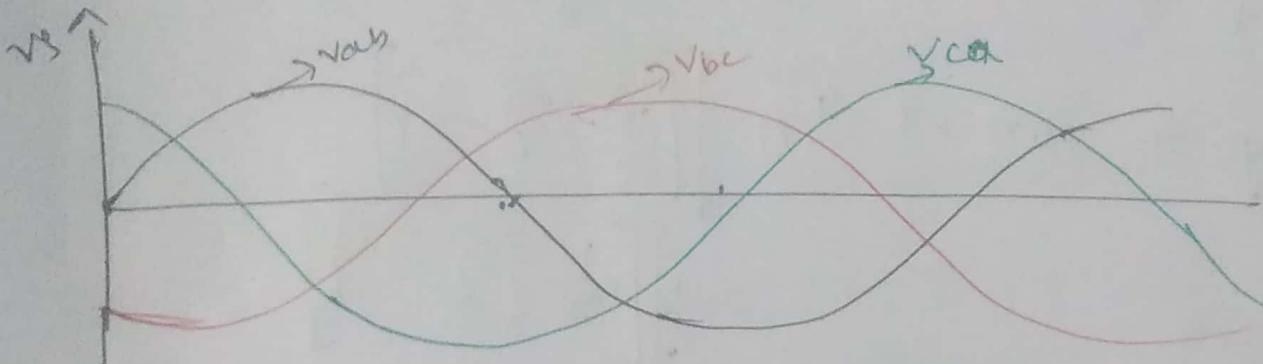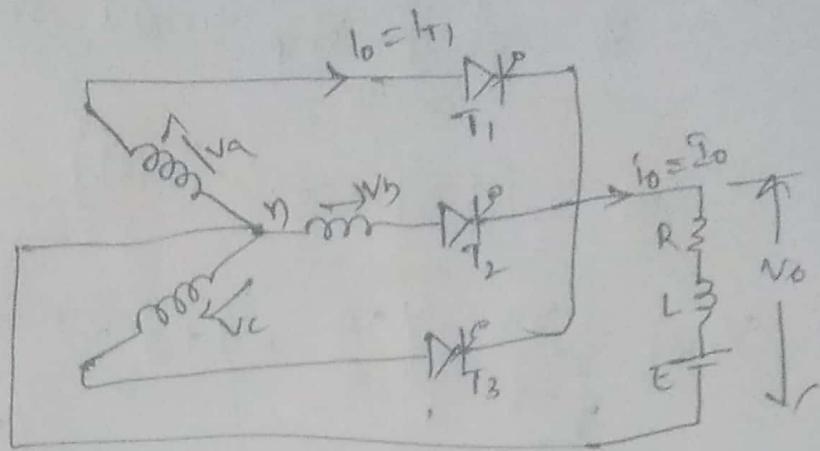
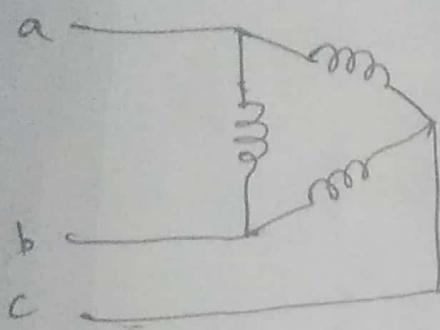
\Rightarrow 3- ϕ half wave rectifier with RLE loads :-



$$\begin{aligned}
 \text{Avg. o/p voltage} &= V_{avg} = \frac{3V_m}{2\pi} \int_{\pi/6+\alpha}^{150+\alpha} \sin \omega t \cdot d(\omega t) \\
 &= \frac{3V_m}{2\pi} \left[-\cos(\omega t) \right]_{30+\alpha}^{150+\alpha} \\
 &= \frac{3V_m}{2\pi} \left[-\cos(150+\alpha) + \cos(30+\alpha) \right] \\
 &= \frac{3V_m}{2\pi} \left[(\cos(150)\cos\alpha + \sin(150)\sin\alpha) \right. \\
 &\quad \left. + (\cos 30 \cos\alpha - \sin 30 \sin\alpha) \right] \\
 &= \frac{3V_m}{2\pi} [2\cos(30') \cos\alpha] \\
 &= \frac{3V_m}{2\pi} [2 \times \sqrt{3}/2 \cos\alpha] \\
 &= \frac{3\sqrt{3}V_m}{2\pi} \cos\alpha
 \end{aligned}$$

$$\begin{aligned}
 \text{Rms voltage} &= \sqrt{\int_{\pi/6+\alpha}^{150+\alpha} \frac{V_m^2 \sin^2 \omega t \cdot d(\omega t)}{2\pi/3}} \\
 &= \sqrt{3}V_m \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha} \\
 &= \sqrt{8}V_m \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha}
 \end{aligned}$$

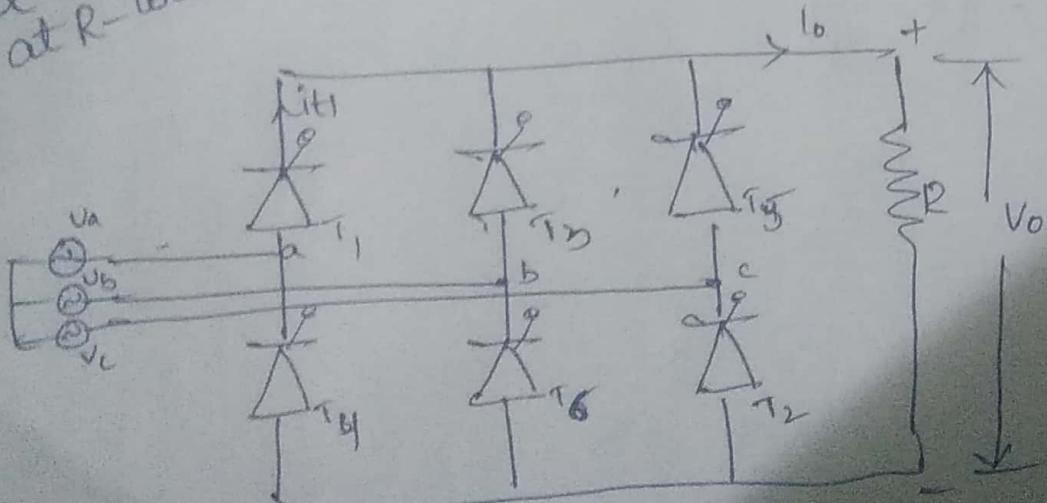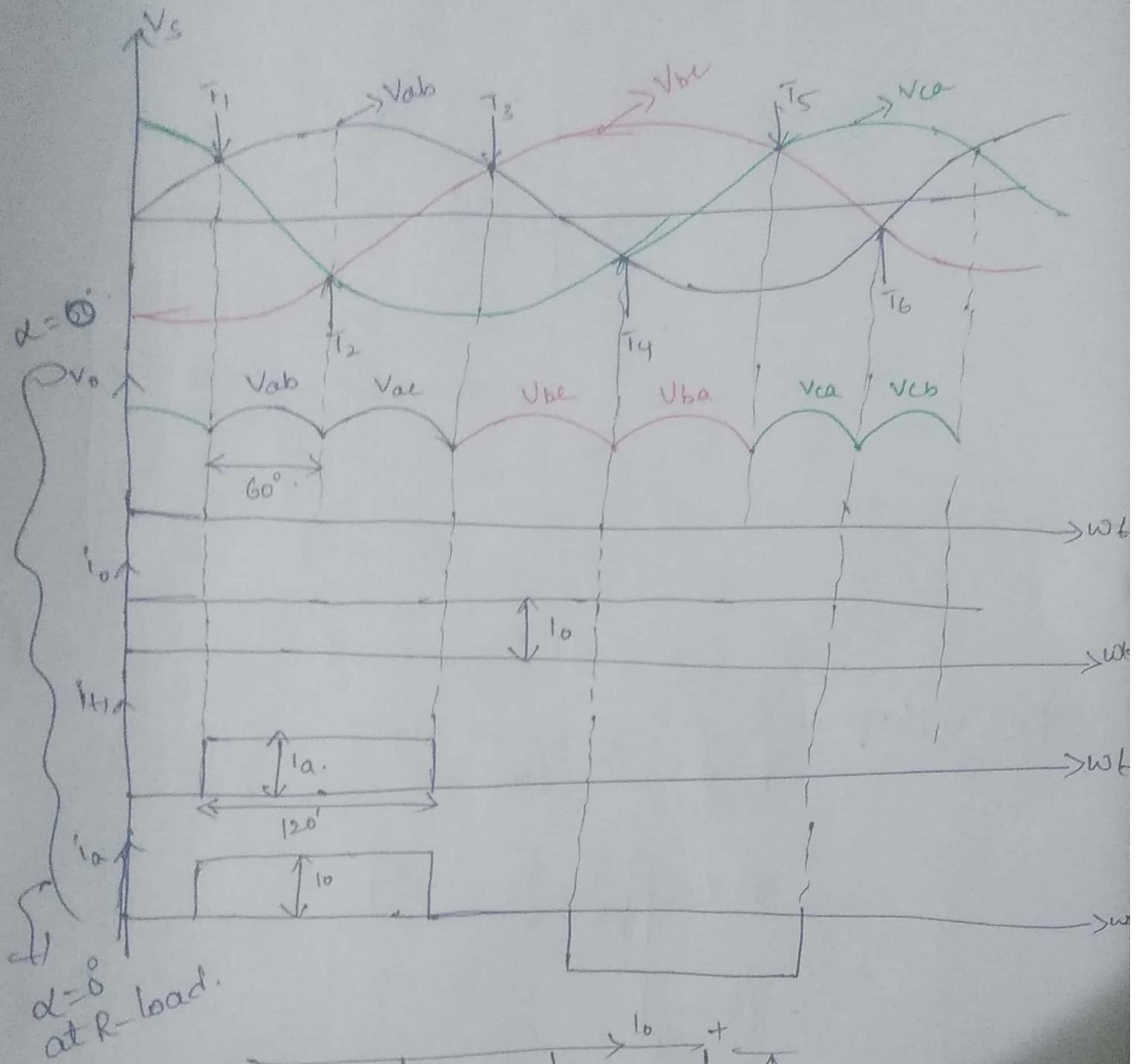3-Φ full wave controlled Rectifier with R-load



→ T_1 is triggered at $wt = (30 + \alpha)$, T_6 is already conducting when T_1 is turned ON.

→ During the interval $(30 + \alpha)$ to $(90 + \alpha)$, T_1 & T_6 conduct together & the o/p load voltage is equal to

$$V_o = V_{ab} = (V_{an} - V_{bn})$$

→ T_2 is triggered at $wt = (90 + \alpha)$, T_6 turns off naturally as it is reverse biased as soon as T_2 triggered

→ During the interval $(90 + \alpha)$ to $(150 + \alpha)$, T_1 & T_2 conduct together & the o/p load voltage

$$V_o = V_{ae} = (V_{an} - V_{ce})$$

→ T_3 is triggered at $wt = (150 + \alpha)$, T_1 turns off naturally as it is reverse biased as soon as T_3 is triggered

→ During the interval $(150 + \alpha)$ to $(210 + \alpha)$, T_2 & T_3 conduct together & the o/p load voltage

$$V_o = V_{be} = (V_{bn} - V_{ce})$$

→ T_4 is triggered at $wt = (210 + \alpha)$, T_2 turns off naturally as it is reverse biased as soon as T_4 is triggered


→ During the interval $(210 + \alpha)$ to $(270 + \alpha)$, T_3 & T_4 conduct together & the o/p load voltage





$$V_o = V_{ba} = (V_{bn} - V_{an})$$

→ T_5 is triggered at $wt = (270 + \alpha)$, T_3 turns off naturally as it is reverse biased as soon as T_5 is triggered

→ During the interval $(270 + \alpha)$ to $(230 + \alpha)$, T_4 & T_5 conduct together & the o/p load voltage

$$V_o = V_{ca} = (V_{an} - V_{an})$$

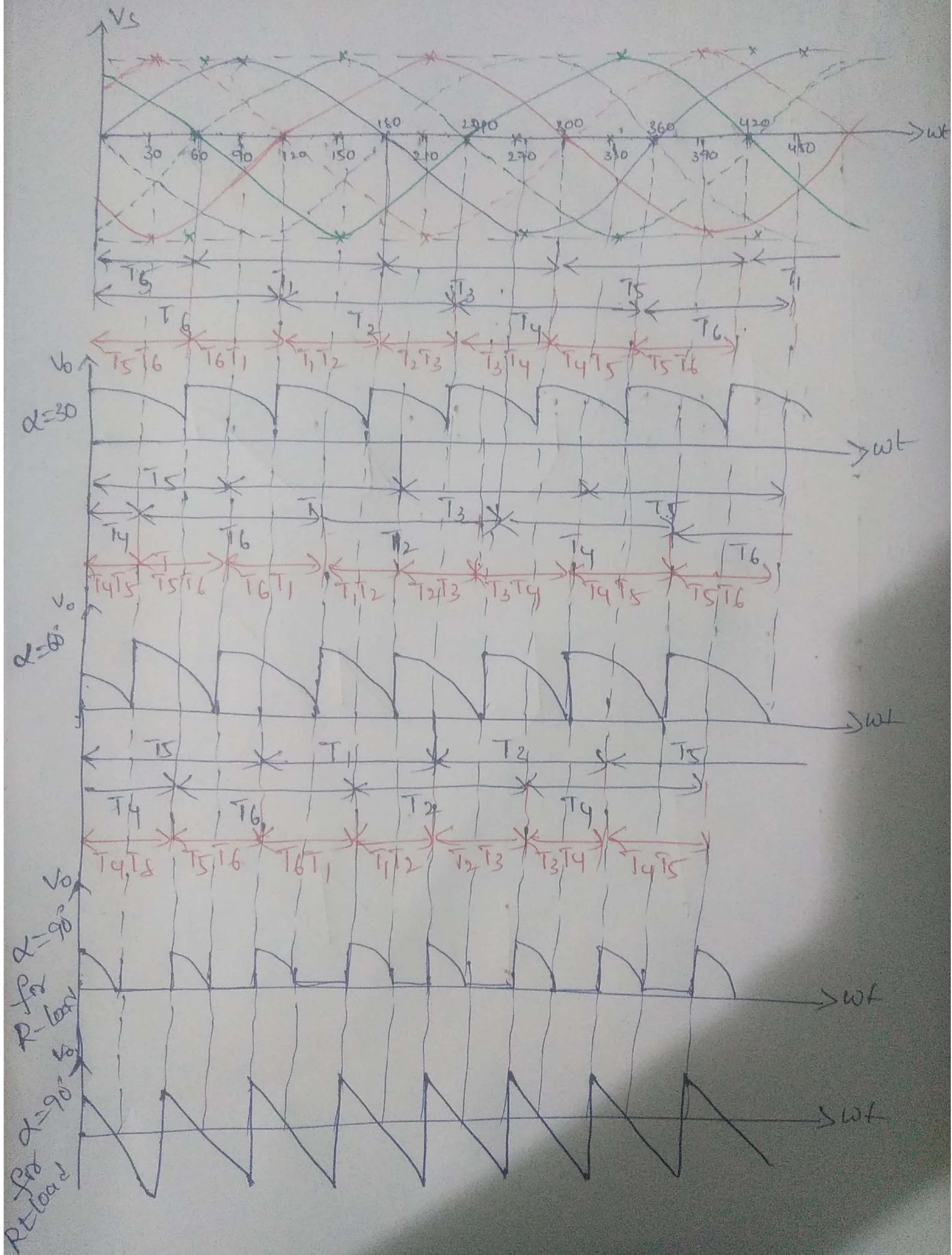

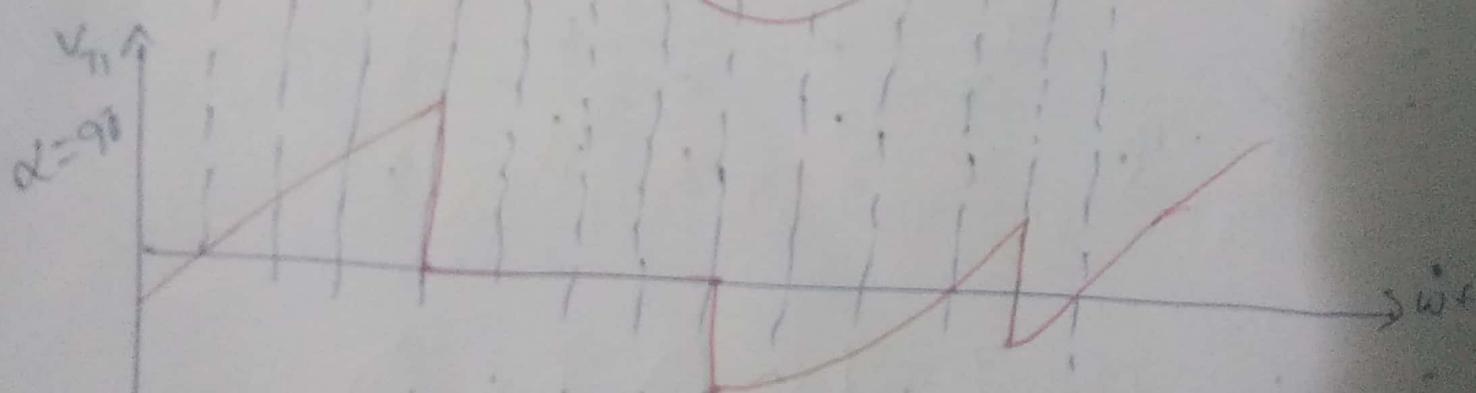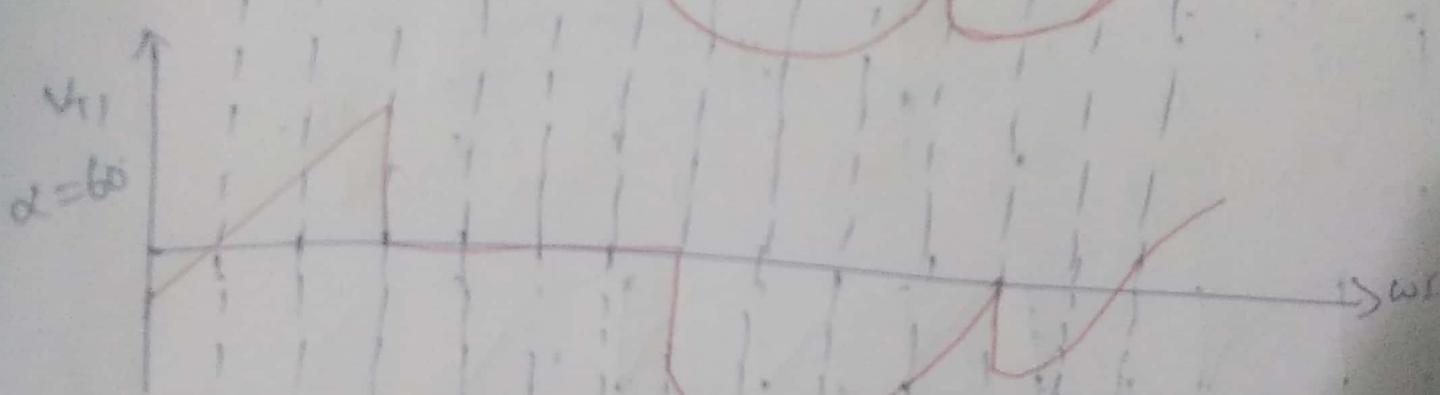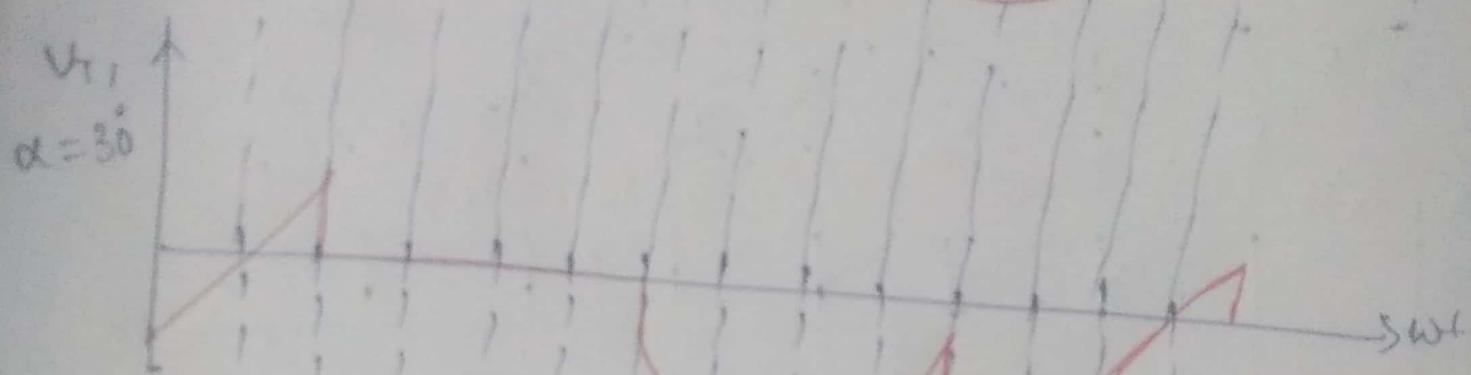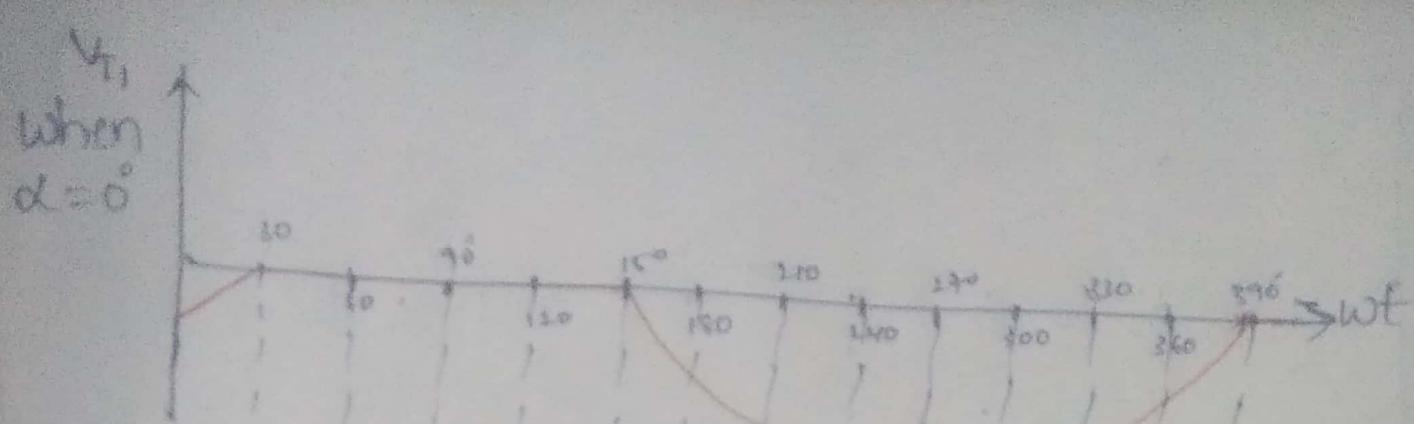

Let

$$V_{an} = V_m \sin \omega t$$

$$V_{bn} = V_m \sin(\omega t - 2\pi/3)$$

$$V_{cn} = V_m \sin(\omega t - 4\pi/3)$$

$$V_{ab} = \sqrt{3} V_m \sin(\omega t + \pi/6)$$

$$V_{bc} = \sqrt{3} V_m \sin(\omega t - \pi/2)$$

$$V_{ca} = \sqrt{3} V_m \sin(\omega t - 2\pi/3)$$

The dc component of the o/p voltage & current can be found as

$$\begin{aligned} V_{dc} &= \frac{3}{\pi} \int_{\pi/6 + \alpha}^{\pi/2 + \alpha} \sqrt{3} V_m \sin(\omega t + \pi/6) d(\omega t) \\ &= \frac{3\sqrt{3} V_m}{\pi} \cos \alpha \end{aligned}$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{3\sqrt{3} V_m}{\pi R} \cos \alpha$$

$$V_{Rms} = \sqrt{\frac{3}{\pi} \int_{\pi/6 + \alpha}^{\pi/2 + \alpha} (\sqrt{3} V_m \sin(\omega t + \pi/6))^2 d(\omega t)}$$

$$V_{Rms} = \sqrt{3} V_m \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha}$$

$$I_{Rms} = \frac{V_{Rms}}{\sqrt{R^2 + (\omega L)^2}} = \frac{\sqrt{3} V_m}{\sqrt{(R^2 + (\omega L)^2)}} \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha}$$

when $\alpha \geq 60^\circ$

$$V_o = \frac{3}{\pi} \int_{\pi/6+\alpha}^{\pi} \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}) d(\omega t)$$

$$= \frac{3\sqrt{3} V_m}{\pi} \cos\left(\frac{\pi}{3} + \alpha\right)$$

$$I_o = \frac{V_o}{R} = \frac{3\sqrt{3} V_m}{\pi R} \cos\left(\frac{\pi}{3} + \alpha\right)$$

$$V_{rms} = \sqrt{\frac{3}{\pi} \int_{\pi/6+\alpha}^{\pi} (\sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}))^2 d(\omega t)}$$

$$I_{rms} = \frac{V_{rms}}{\sqrt{R^2 + (wL)^2}}$$