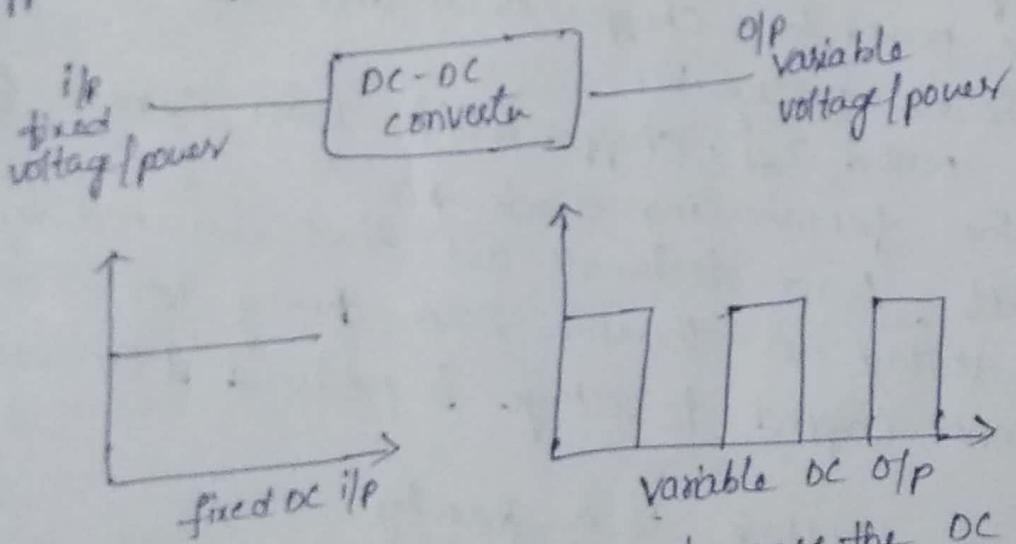


UNIT - III

DC-DC converter is very much needed nowadays as many industrial applications are dependent upon DC voltage source. The performance of these applications will be improved if we use a variable DC supply. It will help to control improve controllability of the equipments also.


Eg: are subway cars, trolley buses, battery operated vehicles etc. we can control & vary a constant DC voltage with the help of a chopper.

- Chopper is a basically static power electronic device which convert fixed DC voltage/power to variable DC voltage or power
- it is nothing but a high speed switch which connects & disconnects the load from it at a high rate to get variable or chopped voltage at the o/p



Principle of chopper operation:-

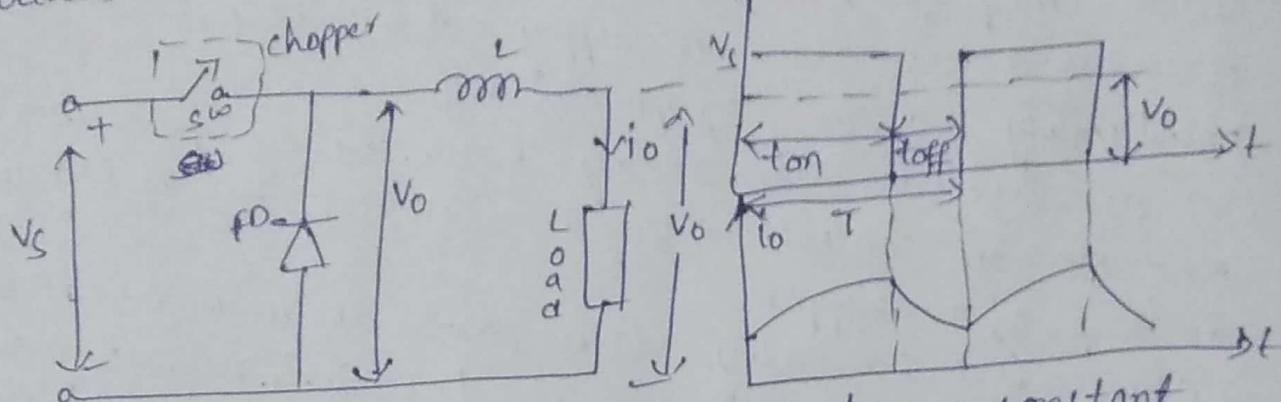- A chopper is a high speed on/off semiconductor switch.
- It connects source to load & disconnects the load from source at a fast speed.



- A chopped load voltage is obtained from a constant dc supply of magnitude \$V_s\$.
- Chopper is represented by a switch \$S_0\$ inside a dotted rectangle, which may be turned on or turned-off as desired.
- During the period \$T_{on}\$, chopper is on and load voltage is equal to source voltage \$V_s\$.
- During the period \$T_{off}\$, chopper is off, load current flows through the free-wheeling diode \$f_D\$.
- As a result, load terminals are short circuited by \$f_D\$ and load voltage is therefore zero during \$T_{off}\$.
- In this manner chopped dc voltage is produced at the load terminals.

The avg load voltage \$V_o\$ is given by

$$V_o = \frac{T_{on}}{T_{on} + T_{off}} V_s = \frac{T_{on}}{T} V = \alpha V_s$$

where \$T_{on}\$ = on-time, \$T_{off}\$ = off-time

$$T = T_{on} + T_{off}$$

$$\alpha = \frac{T_{on}}{T} = \text{duty cycle}$$

- Thus load voltage can be controlled by varying duty cycle.
- Load voltage is independent of load current. It can be written as \$V_o = f \cdot T_{on} \cdot V_s\$.

where $f = \frac{1}{T} = \text{chopping frequency}$.

Control strategies:-

The average value of o/p voltage V_o can be controlled through a 'd' by opening & closing the semiconductor switch periodically. The various control strategies for varying duty cycle 'd' are as follows

1. Time ratio control (TRC) and
2. current limit control

Time ratio control (TRC):-

In this scheme, time ratio T_{on}/T (or duty cycle) is varied. This is realized in two different strategies called constant frequency s/m and variable frequency s/m

1. Constant frequency s/m :

Here, the on-time T_{on} is varied but chopping frequency f (or chopping period T) is kept constant. Variation of T_{on} means adjustment of pulse width, as such this scheme is also called pulse width modulation.

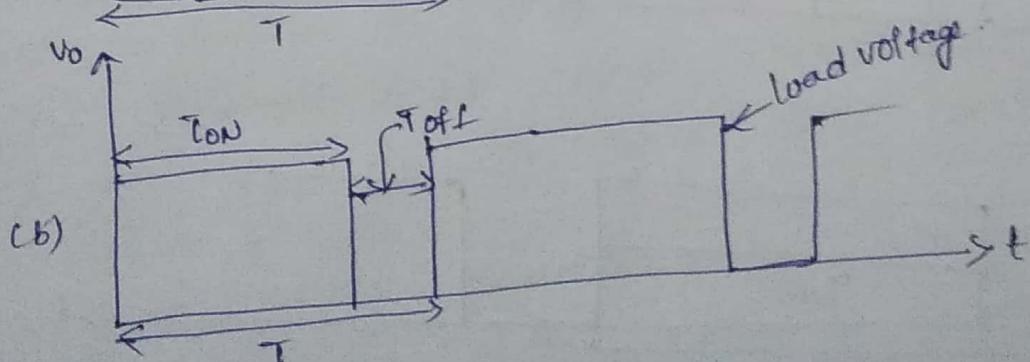
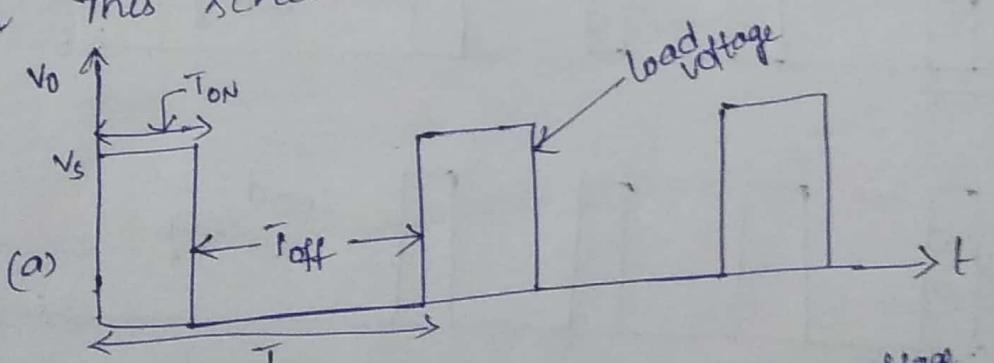


fig: principle of PWM

→ Here chopping period T is constant.

In (a) $T_{on} = \frac{1}{4}T$ so that $\alpha = 0.25$ (or) 25% .

(b) $T_{on} = \frac{3}{4}T$ so that $\alpha = 0.75$ (or) 75% .

ideally α can be varied from zero to unity.

∴ o/p voltage V_o can be varied b/w zero & source voltage V_s .

2. Variable frequency s/m :-

Here, the chopping frequency f (or chopping period T) is varied and either i) on-time T_{on} is kept constant

ii) off-time T_{off} is kept constant

This method of controlling α is also called frequency modulation scheme.

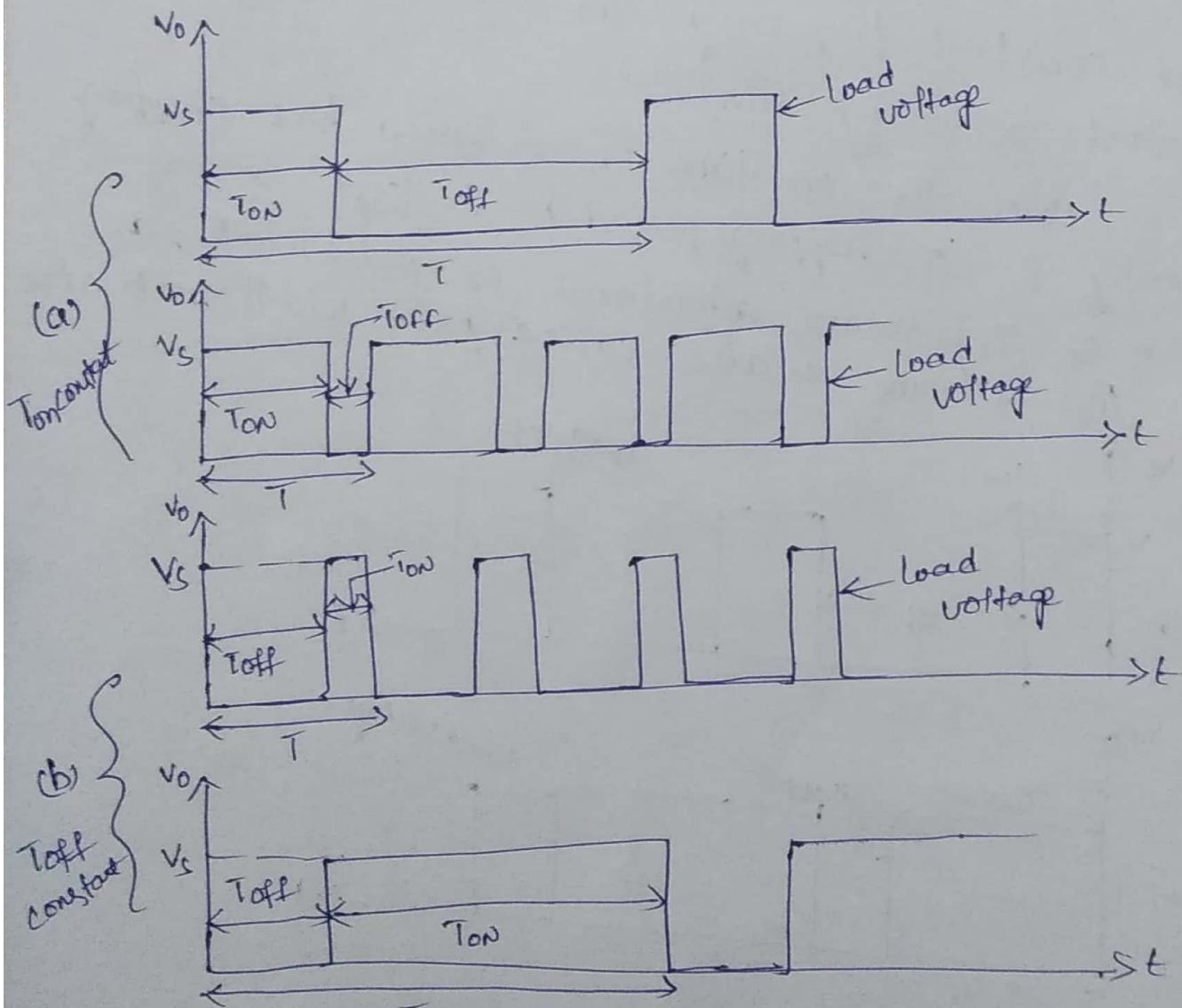


fig: principle of frequency modulation

→ Here, T_{on} is kept constant but T is varied.

fig (a) $T_{on} = \frac{1}{4}T$ so that $\alpha = 0.25$.

fig (b) $T_{on} = \frac{3}{4}T$ so that $\alpha = 0.75$

fig (b) T_{off} is kept constant and T is varied

In fig (b) upper, $T_{on} = \frac{1}{4}T$ so that $\alpha = 0.25$

lower, $T_{on} = \frac{3}{4}T$ so that $\alpha = 0.75$

→ frequency modulation scheme has some disadvantages as compared to PWM scheme

- i) The chopping frequency has to be varied over a wide range for the control of DC voltage in frequency modulation filter design. For such wide frequency variation is quite difficult.
- ii) For the control of α , frequency variation would be wide. As such, there is a possibility of interference with signalling & telephone lines in frequency modulation scheme.
- iii) The large off-time in frequency modulation scheme may make the load current discontinuous which is undesirable.

→ Constant frequency scheme is better than the variable frequency scheme.

→ PWM technique has T_{on} cannot be reduced to near zero for most of the communication choppers used in choppers. As such, low range of α control is not possible in PWM.

→ This can however, be achieved by increasing the chopping period of the frequency choppers.

\Rightarrow current limit control:

- In this scheme, the on & off chopper ckt is guided by the previous set value of load current. These two set values are max. load current $I_{o,max}$ and min. load current $I_{o,min}$.
- When load current reaches the upper limit $I_{o,max}$, chopper is switched off. Now load current freewheels & begins to decay exponentially.
- When it falls to lower limit $I_{o,min}$, chopper is switched on & load current begins to rise. Profile of load current shows that it fluctuates b/w $I_{o,max}$ & $I_{o,min}$ & therefore cannot be discontinuous.

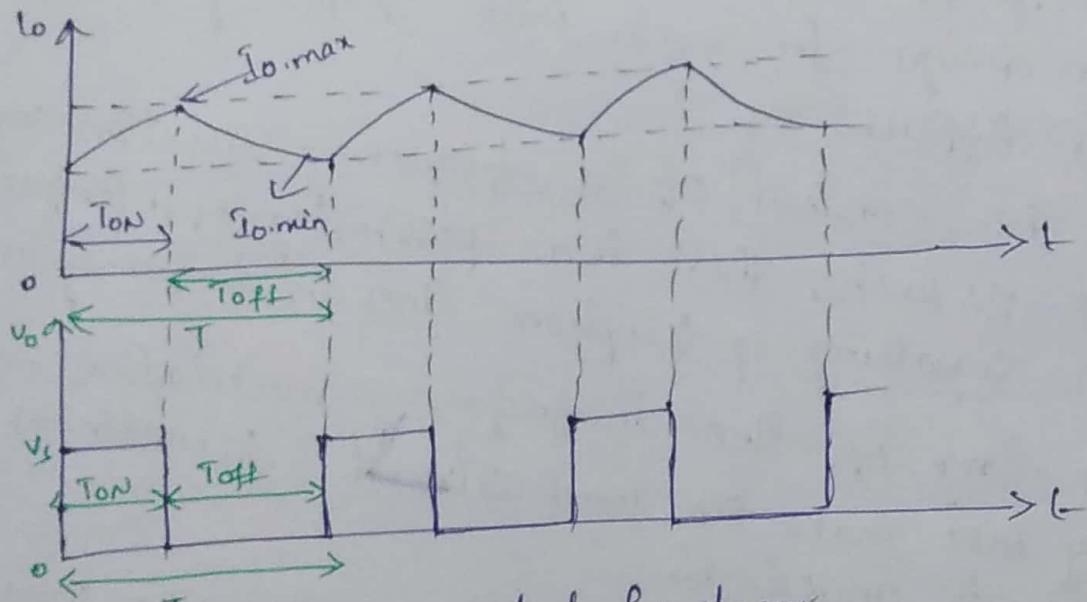



fig: current limit control for chopper

- Switching frequency of chopper can be controlled by switching setting $I_{o,max}$ & $I_{o,min}$. Ripple current = $(I_{o,max} - I_{o,min})$ can be lowered & this in turn necessitates higher switching frequency. E.g.: more switching losses
- Current limit control involves feedback loop, the trigger circuitry for the chopper is therefore more complex.
- PWM technique is more commonly used control strategy for the power control in chopper ckt.

DC-DC BUCK converter (or)



Step down converter

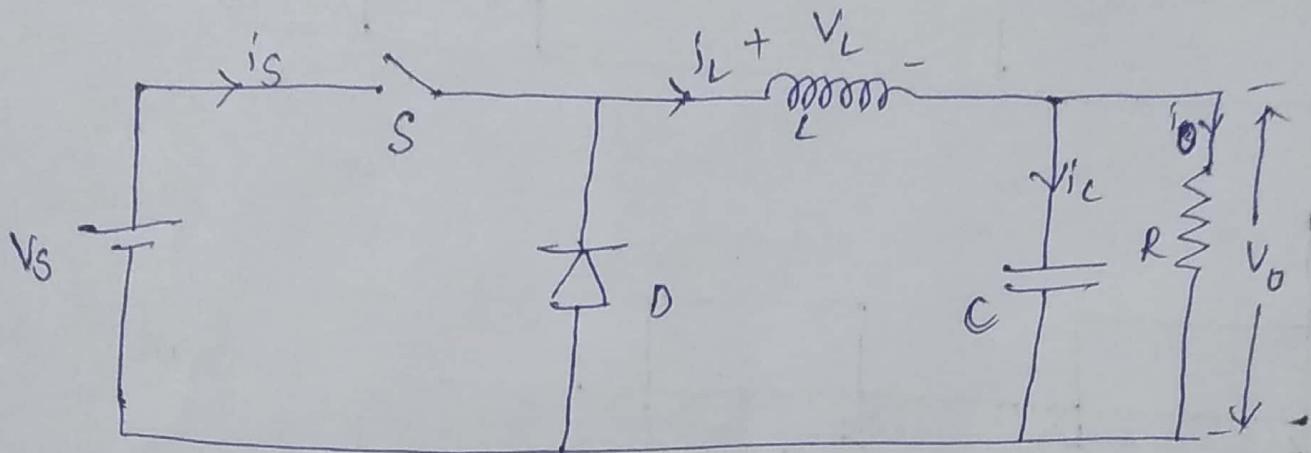- A buck converter is a dc-dc converter.
also avg o/p voltage is less than the i/p voltage
 $[V_o < V_s]$



- The ckt diagram consists of voltage source V_s , switch, inductor, capacitor & Resistor
- The 'i' in the o/p ckt is assumed to be large enough so that the time constant of RC circuit is very high & it ensures a o/p voltage.
- Buck converter operating two modes
 - continuous conduction mode
 - discontinuous conduction mode
- continuous conduction mode
 - The current through the inductor "L" never goes to zero
 - discontinuous conduction mode
 - The current through the inductor "L" goes to zero

Continuous conduction mode :-

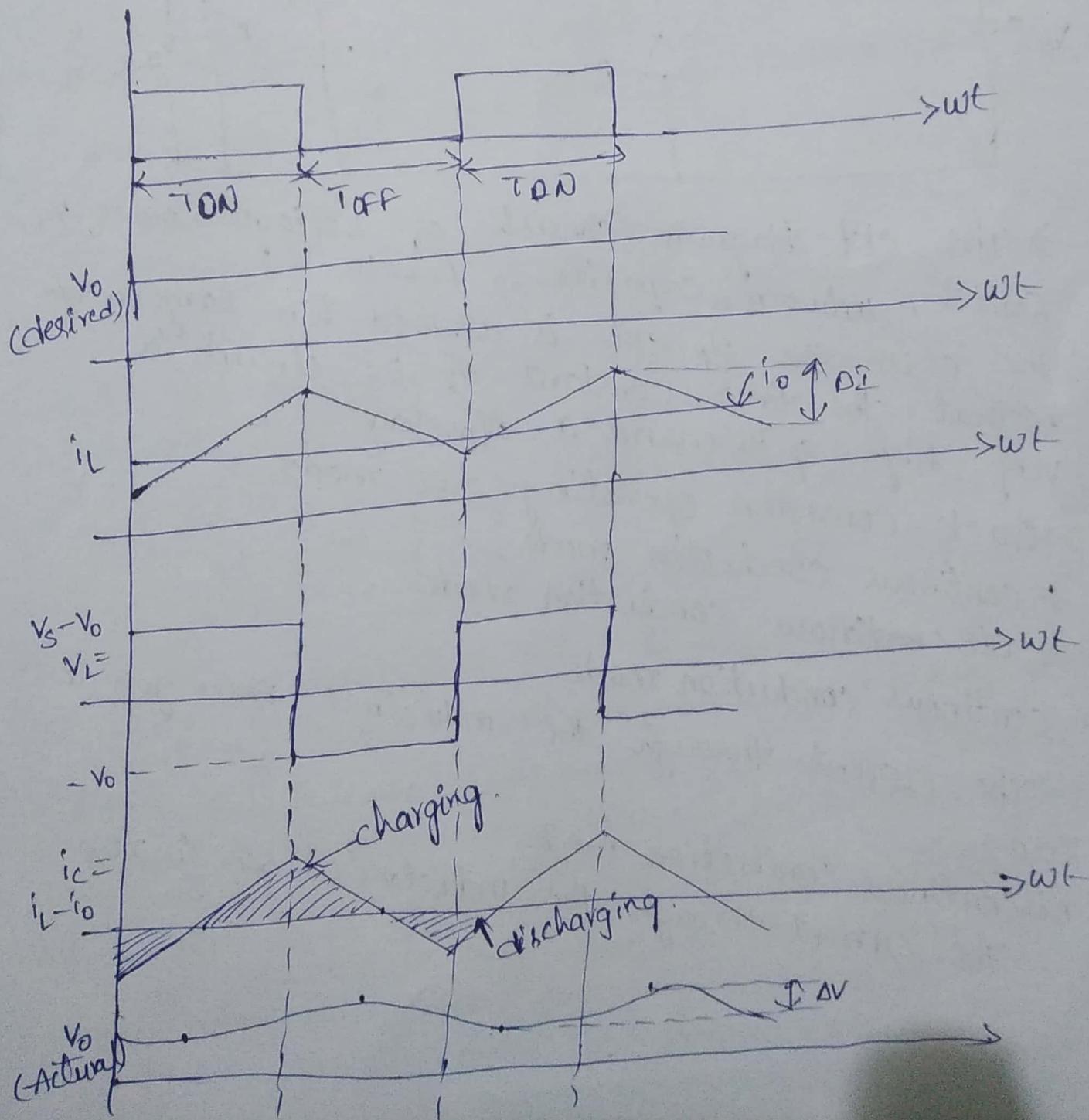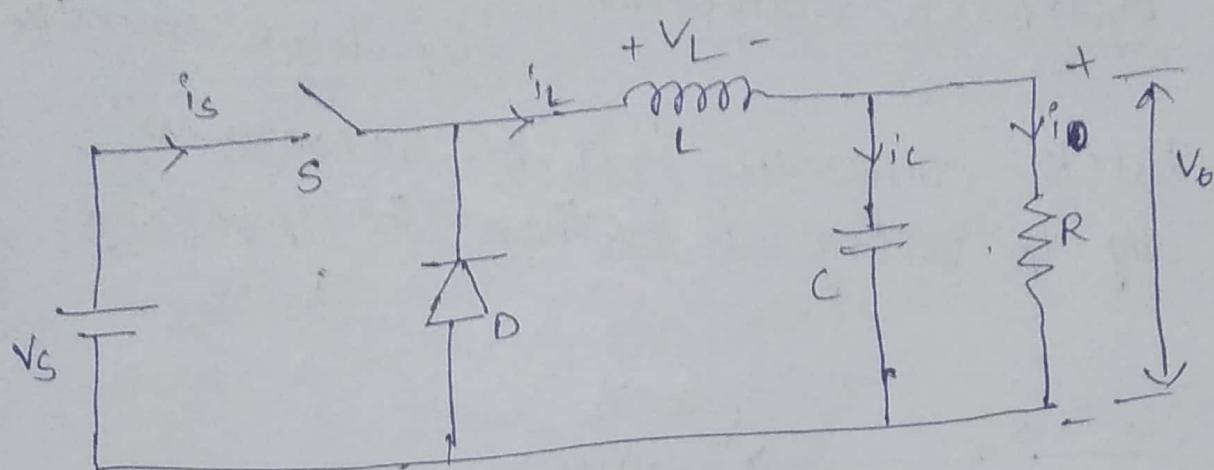

→ Already we know when the inductor "L" value is large means the o/p voltage is constant

→ case i) when switch "S" is ON

~~for diodes~~, the diode "D" becomes reverse bias current (I_L) flows through the

so the o/p voltage

is, L, C, R

→ During this time the inductor stores energy so inductor current increases gradually

→ During this time the voltage is $\rightarrow V_L = V_S - V_o$

case ii) when switch "S" is OFF

the diode "D" becomes forward bias and the stored energy in the "L" discharge through the

diode & RC circuit

∴ The current through the inductor "I_L" decreases gradually

In this case V_L is the voltage across the "L"
 V_o is the o/p voltage

Apply mesh analysis, we get

$$V_L + V_o = 0$$

$$V_L = -V_o$$

→ Again during the turn on time increases turn off time decreases

→ "i_c"

$$i_L = i_{ct} + i_o$$

$$\therefore i_c = i_L - i_o$$

we already know i_L , in order to get i_c
we know V_o , & load is resistive nature
 \therefore o/p current same as that as o/p voltage with
reduced magnitude.

→ when capacitor current is "+ve" charging current
is "-ve" discharging current

→ Both RSpC are connected parallel

\therefore The voltage across the capacitor is same as that
of the o/p voltage V_o

when capacitor is charging o/p voltage is maximum
when capacitor is discharging o/p voltage is decreased

→ observe desired o/p voltage & actual o/p has some
ripple content (ΔV)

* O/p voltage is

$$(V_s - V_o)t_{on} + (-V_o)t_{off} = 0$$

$$V_s \cdot t_{on} = V_o \cdot (t_{off} + t_{on})$$

$$\{ \because T = t_{on} + t_{off} \}$$

$$V_s \cdot t_{on} = V_o \cdot T$$

$$V_o = \left[\frac{t_{on}}{T} \right] V_s$$

$$V_o = \alpha \cdot V_s \quad \{ \because \alpha = \text{duty cycle.} \}$$

Design of filter inductance (L) & capacitance (C) :-

$$L \rightarrow V_L = L \frac{di}{dt}$$

when switch is ON

$$\therefore V_L = V_s - V_o$$

$$V_s - V_o = L \cdot \frac{di}{dt}$$

$$V_s - V_o = \cancel{L} \cdot L \cdot \frac{\Delta I}{t_{on}} \Rightarrow t_{on} = \frac{L \cdot \Delta I}{V_s - V_o}$$

$$t_{on} = \frac{L \cdot \Delta I}{V_s - V_o} \rightarrow ①$$

when switch is OFF

$$\therefore V_L = -V_o$$

$$-V_o = L \cdot \frac{\Delta I}{t_{off}} \Rightarrow t_{off} = L \cdot \frac{\Delta I}{V_o}$$

$$t_{off} = L \cdot \frac{\Delta I}{V_o} \rightarrow ②$$

we know

$$T = T_{on} + T_{off}$$

$$= L \cdot \frac{\Delta I}{V_s - V_o} + L \cdot \frac{\Delta I}{V_o}$$

$$= L \cdot \Delta I \left[\frac{1}{V_s - V_o} + \frac{1}{V_o} \right]$$

$$= L \cdot \Delta I \left[\frac{V_o + V_s - V_o}{V_o(V_s - V_o)} \right]$$

$$= L \cdot \Delta I \left[\frac{V_s}{V_o(V_s - V_o)} \right]$$

$$\boxed{L = \frac{T \cdot V_o (V_s - V_o)}{\Delta I \cdot V_s}}$$

C → we know $Q = C \cdot V$
in buck converter $\Delta Q = C \cdot \Delta V \rightarrow ①$

$$\Delta Q = \frac{1}{2} \frac{T}{2} \times \frac{\Delta I}{2} = \frac{T \Delta I}{8} \rightarrow ②$$

Equ ① & ②



$$C \cdot \Delta V = \frac{T}{8} \cdot \frac{\Delta I}{\Delta V}$$

$$C = \frac{T \cdot \Delta I}{8 \cdot \Delta V} \Rightarrow \Delta I = \frac{T \cdot V_o (V_s - V_o)}{L \cdot V_s}$$

$$\boxed{C = \frac{T^2 \cdot V_o (V_s - V_o)}{L \cdot V_s \cdot 8 \cdot \Delta V}}$$

Boost converter:- (step up converter)

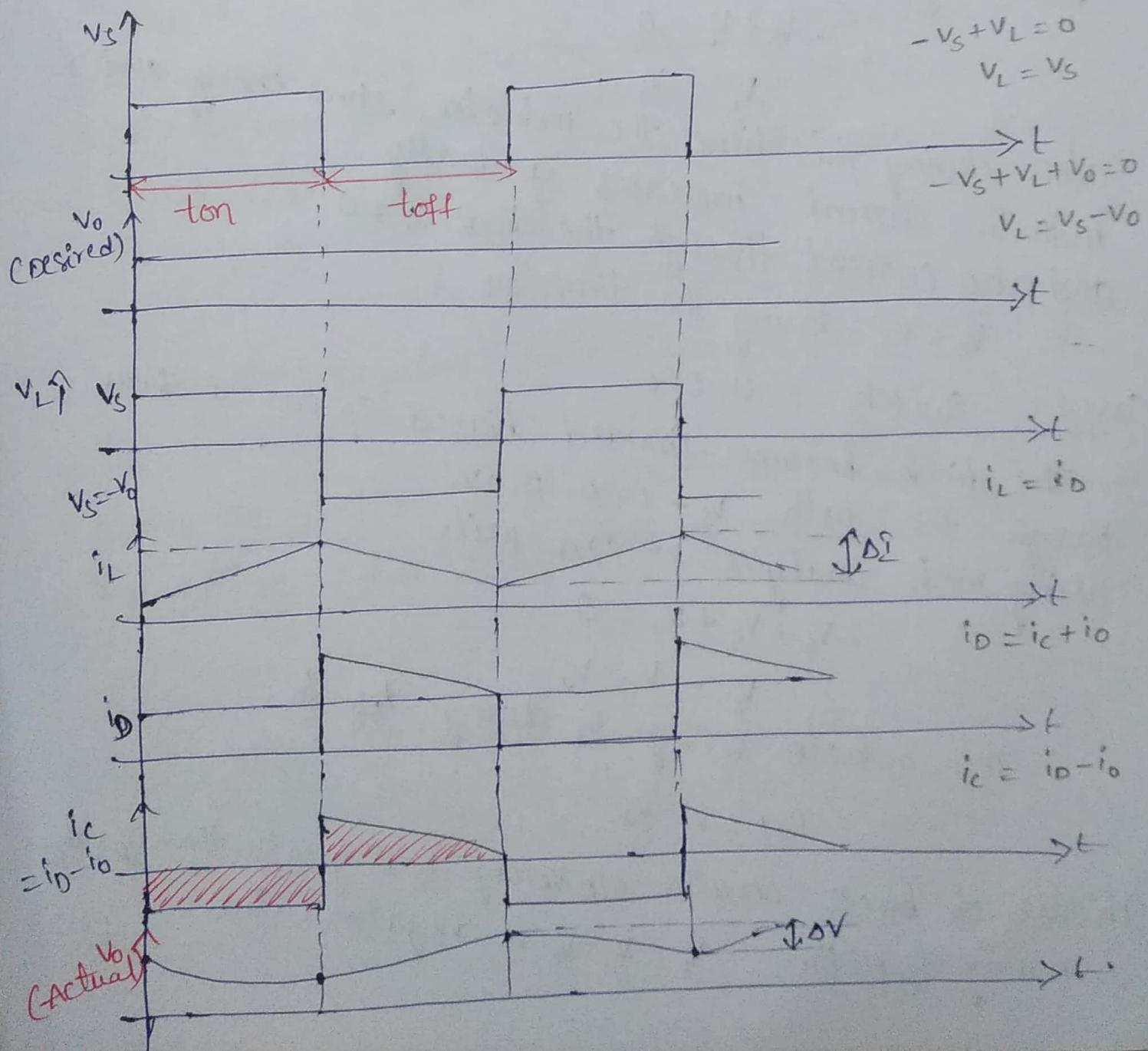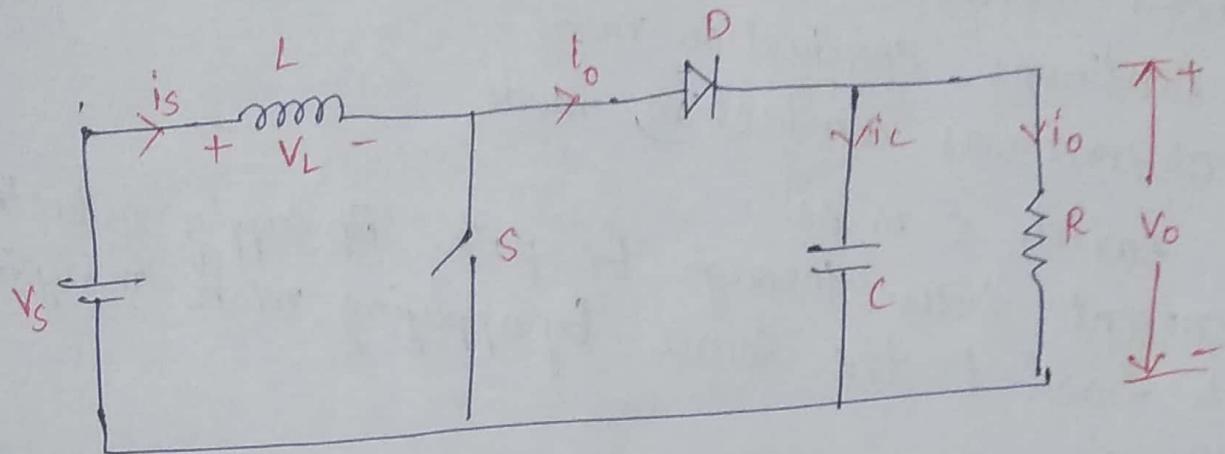→ In a boost converter the o/p voltage is greater than the i/p voltage hence named as boost ckt diagram of boost converter



→ it consists of i/p source V_s , inductor, switch, diode, capacitor & resistor

Both resistor & capacitor connected in parallel

→ The boost converter can operate in two modes.

1. continuous conduction mode

2. Discontinuous conduction mode

Case(i) switch 's' is ON

The current flows through the path i/p supply inductor switch back to the source. by applying mesh analysis we will get

$$-V_s + V_L = 0$$

$$V_L = V_s$$

also during this time the inductor stores energy and the inductor current increases gradually.

and also current through the diode $I_d \neq 0$

so, $V_L = V_s$ during the time on

Case(ii) switch 's' is OFF

The diode becomes forward biased & current flows through the path $V_s + L, D - R \rightarrow V_s$ using mesh analysis we can write

$$-V_s + V_L + V_o = 0$$

$$V_L = V_s - V_o$$

∴ The inductor voltage V_L during T_{off} is

$$V_{off} = V_s - V_o$$

In case of buck converter o/p voltage V_o is greater than i/p voltage
∴ during T_{off} time $V_L = V_s - V_o$ is negative value

→ During this interval the energy stored in the inductor is released to the load
∴ inductor current decreases gradually
→ Here, when switch is off $i = i_0$

∴ $i_L = i_0$
The diode current i_0 can be divided into $i_C \& i_D$
Apply nodal analysis we will get

$i_0 = i_C + i_D$
So, if we want to draw the current through the capacitor i_C we have to draw i_D
Here we are using Resistive load therefore i_C is a straight line with the reduced magnitude
→ Using $i_0 \& i_D$ we can draw i_C , because i_C is equal to $i_D - i_0$

→ During the negative cycle capacitor is discharging minimum O/P voltage
During the positive cycle capacitor is charging maximum O/P voltage. This magnitude is DV . i.e., voltage ripple

output load voltage

$$V_s \cdot t_{on} + (V_s - V_o) t_{off} = 0$$

$$V_s (t_{on} + t_{off}) - V_o t_{off} = 0$$

$$V_s (t_{on} + t_{off}) = V_o t_{off}$$

$$V_s \cdot T = V_o \cdot T_{off}$$

$$V_o = \frac{V_s \cdot T}{T_{off}}$$

$$\therefore T_{off} = T - T_{on}$$

$$V_o = V_s \cdot \frac{T}{T - T_{on}}$$

$$V_o = \frac{V_s}{1 - \frac{T_{on}}{T}}$$

$$\therefore \frac{T_{on}}{T} = \alpha$$

filter inductance :-

$$V_L = L \cdot \frac{di}{dt}$$

when switch is ON, $V_L = V_s$

$$V_s = L \cdot \frac{\Delta I}{t_{on}} \Rightarrow t_{on} = \frac{L \cdot \Delta I}{V_s} \rightarrow ①$$

when switch is OFF, $V_L = V_s - V_o$

$$V_s - V_o = L \cdot \frac{\Delta I}{t_{off}} \Rightarrow t_{off} = \frac{L \cdot \Delta I}{V_s - V_o} \rightarrow ②$$



we know $T = t_{on} + t_{off}$

$$= \frac{L \cdot \Delta I}{V_s} + \frac{L \cdot \Delta I}{V_s - V_o}$$

$$= L \cdot \Delta I \left[\frac{1}{V_s} - \frac{1}{V_s - V_o} \right]$$

Buck-Boost converter

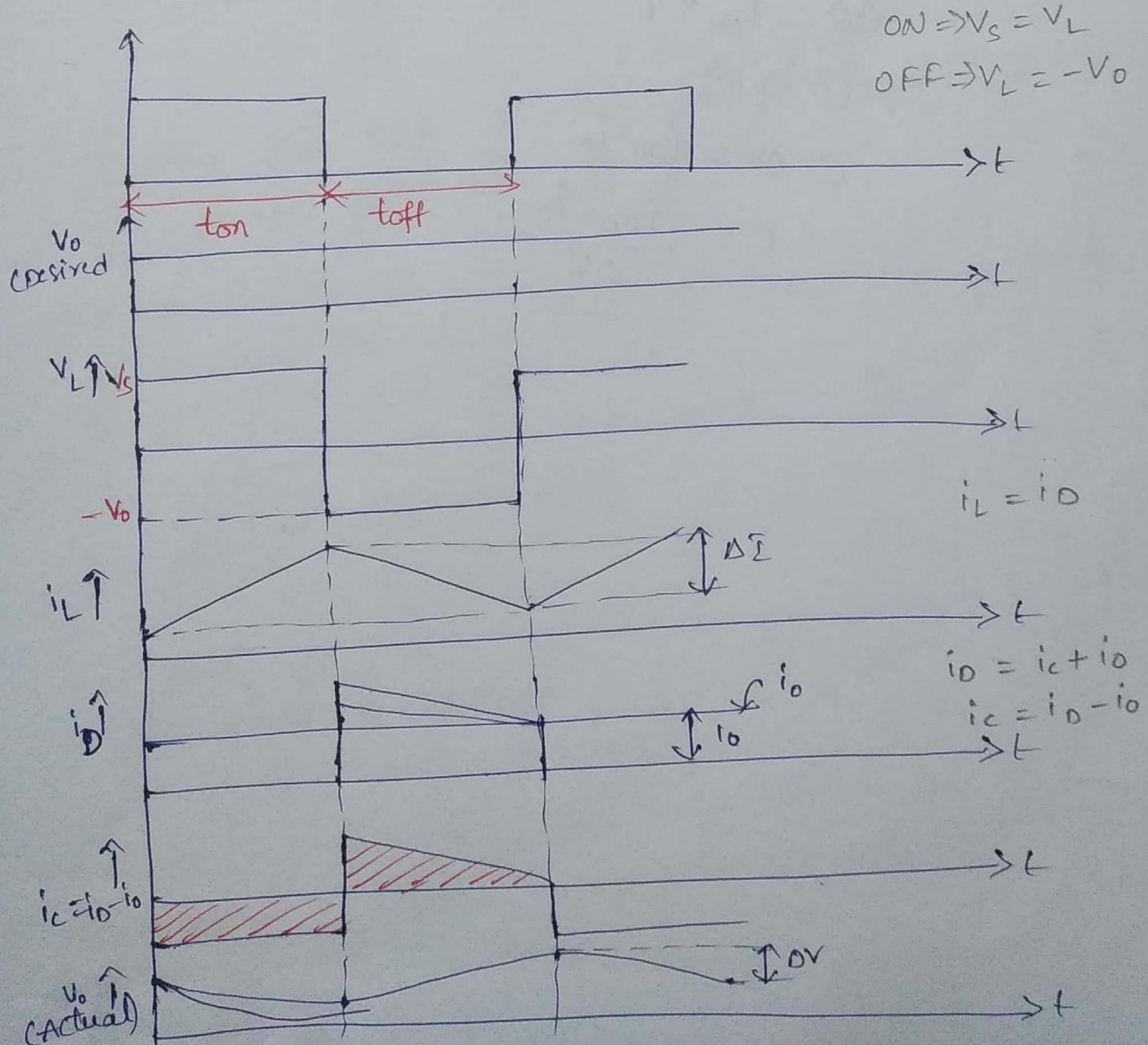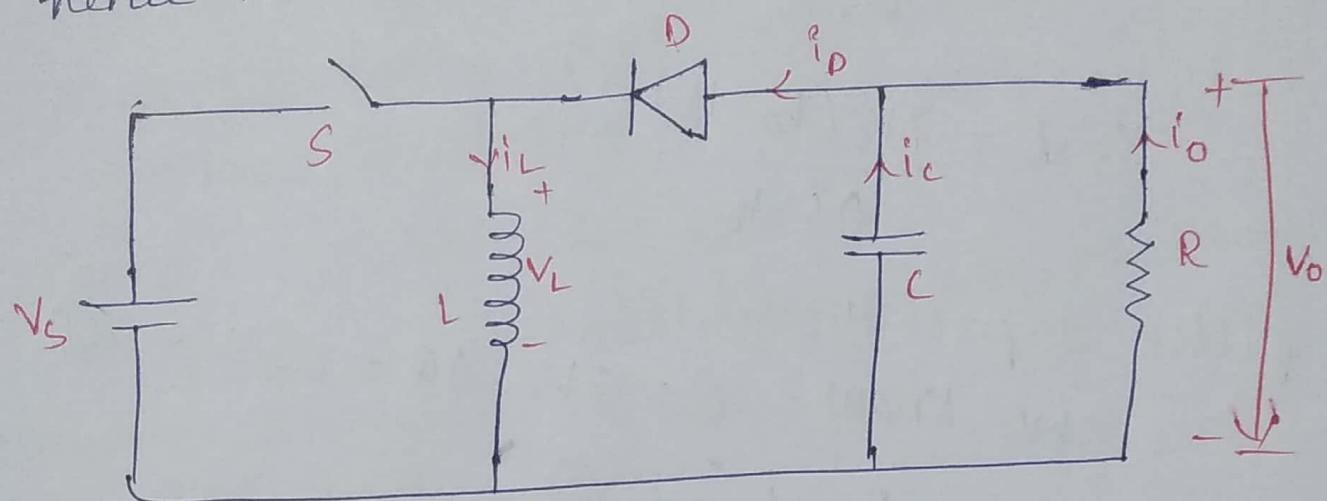→ A Buck-Boost converter provides o/p voltage that may less than or greater than the i/p voltage hence named as Buck-Boost converter



$$= L \cdot \Delta I \left[\frac{V_S - V_o - V_S}{V_S(V_S - V_o)} \right]$$

$$\therefore T = -\frac{L \cdot \Delta I \cdot V_o}{V_S(V_S - V_o)}$$

$$\therefore L = \frac{T V_S (V_o - V_S)}{\Delta I \cdot V_o}$$

filter capacitance :- (c)

we know, $Q = CV$, $\Delta Q = C \Delta V \rightarrow ①$

$$\Delta Q = t_{on} \times i_o \rightarrow ②$$

Equ ① & ②

$$C \cdot \Delta V = t_{on} \times i_o$$

$$C = \frac{t_{on} \cdot i_o}{\Delta V}$$

B

→ it consists of o/p voltage polarity ~~is~~ opposite to that of i/p voltage
∴ Buck-Boost converter is also known as inverting regulator

→ it can divide two modes
i) circulating mode current mode.
ii) non circulating current mode

case i) switch is 'ON'

= diode 'D' becomes ~~forward~~ reverse bias, the current flows through the path $V_s - S - L - V_s$

Apply mesh analysis

$$V_s = V_L$$

During this time the inductor ~~starts~~ stored energy & i_L increases gradually. & $i_D = 0$

case ii) switch is 'S' OFF

During the t_{off} time the stored energy can be transferred to the load

∴ current path $L - C - D - R$

Apply mesh analysis

$$V_L = -V_o$$

During this time t_{off} the energy stored in the inductor is transferred to the load

∴ i_L decreases gradually

$i_L = i_D$, this magnitude is ΔI

→ ~~apply~~ we draw capacitor current is

∴ apply node analysis

$$\therefore i_b = i_c + i_o$$

$$i_c = i_b - i_o$$

→ Actual o/p voltage V_o
 During turn on time capacitor current is discharging
 after discharging V_o is minimum value.
 During +ve i_c capacitor current C is charging
 V_o is maximum value.
 This magnitude is ΔV

⇒ o/p voltage using volt-second balance theory

$$t_{on} \times V_s + t_{off} \times (-V_o) = 0$$

$$V_s \cdot t_{on} = V_o \cdot t_{off}$$

$$V_o = \frac{V_s \cdot t_{on}}{t_{off}}$$

$$V_o = \frac{V_s \cdot \frac{ton}{T}}{1 - ton/T}$$

$$V_o = \frac{V_s \cdot \frac{\alpha}{T}}{1 - \alpha}$$

$$= \frac{V_s \cdot \alpha}{1 - \alpha}$$

$$\therefore V_o = \frac{V_s \cdot \alpha}{1 - \alpha}$$

The value of ' α ' is 0 to 1

$0 < \alpha < 0.5$, Buck ($V_o < V_s$)

$0.5 \leq \alpha < 1$, Boost ($V_o > V_s$)

filter inductance L :-

$$V_L = L \cdot \frac{di}{dt}$$

Switch S-ON; $V_L = V_s$

$$V_s = L \cdot \frac{\Delta I}{t_{on}} \Rightarrow t_{on} = \frac{L \cdot \Delta I}{V_s} \rightarrow ①$$

Switch S-OFF $V_L = -V_o$

$$-V_o = L \cdot \frac{-\Delta I}{t_{off}} \Rightarrow t_{off} = \frac{L \cdot \Delta I}{V_o} \rightarrow ②$$

we know that

$$T = t_{on} + t_{off}$$

$$T = \frac{L \cdot \Delta I}{V_s} + \frac{L \cdot \Delta I}{V_o}$$

$$= L \cdot \Delta I \left[\frac{1}{V_s} + \frac{1}{V_o} \right]$$

$$T = L \Delta I \left[\frac{V_o + V_s}{V_s \cdot V_o} \right]$$

$$L = \frac{T \times V_o \cdot V_s}{\Delta I [V_o + V_s]}$$

filter capacitance 'C' :-

$$Q = CV \Rightarrow \Delta Q = C \cdot \Delta V \rightarrow ①$$

$$\Delta Q = ton \cdot i_o \rightarrow ②$$

Eqn ① & ②, we get

$$C \cdot \Delta V = ton \cdot i_o$$


$$\therefore C = \frac{ton \cdot i_o}{\Delta V}$$

Classification of chopper circuits:-

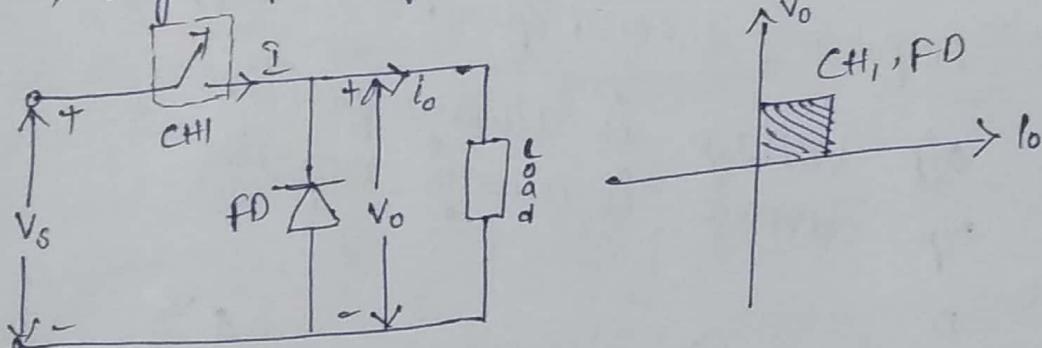
1. Class-A chopper :-

chopper:- it is a ^{switch} power electronic device which fixed DC voltage to variable voltage it is nothing but a high speed switch. which connects or disconnects the load from source at a high rate to get variable voltage at o/p

→ class A chopper is also known as step down / first quadrant chopper so, avg o/p voltage is always less than the p.d. voltage



$$T = T_{on} + T_{off}$$

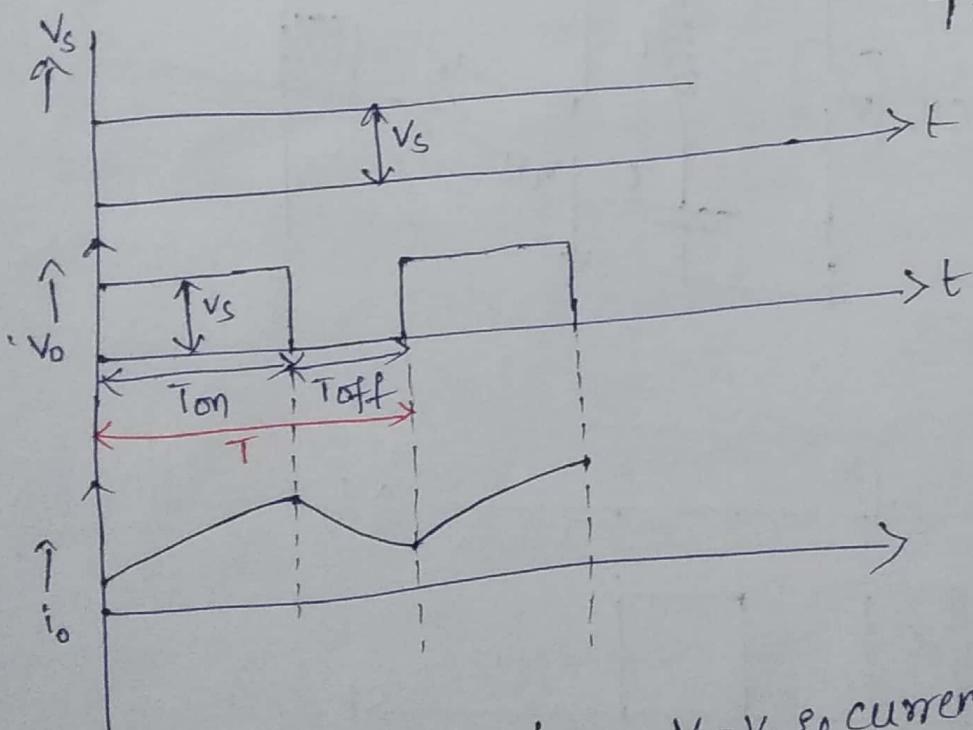

- when chopper CTH1 is on, $V_0 = V_s$ & current i_0 flows in the arrow direction
- when chopper CTH1 is off, $V_0 = 0$, but i_0 is the load current continuous flowing in the same direction through freewheeling diode FD.



The average values of both load voltage and current v_o & i_o are always positive.

$$v_o = \frac{1}{T} \int_0^{T_{on}} v_s dt = \frac{v_s}{T} \int_0^{T_{on}} dt = \frac{v_s}{T} \cdot T_{on} \quad \left[\frac{T_{on}}{T} = \alpha \right]$$

$$v_o = \alpha \cdot v_s \Rightarrow v_o = 0 \text{ (minimum value)}$$

$$v_o = v_s \text{ (maximum value)}$$

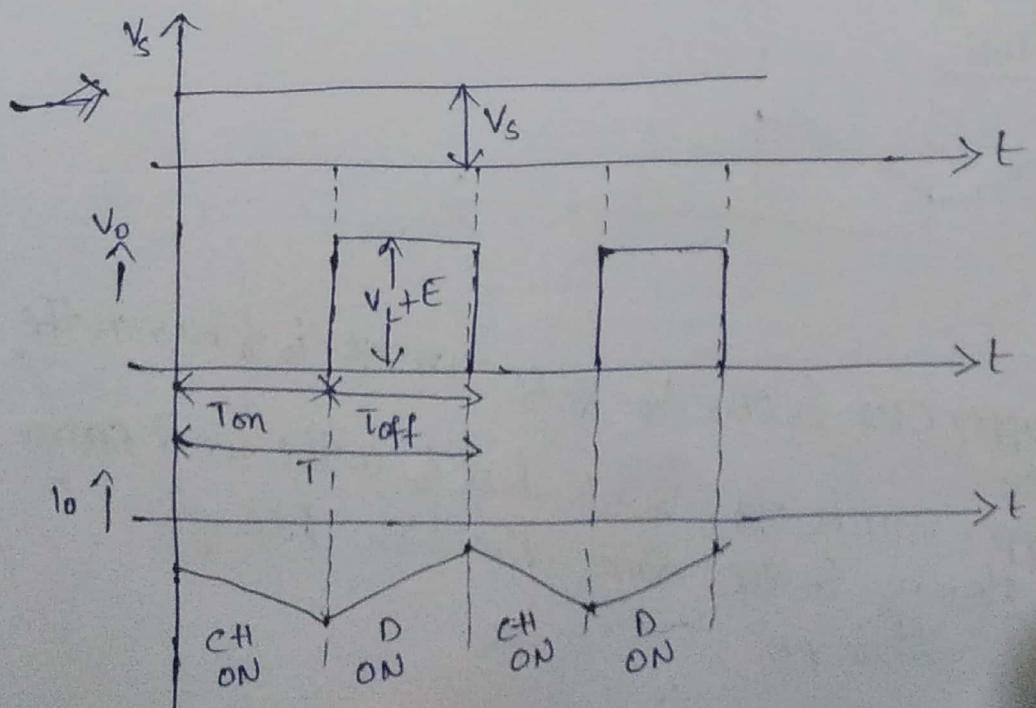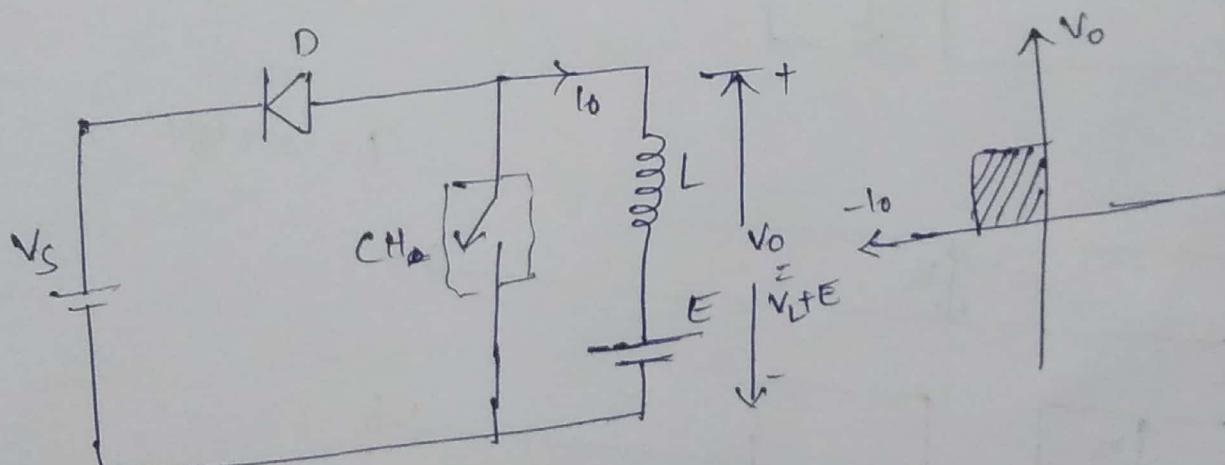\Rightarrow class-B chopper [second quadrant chopper]
because off voltage is always positive if
off current is always negative



→ when CH is on, $V_o = 0$ but load voltage E drives current through L and CH.

→ inductance L stores energy during T_{on} (on period) of CH.

→ when CH is off,

$$V_o = \left(E + L \frac{di}{dt} \right)$$
 exceeds source voltage V_s .

As a result, diode D' is forward-biased and begins conduction

thus allowing power to flow to the source.

→ CHopper CH may be on or off, current i_o flows out of the load, current i_o is treated as negative.

$\therefore V_o$ is +ve, i_o is -ve

→ power flow is always from load to source

As load voltage is

$$V_o = \left[E + L \cdot \frac{di}{dt} \right]$$
 is more than source voltage V_s .

Type-B chopper is also called step-up chopper

⇒ Class-C chopper [~~single~~ quadrant chopper]

→ it can operate first two quadrants
means the power can transfer from source to load (or)
load to source

we know that class A operate in first quadrant



class B operate in second quadrant

\therefore class C chopper can be obtained as the parallel connection of class A and class B chopper

from the circuit diagram

$V_s - CH_1 - FD -$ load are flowing class-A chopper

D - $CH_2 -$ load are flowing class-B.

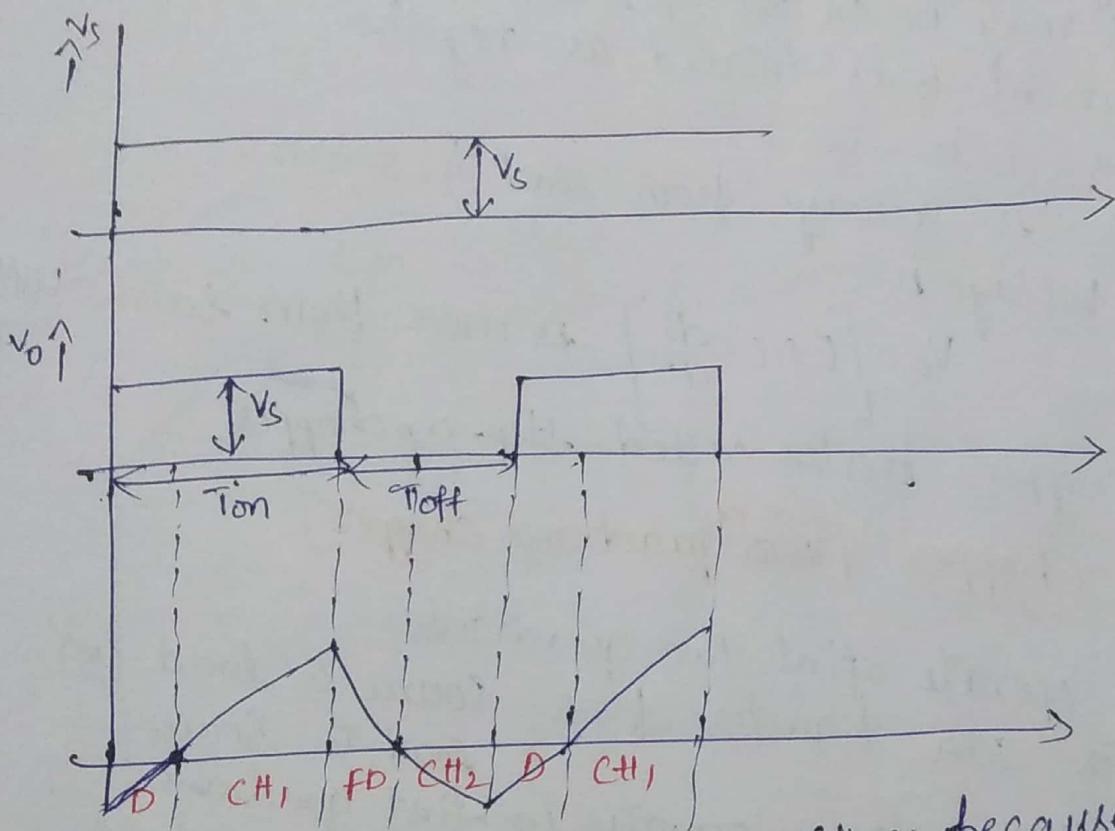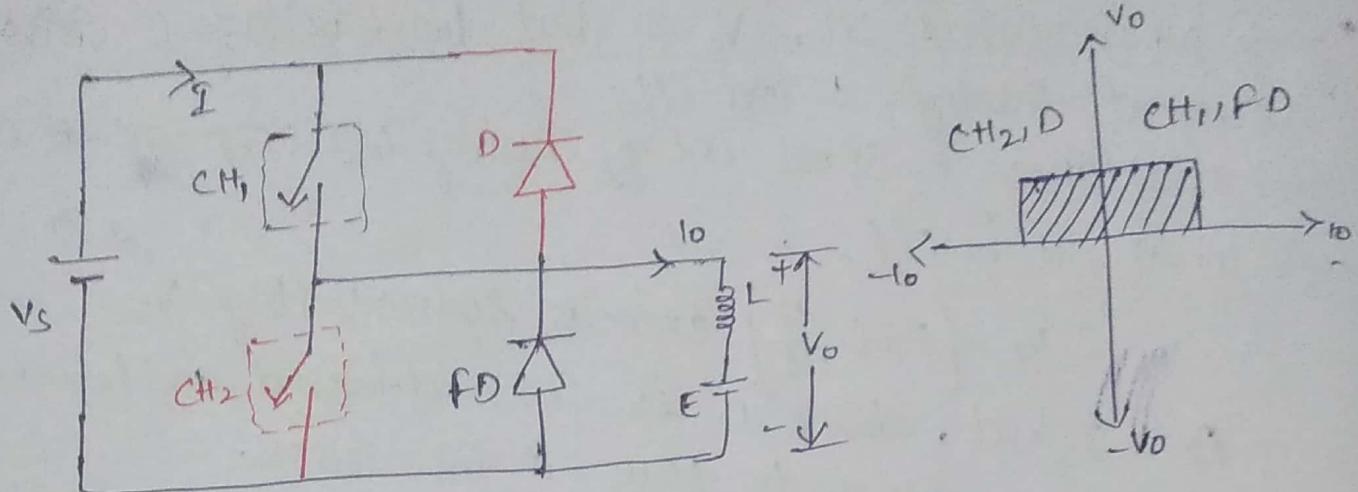

- The o/p voltage V_0 is always positive because of the presence of free wheeling diode FD across the load
- when CH_2 is on, or FD conducts,
- o/p voltage $V_0 = 0$ &
- CH_1 is on, or diode D2 conducts
- o/p voltage $V_0 = V_s$
- The load current i_0 can reverse its direction
- when CH_1 is on or FD conducts at load current is +ve
- load current is -ve if CH_2 is on or D2 conducts

→ class D chopper is also known as two quadrant chopper because the operation of this type of chopper is confined to the first & fourth quadrant means the off voltage V_o is either positive or -ve. but off current is always positive.

→ Here C_{H1} & C_{H2} represents two choppers & D_1, D_2 are two diodes

Case(i) Both C_{H1} & C_{H2} are 'ON'

current flows path $V_s - C_{H1} - L - C_{H2} - V_o$
∴ the load is directly connected to the V_s





∴ $V_o = V_s$
and off current is +ve & increases gradually
→ Here D_1, D_2 are reverse biased by the source voltage V_s
hence they can be treated as open switch

Case(ii) Both C_{H1} & C_{H2} are OFF simultaneously
when the choppers are made simultaneously
the current through the load does not suddenly drops
to zero due to the inductive nature of the load
because of the presence of induced voltage in inductor
diode D_1, D_2 becomes forward biased
thus D_1, D_2 starts conducting & connects the load to the

source
→ Here the induced voltage in inductor is ~~base~~ negative
induced voltage in the inductor V_L the diode D_1, D_2
are forward biased & current flows from the
load to the source

- Avg load voltage is always positive but avg load current may be positive or negative
- This type of chopper configuration is used for motoring & regenerative braking of dc motors

class-D chopper [Two quadrant chopper]

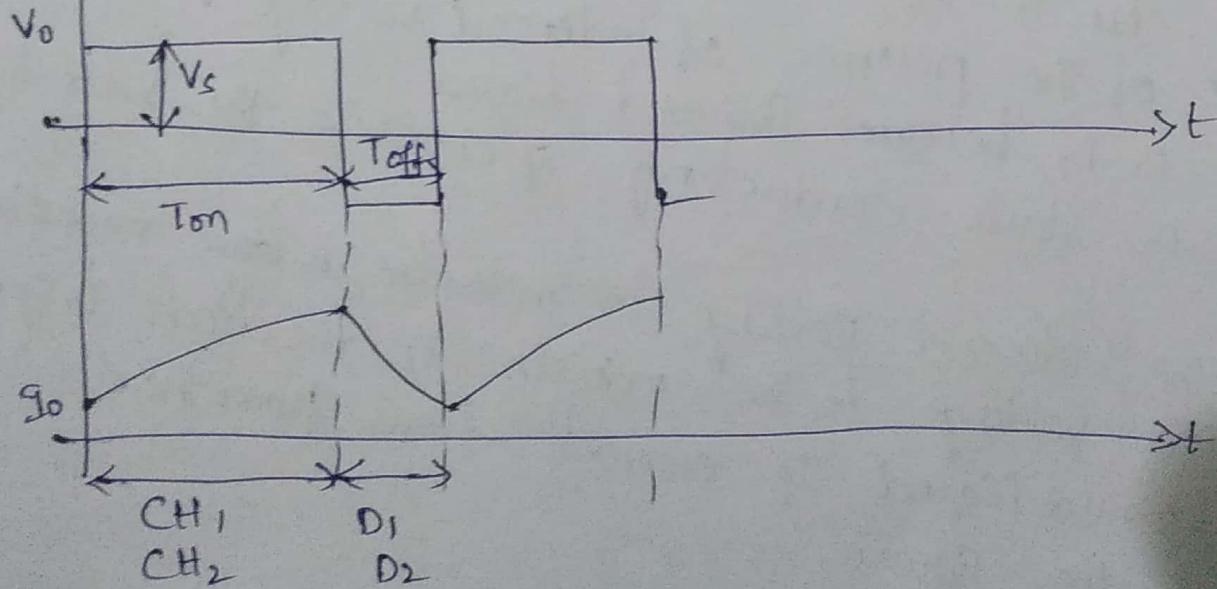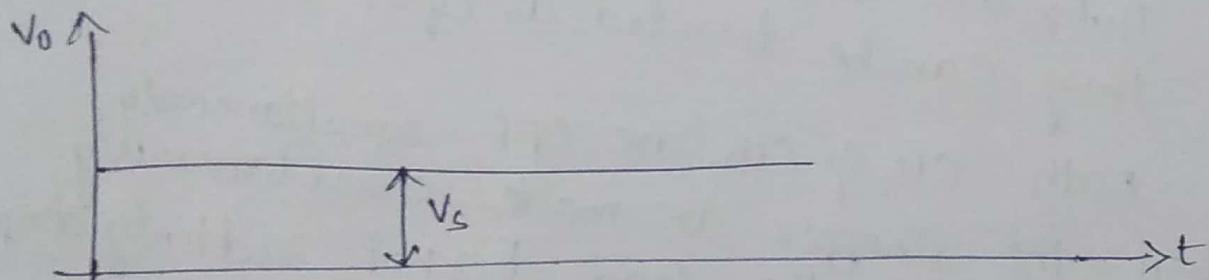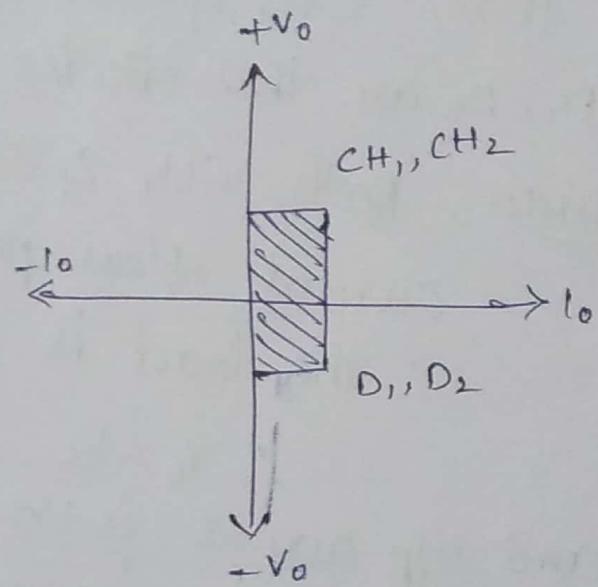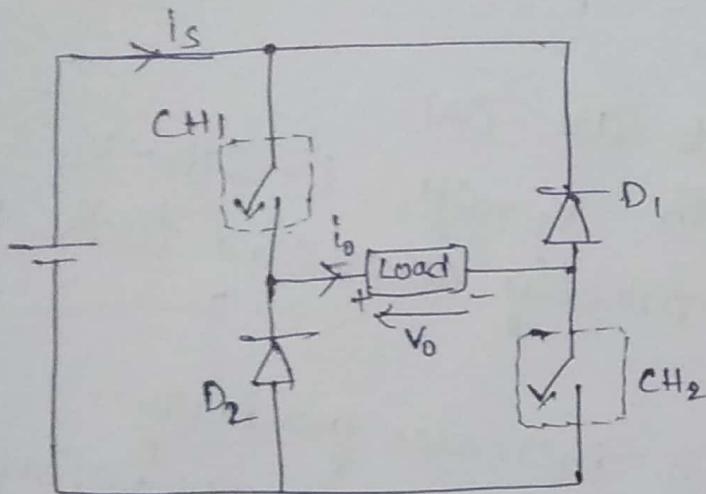

$\rightarrow \therefore$ o/p voltage is +ve & o/p v_o is -ve
hence the operation of chopper is in the fourth quadrant
and the power flows from load to the source

\rightarrow when CH₁, SP, CH₂ ON \rightarrow ~~o/p~~ $V_o = +ve$, $I_o = +ve$

first quadrant operation
power flows from source to load

\rightarrow when CH₁, SP, CH₂ OFF \rightarrow $V_o = -ve$, $I_o = +ve$
fourth quadrant operation
power flows from load to source


Average value of o/p voltage

$$V_o = \frac{V_s \cdot T_{on} - V_s \cdot T_{off}}{T}$$

$$V_o = V_s \cdot \frac{T_{on} - T_{off}}{T}$$

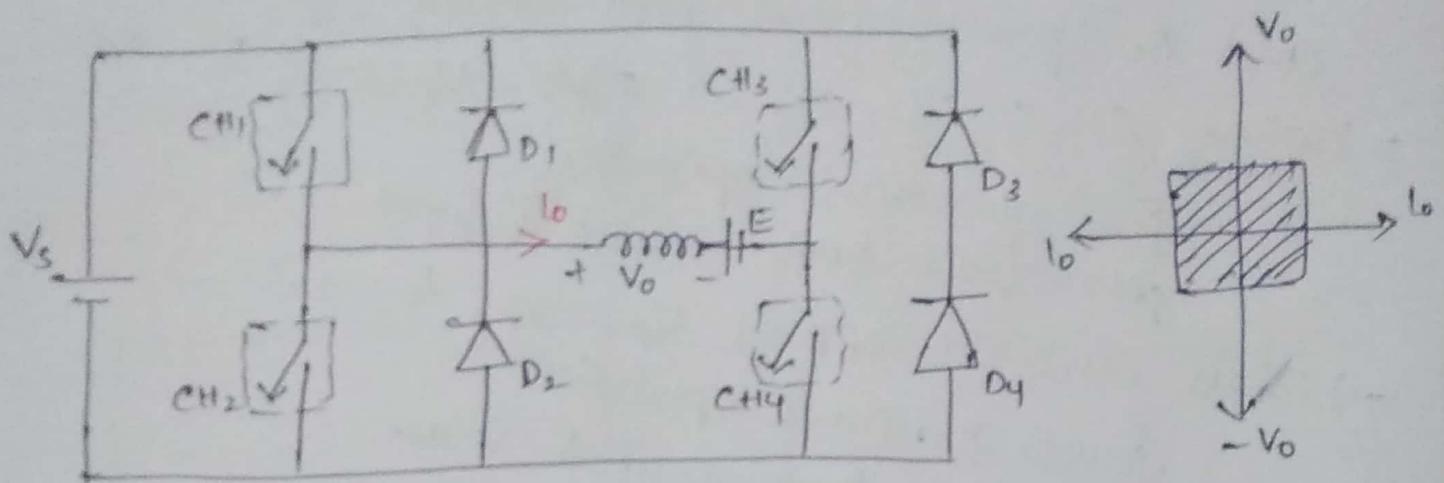- i) In case $T_{on} > T_{off}$, $\alpha > 0.5$, V_o is +ve
- ii) In case $T_{on} < T_{off}$, $\alpha < 0.5$, V_o is -ve
- iii) In case $T_{on} = T_{off}$, $\alpha = 0$, $V_o = 0$.

\Rightarrow class-E chopper [four quadrant chopper]:-



CH₂ operated

CH₂-D₄; L stores energy
CH₂-OFF; then
D₁-D₄ conduct

CH₁ operated

CH₁-CH₄ ON
CH₄-off; then CH₄-D₂ conduct

CH₃ operated

CH₃-CH₂: ON
CH₃-off; then
CH₂-D₄ conduct
E reversed

CH₄ operated

CH₄-D₂; L stores energy
CH₄-off; then D₂-D₃ conduct
E reversed.

→ four quadrant chopper can operate in all four quadrants
∴ The power can flow either from source to load or from load to source

→ it basically consists of four semiconductor switches ($C_{H1}, C_{H2}, C_{H3}, C_{H4}$) and four diodes [D_1, D_2, D_3, D_4]
→ In first quadrant operation the chopper C_{H1} is operated & C_{H4} is ON, C_{H1} is either ON/OFF

→ In second quadrant operation C_{H2} is operated
→ In third quadrant operation C_{H3} is operated & C_{H2} is always ON

→ In fourth quadrant operation C_{H4} is operated

case i : C_{H1} is ON, here both C_{H1} & C_{H4} are ON simultaneously

∴ current flows through the path

$$V_s - C_{H1} - \text{load} - C_{H4} - V_s$$

$$\therefore I_o = +ve, V_o = +ve \text{ & } V_o = V_s$$

∴ the power flows from source to the load & also when the current flows through the load the inductor stores the energy the voltage induced in the inductor

case ii : C_{H1} is OFF.

+ve current freewheels through C_{H4}, D_2 .

Here, both V_o, I_o can be controlled in the first quadrant

case iii : C_{H1} is OFF, when C_{H1} is OFF due to the induced voltage in the inductor the diode D_2 becomes forward biased

∴ The current flows through the path

$$C_{H4} - D_2 - \text{load}$$

$$\therefore I_o = +ve$$

Case ii :- C_{T2} is operated

C_{T1} , C_{T3} & C_{T4} are kept off.
with C_{T2} - ON, reverse (or negative) current flows
 $L - C_{T2} - D_4 - E$

Inductor L stores energy during the time C_{T2} is ON.

- when C_{T2} is OFF,
current fed back to the source through diodes D_1, D_4
- Here $[E + L \cdot \frac{di}{dt}]$ is more than the source voltage V_s .

$\therefore V_o = +ve, i_o = -ve$
it is second quadrant operation of chopper.
power is fed back from load to source.

Case iii :- C_{T1} is kept off, C_{T2} is kept ON

C_{T3} is operated.

- polarity of load emf E must be reversed for this quadrant working
- when C_{T3} is ON,
load gets connected to source V_s
 $\therefore V_o, i_o$ are negative leading to the third quadrant operation.
- when C_{T3} is OFF
negative current freewheels through C_{T2}, D_4
so, V_o, i_o are controlled in third quadrant

Case iv :- CT₄ is operated &
other devices are kept off.
load emf E has its reverse polarity
operation is in the fourth quadrant.

- when CT₄ - ON
+ve current flows through
CT₄ - D₂ - L - E
inductor L stores energy
- when CT₄ - Off
current is fed back to source through diodes
D₂, D₃.
here load voltage is negative
but load current is positive
power is fed back from load to source.

Thyristor chopper circuits:-

- Actually, a chopper consists of main power semiconductor device together with their turn-on & turn-off mechanisms
 - In low power chopper ckt: ptransistors, GTOs, PMOSFET etc
 - In high power chopper ckt: thyristors are in common use
 - The process of opening, or, turning-off, a conducting thyristor is called commutation
 - All these commutation ckt can, be broadly classified into two groups as
- a) forced commutation:- In this commutation, external elements L and C which do not carry the load current continuously, are used to turn-off a conducting thyristor.
- i) forced voltage commutation:- In this scheme, a conducting thyristor is commutated by the application of a pulse of large reverse voltage. This reverse voltage is usually applied by switching a previously charged capacitor.
- The sudden application of reverse voltage across the conducting thyristor reduces the anode current to zero rapidly. Then the presence of reverse voltage across the SCR aids in the completion of its turn-off process.
- ii) current commutation:- In this scheme, an external pulse of current greater than the load current is passed in the reversed direction through the conducting SCR. When the current pulse attains a value equal to the load current, net pulse current through thyristor becomes zero and the device is turned off.
- The current pulse is usually generated by an initially charged capacitor.

→ An important feature of current commutation is the connection of a diode in antiparallel with the main thyristor so that voltage drop across the diode reverse biases under the main SCR.

b) load commutation:- In load commutation, a conducting thyristor is turned off. when load current flowing through a thyristor either

- i) either zero due to the nature of load circuit parameters (or)
- ii) is transferred to another device from the conducting thyristor

\Rightarrow voltage commutated = chopper :-

voltage commutated =
 This chopper is generally used in high-power ckt's where load fluctuation is not very large. This chopper is generally used in high power circuits also known as parallel-capacitor turn-off chopper, impulse commutated chopper (or) classical chopper

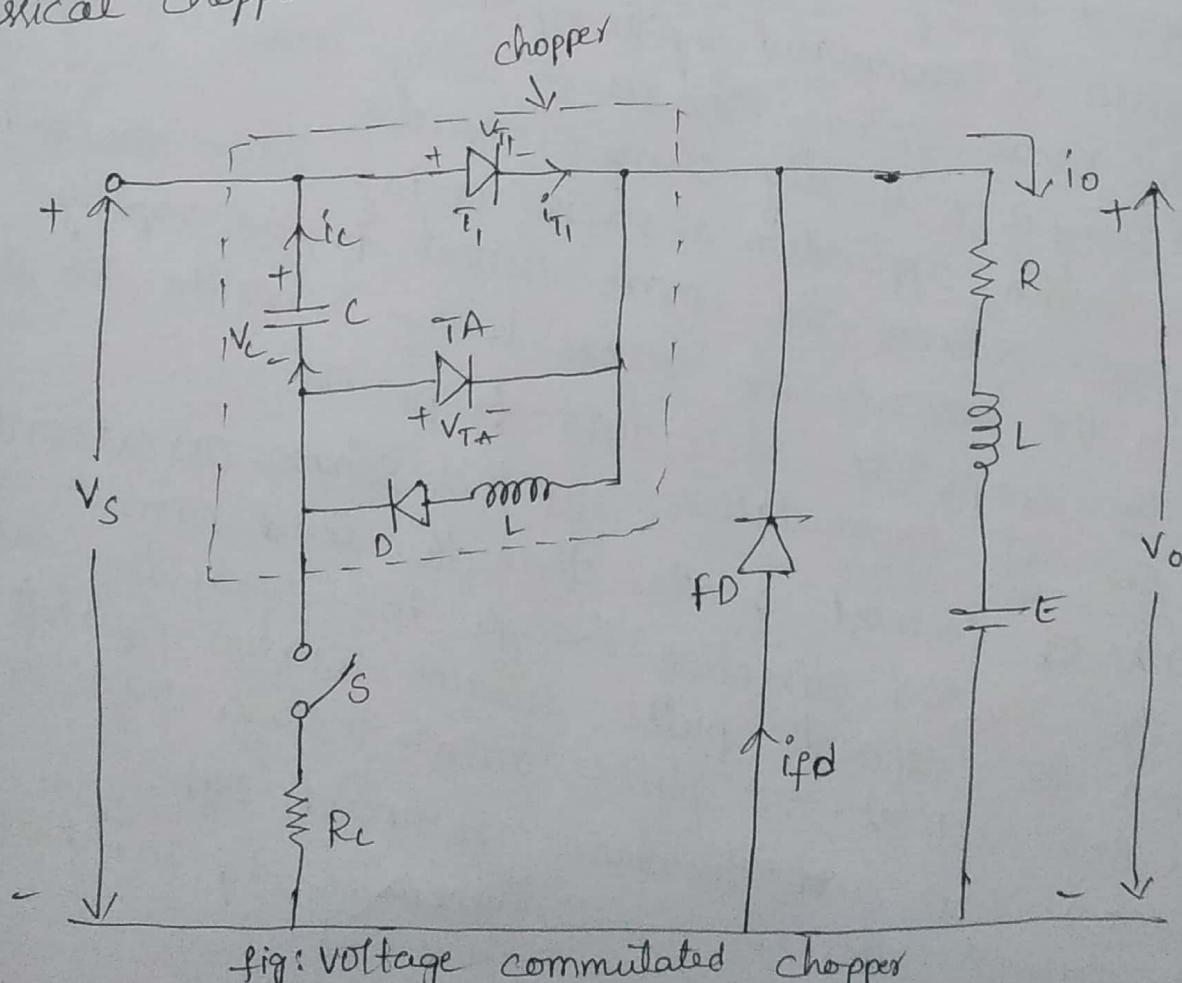


fig: Voltage commutated chopper

→ Thyristor T_1 is the main power switch. Commutation circuitry for this chopper is made up of an auxiliary SCR TA, capacitor C, diode D and inductor L.

FD is the freewheeling diode connected across the RLE type load
→ Working of this chopper can start only if the capacitor C is charged with polarities as marked.

This can be achieved in one of the two ways as under
i) Close switch S so that capacitor gets charged to voltage V_S through source V_S , C, S, ϵ_P charging Resistor R_C .

Switch S is then opened
ii) Auxiliary thyristor TA is triggered so that C gets charged

through source V_S , C, TA and the load.
The charging current through capacitor C decays and as it reaches zero, $V_C = V_S$ and TA is turned off.

→ With capacitor C charged with polarities, the chopper circuit is ready for operation. This current i_C , i_T , i_{fd} & i_O are taken as positive in the arrow directions marked.
Similarly, the voltages V_C , V_T , V_{TA} & V_O across C, T, TA and load are taken as positive with the polarities marked.

Simplifying assumptions for this chopper are

i) Load current is constant and


ii) Thyristor & diodes are ideal elements.

The chopper operation, for convenience, is divided into certain modes. ϵ_P is explained as.

Mode 1 - The main thyristor is triggered at $t=0$ and RLE load gets connected across source V_S so that load voltage $V_O = V_S$.

During this mode, there are two current paths.

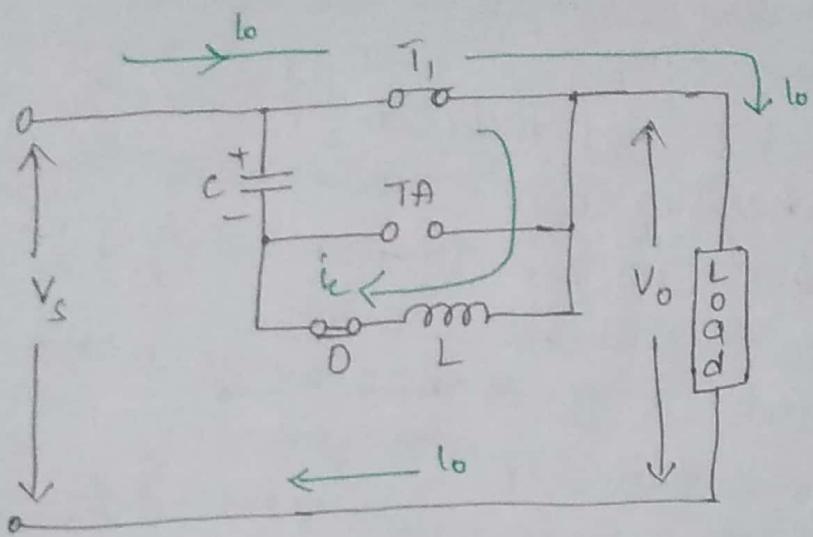
Load current i_O flows through source V_S , main SCR T_1 and load whereas the current i_C flows through oscillatory circuit formed by C, T, L and D.



a) Model, $0 < t < t_1$

- The capacitor current first rises from zero to a maximum value when voltage across is zero at $t = t_1/2$
- After i_c decreases to zero, capacitor is charged to $-(-V_s)$ at $t = t_1$.
- The capacitor current changes sinusoidally whereas the capacitor voltage cosinusoidally from $t=0$ to $t=t_1$. This voltage is held constant at $(-V_s)$ by diode D.
- Voltage across TA is $(-V_s)$ at $t=0$, zero at $t_1/2$ and V_s at t_1 .
- Voltage across T₁ current i_t has a peak at $t_1/2$, because $i_{T_1} = i_c + i_o$ between $t=0$ and $t=t_1$, $i_c = 0$, $i_{T_1} = i_o$, $V_c = -V_s$, At the end of model at t_1 ; $i_c = 0$, $i_{T_1} = i_o$, $V_{TA} = V_s$, $V_o = V_s$, $i_D = 0$

Mode II

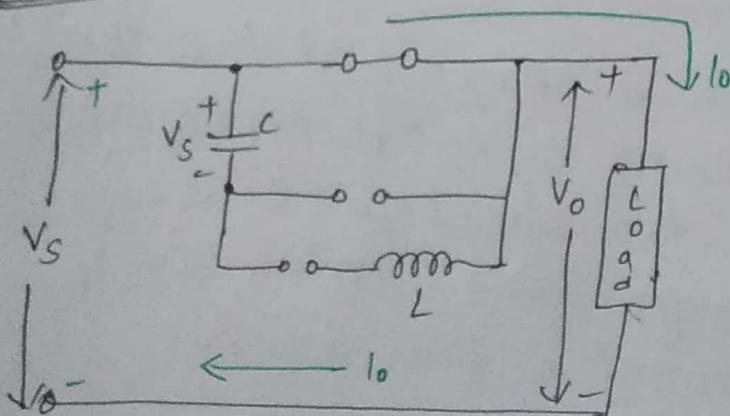


b) Mode II, $t_1 \leq t < t_2$

→ The condition existing at t_1 continue during mode II
→ In other words, for $t_1 \leq t < t_2$,

$$i_c = 0, i_{T_1} = i_o, V_c = -V_s \\ V_{TA} = V_s, V_o = V_s, i_D = 0$$

Note:- only main SCR T_1 is conducted

Mode III :-

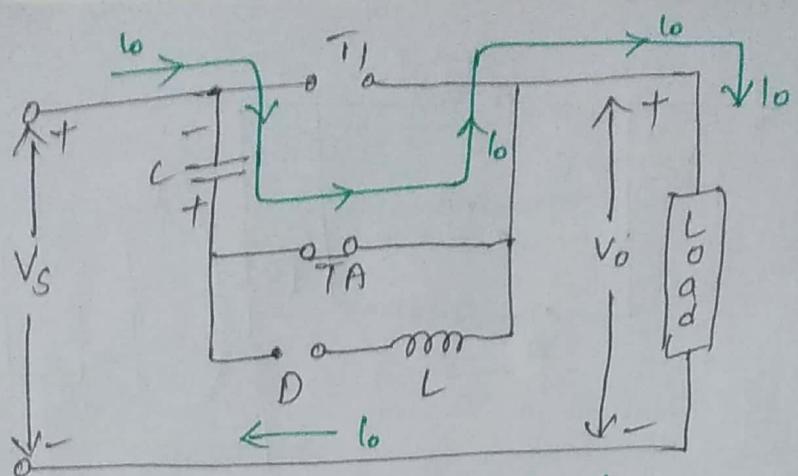

c) Mode III: $t_2 \leq t \leq t_3$

- when main thyristor T_1 is to be turned off, auxiliary thyristor TA is triggered at desired instant t_2 .
- with the turning on of TA at t_2 , capacitor voltage ($-V_C$) appears across T_1 , it is therefore reverse biased & turned off.
- As the capacitor voltage does the required job of commutating the main thyristor T_1 , it is called voltage commutated chopper. Current I_{T_1} becomes zero at t_2 .
- After T_1 is turned off, capacitor C and auxiliary SCR TA provide the path for load current I_0 through V_S, C, TA and the load.


The load voltage is sum of the source voltage and the voltage across capacitor C.

- Voltage across capacitor C.
- ∴ at instant t_2 , load voltage at $V_O = V_S + V_C = 2V_S$, and it decreases linearly as the voltage across capacitor decreases.
- During this mode $V_C = V_{T_1}$, because capacitor is directly connected across T_1 through TA.

- Load voltage V_O changes from $2V_S$ at t_2 to V_S at $(t_2 + t_c)$. After $(t_2 + t_c)$, V_C & V_{T_1} starts rising from zero towards V_S whereas V_O starts falling towards zero.

Note:- $i_C = -I_0$ & $I_{TA} = I_0$

Mode IV :-

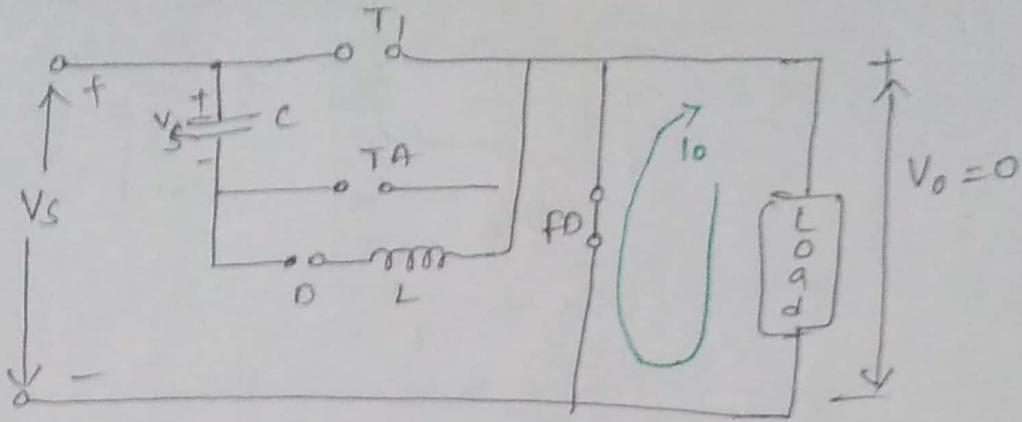


d) Mode IV, $t_3 \leq t < T$

- for this mode, $t_3 < t < T$. At t_3 , $V_c = V_{T_1} = V_s$ & $V_o = 0$
- At t_3 capacitor is slightly overcharged, freewheeling diode FD , therefore gets forward biased at t_3 ,
- In the load circuit formed by FD , TA , C & V_s $V_c > V_s$ at t_3
 \therefore current i_c tends to go negative.
- As i_c or i_{TA} , tends to reverse, auxiliary thyristor TA is turned off naturally at t_3 .
- Thus at time t_3 , FD gets turned on & TA is turned off.
- As a result, load current after t_3 free wheels through the load & FD , through t_3 , free wheels from t_3 to T .
- Note that during freewheeling period from t_3 to T , V_{TA} is slightly negative as C is somewhat overcharged
- During this mode, $i_c = 0$, $i_{T_1} = 0$, $i_{FD} = i_L$, $i_{TA} = 0$

$$V_{T_1} = V_s, V_c = V_s + \Delta V_s, V_{TA} = -\Delta V$$

$$V_o = 0.$$

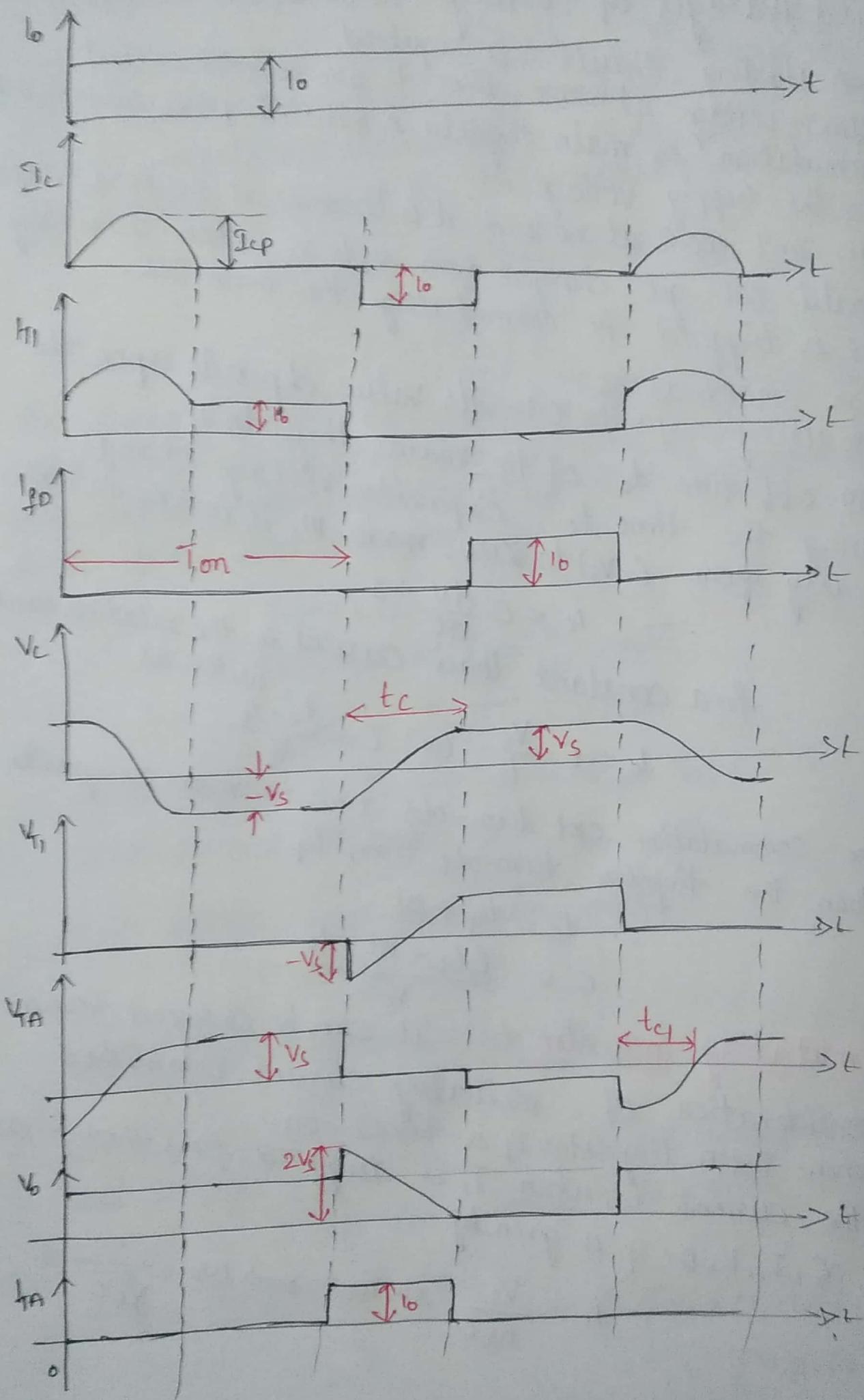At $t=T$, the main thyristor T_1 is triggered & the cycle repeats from $t=0$ to $t=T$ repeats



Disadvantages of voltage commutated chopper

- i) A starting circuit is required
- ii) Load voltage at once rises to $2V_s$ at the instant commutation of main thyristor is initiated. PD is subjected to twice the supply voltage
- iii) It can't work at no load. it is because at no load, capacitor would not get charged from $-V_s$ to V_s . when auxiliary SCR is triggered for commutating the main SCR.

Design considerations :-

commutating capacitor C :- its value depends upon the

tum-off time t_c of the main thyristor T_1 .

During the time t_c , capacitor voltage changes linearly from $(-V_s)$ to zero, mode-III, it is known that

$$i_C = C \cdot \frac{dV}{dt}$$

for a constant load current I_o , the relation can be written as

$$I_o = C \cdot \frac{V_s}{t_c} \quad (\text{or}) \quad C = \frac{t_c \cdot I_o}{V_s}$$

The commutation ckt tum-off time t_c , must be greater than the thyristor tum off time t_q ,

$$\therefore t_c = t_q + \Delta t$$

$$C = \frac{(t_q + \Delta t) \cdot I_o}{V_s}$$

Commutating inductor L :- It can be designed from a

consideration of oscillatory current established when main thyristor T_1 is turned-on.

The current i_C , when T_1 is triggered, flows through the C, T_1, L, D_{sp} is given by

$$i_C = \frac{V_s}{\omega_0 C} \sin \omega_0 t \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\text{The peak capacitor current } I_{cp} = \frac{V_s}{w_0 L} = V_s \cdot \sqrt{\frac{C}{L}}$$

This current flows through T, when it is turned-on.
As T, handles load current as well as I_{cp} , peak capacitor current should not be too large. It is usual to take I_{cp} less than, or equal to, load current I_o . i.e.,

$$I_{cp} \leq I_o \quad \text{or} \quad V_s \sqrt{\frac{C}{L}} \leq I_o$$

$$L \geq \left(\frac{V_s}{I_o}\right)^2 C$$

The second method of designing the value of L is from consideration of the ckt turn-off time for TA. It is seen from time variation of V_{TA} that turn off time for TA is t_{c1} and it is given by

$$t_{c1} = t_1/2$$

$$w_0 t_1 = \pi \quad \text{or} \quad t_1 = \frac{\pi}{w_0} = \pi \sqrt{LC}$$

$$t_{c1} = \frac{\pi}{2} \sqrt{LC}$$

peak voltage across T, & TA is $V_{TAP} = \pm V_s$

peak current through TA is $I_{TAP} = \frac{CV_s}{t_{c1}} = I_o$

peak voltage across freewheeling diode.

$$V_{FDP} = 2V_s$$

peak diode current, $i_{Dp} = V_s \sqrt{\frac{C}{L}}$

voltage commutated chopper:-

i) load voltage V_o from $t=0$ to t_2 and it varies from $\pm V_s$ at t_2 to zero at t_3 . \therefore avg load voltage V_o is given by

$$V_o = \frac{V_s \cdot t_2 + 2V_s(t_3 - t_2)(1/2)}{T} = \frac{V_s}{T} [t_{on} + (t_3 - t_2)]$$

$(\because A_s t_2 = t_{on})$

During the interval $(t_3 - t_2)$, the voltage across C changes from $-V_s$ to V_s i.e., total change is $2V_s$

$$I_o = C \cdot \frac{2V_s}{(t_3 - t_2)} \quad (\text{or}) \quad t_3 - t_2 = \frac{2CV_s}{I_o}$$

$$V_o = \frac{V_s}{T} \left[T_{on} + \frac{2V_s}{I_o} C \right] = \frac{V_s}{T} T_{on}'$$

where $T_{on}' = T_{on} + \frac{2V_s}{I_o} C$ = effective on period

- ii) Charge on capacitor must be reversed from $+V_s$ to $-V_s$ when T_1 is turned on.

Therefore minimum on period for this chopper is

$$t_1 = \frac{\pi}{\omega_0} = \pi \sqrt{LC}$$

minimum duty cycle, $\alpha_{mn} = \frac{t_1}{T} = \pi f \sqrt{LC}$

$$\begin{aligned} \text{minimum load voltage, } V_{o,mn} &= \alpha_{mn} \cdot V_s + \frac{2V_s \cdot 2t_c}{2T} \\ &= V_s (\alpha_{mn} + 2f t_c) \\ &= V_s [\pi f \sqrt{LC} + 2f t_c] \end{aligned}$$

$$V_{o,mn} = f \cdot V_s [t_1 + 2t_c]$$

Max on period is $(T - 2t_c)$. This gives max value of duty cycles

$$\alpha_{mx} = \frac{T - 2t_c}{T} = 1 - 2f t_c$$

Max load or o/p voltage, V_{omx} is given by

$$V_{omx} = \alpha_{mx} \cdot V_s + \frac{2V_s \cdot 2t_c}{2T} = V_s [\alpha_{mx} + 2f t_c]$$

sub. the value of α_{mx} , gives

$$V_{omx} = V_s [1 - 2f t_c + 2f t_c] = V_s$$

→ If main thyristor T_1 fails to turn off when TA is triggered, C is completely discharged. The commutation ∴ cannot be resumed in the next cycle ∵ control lost must be regained by turning off T_1 by interrupting the supply

→ The circuit cannot be operated at no load.

Current-commutated chopper:-


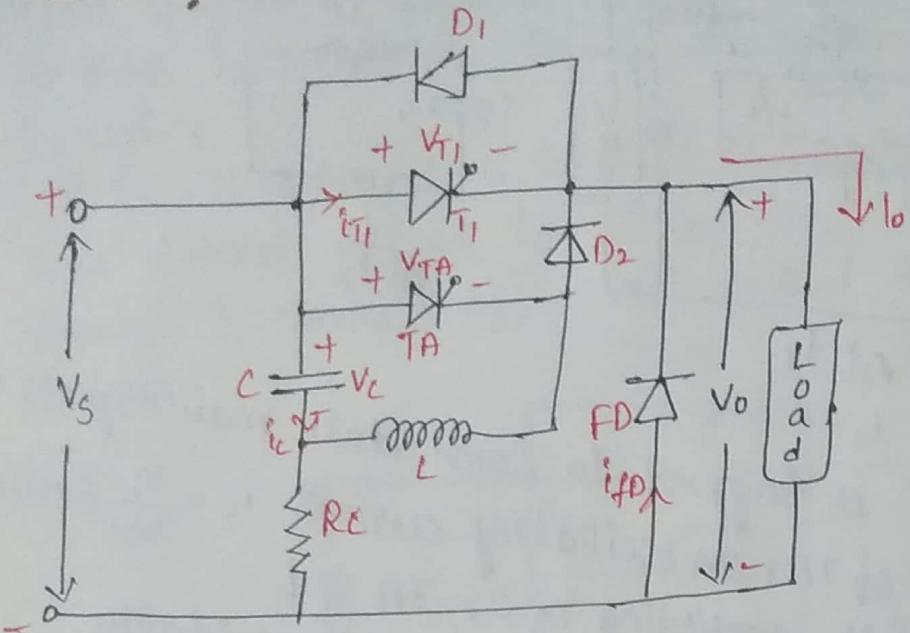


fig: current commutated chopper

→ The circuit diagram consists of T_1 is the main thyristor. The other components, namely, auxiliary thyristor TA, capacitor, inductor L, diodes D_1 & D_2 constitute commutation circuitry.
 → FD is freewheeling diode and R_C is charging resistor.

- Simplifying assumptions for the chopper are as follows:
 - i) load current is constant
 - ii) SCRs & diodes are ideal switches
 - iii) charging Resistor R_C is so large that it can be treated as open circuit during the commutation interval.
- currents i_C , i_{T_1} , i_{FD} and i_o are treated as positive when these are in the arrow directions marked.
- voltages V_C , V_{T_1} , V_{TA} and V_o are taken as positive with the polarities as marked.
- energy stored in capacitor C is charged to a voltage V_s . So that energy for commutation process is available.
- C is charged through source V_s , capacitor C & the charging resistor R_C to a voltage V_s .
- After main thyristor T_1 is fired at $t=0$ so that load voltage $V_o = V_s$ & load current $i_o = i_o$ upto $t=t_1$, commutation circuitry remains inactive. Initiation of commutation process begins with the turning on of thyristor TA.


Mode I:-

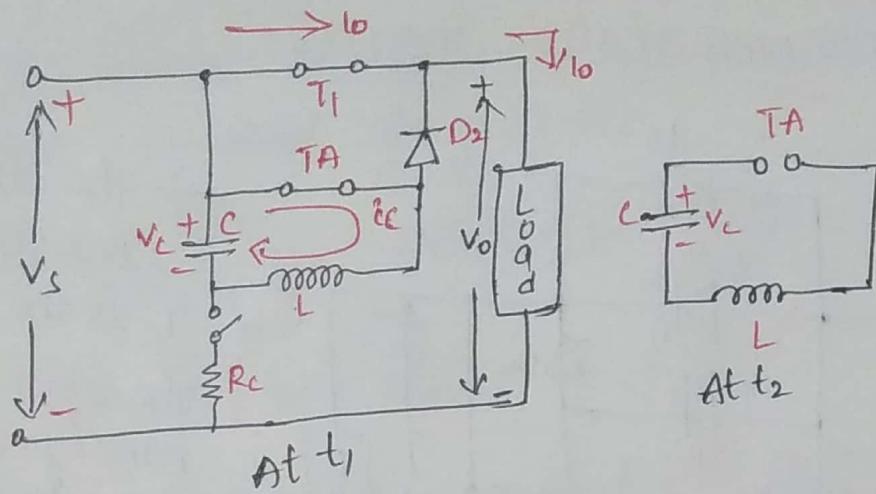

(a) Mode I, $t_1 < t < t_2$

- At time $t=t_1$, TA is triggered to commutate main thyristor T_1 . With the turning-on of TA, an oscillatory current $i_c = \frac{V_s}{w_0 L} \sin \omega_0 t$ is set up in the circuit consisting of C, TA & L. During this interval $(t_2 - t_1)$, i_c & V_c vary sinusoidally through half cycle.
- During this mode when V_c is zero, i_c is max though negative.
- At t_2 , as i_c tends to reverse in the auxiliary Thyristor TA, it gets naturally commutated.
- At t_2 , $V_c = -V_s$, lower plate is +ve & upper plate is $-V_s$. During this mode T_1 remains unaffected, therefore load current & load voltage remains to be V_s respectively.

Mode II :-

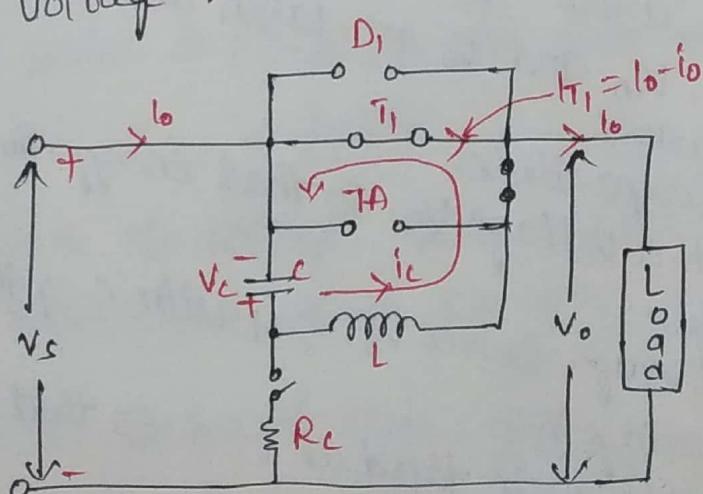


b) Mode II, $t_2 < t < t_3$

- As TA is turned off at t_2 , oscillatory current i_c begins to flow through C, L, D₂ & T₁.
- After t_2 , i_c would flow through T₁ and not through D₁. It is because D₁ is reverse biased by a small voltage drop across conducting thyristor T₁.

- So, after t_2 , i_c would pass through T_1 & not through D_1 .
- In Thyristor T_1 , i_c is in opposition to load current i_o . So that $i_{T_1} = i_o - i_c$. So, i_{T_1} is in the forward direction through T_1 .
 - At t_3 , i_c rises to i_o so that $i_{T_1} = 0$; as a result main SCR T_1 is turned off at t_3 . Since the oscillatory current through T_1 turns it off, it is called current commutated chopper.


Mode: III:

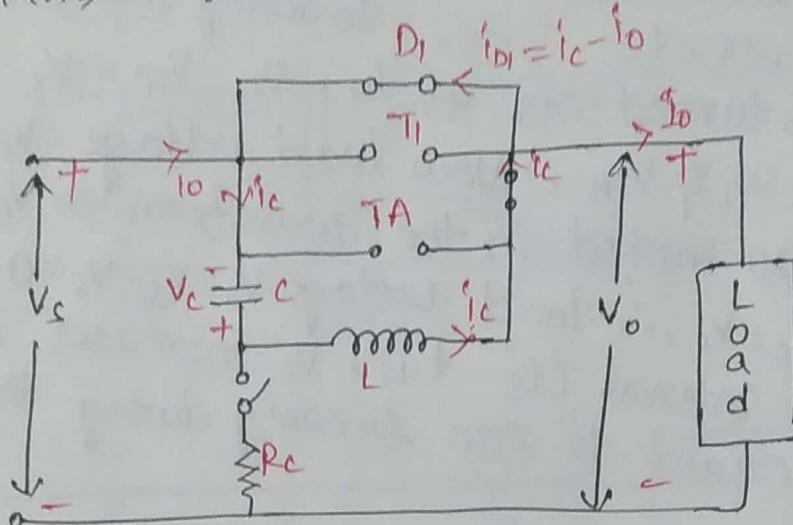

(c) Mode III, $t_3 < t < t_4$

- As T_1 is turned off, i_c becomes more than i_o . After t_3 , i_c supplies load current to & the excess current $i_{D_1} = i_c - i_o$ is conducted through diode D_1 .
- The voltage drop in D_1 due to $(i_c - i_o)$ keeps T_1 reverse biased for $(t_4 - t_3) = t_c$.
- As t_4 in case V_c exceeds V_s , FD comes into conduction, otherwise mode IV would follow.
- During mode III, when i_c is at its peak value of $I_{CP} = \frac{V_c}{\omega L}$, $V_c = 0$. After this peak, capacitor voltage reverses. & at t_4 , upper plate is +ve & lower plate is -ve.

Mode IV :-

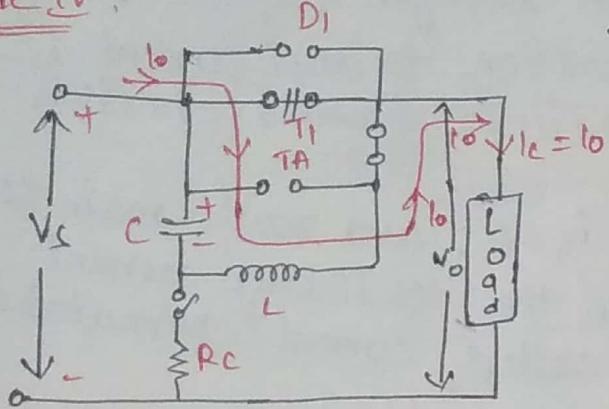


- At t_4 , i_c reduces to i_o , as a result $i_{D1} = 0$ & diode D_1 is therefore turned off.
- After t_4 , a constant current equal to i_o flows through source V_s , C , L , D_2 & load L .
 $\therefore C$ is charged linearly to V_s at t_5 so during time $(t_5 - t_4)$, $i_c = i_o$.

d) Mode IV, $t_4 < t < t_5$

- As D_1 is turned off at t_4 , $V_{T1} = V_{TA} = V_c$; this is in ab for V_c , V_t , & V_{TA} . Now load voltage $V_o = V_s - V_c = V_s - V_{ab}$ This is also marked in the waveform for V_o at t_4 .
- At t_5 , $V_c = V_s$, \therefore load voltage $V_o = V_s - V_s = 0$ at t_5
- During the interval $(t_5 - t_4)$, V_c increases linearly.
 $\therefore V_o$ decreases to zero linearly during this interval


Mode V :-

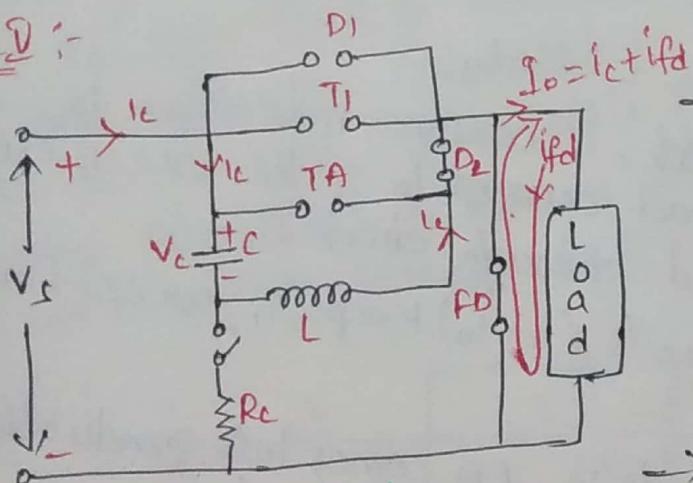

- At t_5 , capacitor C is actually overcharged to a voltage somewhat more than V_s .
 $\therefore FD$ gets forward biased & starts to conduct load current i_o at t_5 .
- V_o is reduced to zero at t_5

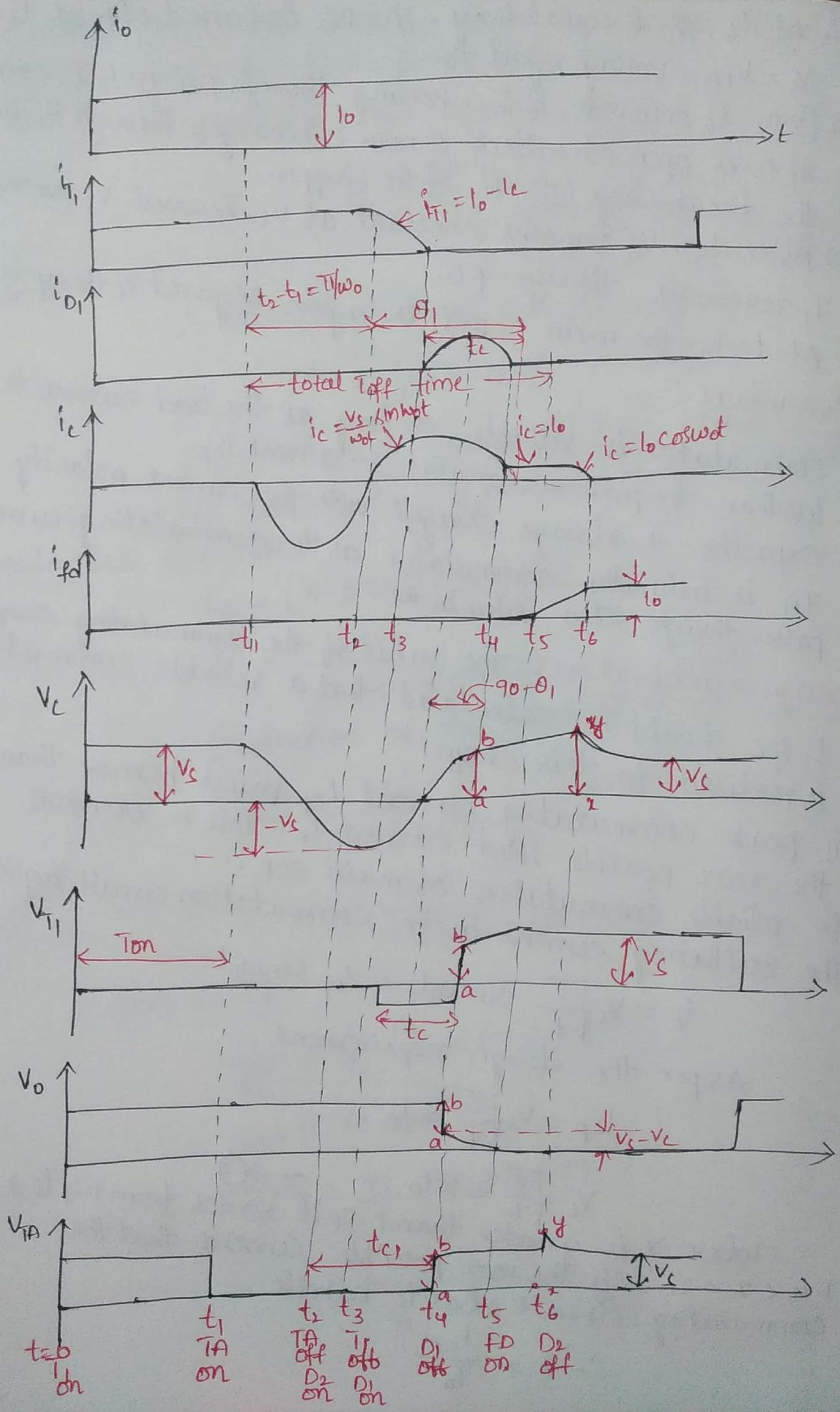e) Mode V, $t_5 < t < t_6$

- As i_c is not zero at t_5 , the capacitor C is still connected to load through source V_s , C , L , & D_2 ; as a consequence C is overcharged by the transfer of energy from L to C .
- At t_6 , $i_c = 0$ & V_c becomes more than V_s
- During $(t_6 - t_5)$, $i_c + i_{FD} = 0$, with the build up of i_{FD} , i_c decays & finally at t_6 , $i_c = 0$ & $i_{FD} = i_o$
- Commutation process is completed at t_6 . Total turn-off time, or commutation interval is $(t_6 - t_5)$



- At t_6 , V_C is equal to v_s . As D_2 is turned off at t_6 .
- $V_C = V_{TA} = \text{voltage across } C \text{ at } t_6$
- From t_6 onwards, C is freewheeling through FD. As i_C is zero & D_2 is open circuited, C now discharges through R_C for the freewheeling interval of the chopper.
- After t_5 , V_T remains constant at v_s , because v_s reaches T , terminals through FD.
- At $t=T$, the main SCR T_1 is again triggered & the cycle repeats

Advantages :-

- 1) Commutation is reliable so long as the load current is less than the peak commutating current I_{CP} .
- 2) Capacitor is always charged with the current polarity.
- 3) TA is naturally commutated as its commutating current passes through zero value.

Design considerations :- The value of the commutating component L_{SPC} should be calculated that a reliable commutation is realised for this chopper.

i) Peak commutating current I_{CP} must be more than the max possible load current I_0 . This is essential for reliable commutation of main SCR.

The oscillating current in the commutation circuit is given by

$$i_c = v_s \sqrt{\frac{C}{L}} \sin \omega t = I_{CP} \sin \omega t.$$

As per the design requirement

$$I_{CP} = v_s \sqrt{\frac{C}{L}} > I_0$$

$$v_s \sqrt{\frac{C}{L}} = x I_0 \rightarrow 0$$

where x is greater than & it varies from 1.4 to 3.
 $1.4 < x < 3$, I_0 is the max possible current that the commutating circuit has to handle

$$\therefore x = \frac{I_{CP}}{I_0}$$

ii) circuit turn-off time t_c must be greater than thyristor turn-off time for the main SCR.
 That is $t_c = t_2 + \Delta t \Rightarrow t_c = t_4 - t_3$

$$\omega_0 t_c = \pi - 2\theta_1$$

$$I_{CP} \sin \theta_1 = I_0$$

$$\theta_1 = \sin^{-1}\left(\frac{I_0}{I_{CP}}\right) = \sin^{-1}\left(\frac{1}{x}\right)$$

\therefore circuit turn-off time for main SCR,

$$t_c = \frac{1}{\omega_0} (\pi - 2\theta_1) \rightarrow ②$$

$$t_c = \frac{1}{\omega_0} \left[\pi - 2 \sin^{-1}\left(\frac{1}{x}\right) \right] \rightarrow ③$$

it reveals load current I_0 increases, turn-off time of main SCR decreases.

$$t_c = [\pi - 2 \sin^{-1}(1/x)] \sqrt{LC} \rightarrow ④$$

$$\sqrt{C} = \frac{t_c}{[\pi - 2 \sin^{-1}(1/x)] \sqrt{L}}$$

in equ ①

substitution of this value of \sqrt{C} , gives

$$\frac{V_s}{L} \cdot \frac{t_c}{[\pi - 2 \sin^{-1}(1/x)]} = x \cdot I_0$$

$$L = \frac{V_s \cdot t_c}{x I_0 [\pi - 2 \sin^{-1}(1/x)]} \rightarrow ⑤$$

from equ ④,

$$\frac{1}{\sqrt{L}} = \frac{1}{t_c} [\pi - 2 \sin^{-1}(1/x)] \sqrt{C}$$

sub \sqrt{L} in equ ①

$$x \cdot I_0 = \frac{V_s}{t_c} [\pi - 2 \sin^{-1}(1/x)] C$$

$$C = \frac{x \cdot I_0 \cdot t_c}{V_s [\pi - 2 \sin^{-1}(1/x)]}$$

Total commutation interval :-

The total turn-off time, or the commutation interval is $(t_6 - t_1)$

$$t_6 - t_1 = (t_2 - t_1) + (t_4 - t_2) + (t_5 - t_4) + (t_6 - t_5)$$

$t_2 - t_1$: waveform of current i_c , oscillating frequency ω_0 , completes one negative half cycle of π radians
 $(t_2 - t_1)$ = time period of half cycle of oscillating current

$$= \frac{\pi}{\omega_0} = \pi \sqrt{LC}$$

$t_4 - t_2$: At t_2 , $i_c = 0$, & at t_4 , i_c attains a value i_0 after passing through its peak. Angle by i_c from t_2 to t_4 is $\pi - \theta_1$ radians and as ω_0 is the angular frequency for i_c

$$t_4 - t_2 = \frac{\pi - \theta_1}{\omega_0} = (\pi - \theta_1) \sqrt{LC}$$

$t_5 - t_4$: The time $(t_5 - t_4)$ can be obtained from voltage across C at t_4 and at t_5 = across C at $t_4 = ab = v_c$ at t_4 . As this voltage at the instant t_4 is $(90 - \theta_1)$ ° away from zero crossing of v_c sine wave, $ab = v_s \sin(90 - \theta_1)$

voltage across C at $t_5 = v_s$

increase in voltage across C during $(t_5 - t_4)$ =

$$v_s - v_s \sin(90 - \theta_1)$$

we know that $i = C \cdot \frac{dv}{dt}$. As i_0 is constant

$$i_0 = C \cdot \frac{v_s - v_s \sin(90 - \theta_1)}{(t_5 - t_4)}$$

$$(t_5 - t_4) = C \cdot v_s \cdot \frac{1 - \sin(90 - \theta_1)}{i_0}$$

$$= C \cdot v_s \cdot \frac{1 - \cos \theta_1}{i_0}$$

$(t_6 - t_5) \approx$ During $(t_6 - t_5)$, current i_c is assumed to be $I_0 \cos \omega_0 t$. As $(t_6 - t_5)$ is equal to the quarter cycle ($\pi/2$ rad). of a sine wave

$$t_6 - t_5 = \frac{1}{2} \frac{\pi}{\omega_0} = \frac{\pi}{2} \sqrt{LC}$$

$\therefore t_6 - t_1 =$ total commutation period

$$= \left(\frac{5\pi}{2} - \theta_1 \right) \sqrt{LC} + C \cdot V_s \cdot \frac{1 - \cos \theta_1}{I_0}$$

$$= \left(\frac{5\pi}{2} - \theta_1 \right) \sqrt{LC} + 2C V_s \cdot \frac{\sin^2 \theta_1 / 2}{I_0}$$

Turn-off times: for main SCR, turn-off time is

$$t_4 - t_3 = t_c = (\pi - 2\theta_1) \sqrt{LC}$$

$$t_c = [\pi - 2 \sin^{-1}(\gamma/2)] \sqrt{LC}$$

turn-off time for TA, is

~~$t_4 - t_4 - t_2 = t_{c1} = (\pi - \theta_1) \sqrt{LC}$~~

$$= [\pi - 2 \sin^{-1}(\gamma_x)] \sqrt{LC}$$

Peak capacitor voltage:-

waveform of V_C reveals the max. capacitor voltage v_{cp} is reached at t_5

\therefore Voltage at $t_6 = v_{cp} =$ voltage at $t_5 +$ voltage rise due to $L \frac{dv}{dt}$


At t_5 , energy in L is $\frac{1}{2} L I_0^2$ & at t_5 , the entire energy is transferred to C . The voltage rise of C due to this energy is

$$\frac{1}{2} C V_C^2 = \frac{1}{2} L I_0^2$$

$$V_C = I_0 \sqrt{\frac{L}{C}}$$

$$V_{cp} = V_s + I_0 \sqrt{\frac{L}{C}} = V_{xy}$$


Load-commutated chopper:-

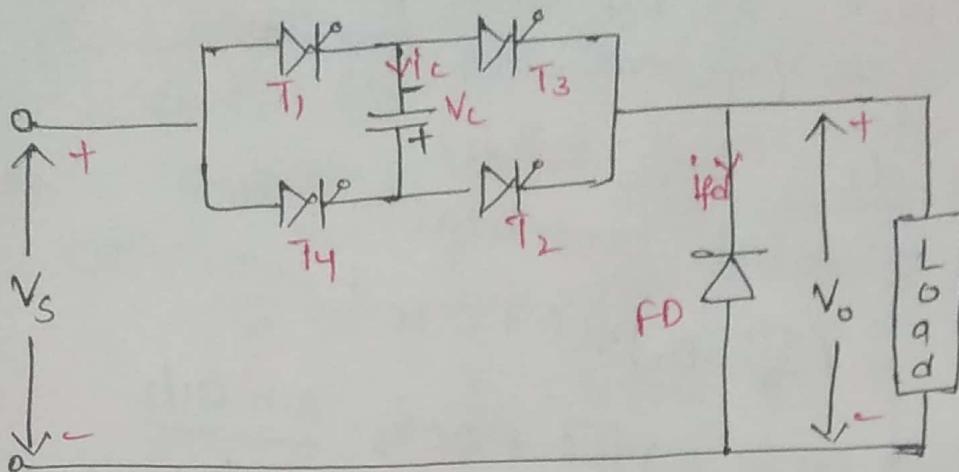

- It consists of four thyristors $T_1 - T_4$ and one commutating capacitor C . The thyristor T_1, T_2 act together as one pair & thyristors T_3, T_4 act together as the second pair for conducting the load current alternately.
- When T_1, T_2 are conducting, these act as main thyristors and T_3, T_4 and C as the commutating components.
- With the conduction of T_3, T_4 ; these become main thyristors and T_1, T_2 and C as the commutating components.
- FD is the freewheeling diode across the load.
- Initially, the capacitor is charged to a voltage V_s with upper plate negative & lower plate positive.
- Assumptions made in current-commutated chopper also apply here. The working of this chopper can be explained in various modes as under.

Mode 1:-

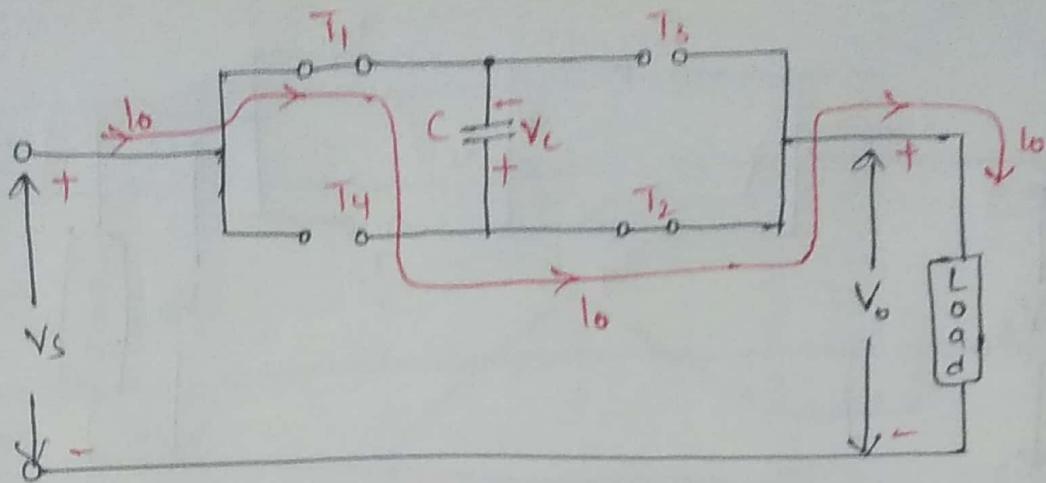
- With the capacitor 'C' charged with lower plate +ve, the load commutated chopper is ready for operation.
- When the thyristor pair T_1, T_2 is triggered at $t=0$, circuit consisting of V_s, T_1, C, T_2 & load shows that load voltage at once shoots to $V_o = V_s + V_C = 2V_s$.



a) Mode I, $0 < t < t_1$

- The capacitor C is charged linearly by constant load current I_o from V_s at $t=0$ to $(-V_s)$ at t_1 .
- When the capacitor voltage becomes $(-V_s)$, the load voltage falls from $2V_s$ to $V_o = V_s - V_s = 0$ at t_1 .
- At $t=0$, when T_1, T_2 are turned on, T_3, T_4 are reverse biased by capacitor voltage, i.e., at $t=0$, $V_{T3} = V_{T4} = -V_s$. At t_1 , $V_{T3} = V_{T4} = V_s$. i.e., T_3, T_4 are forward biased at t_1 .


Mode II:-

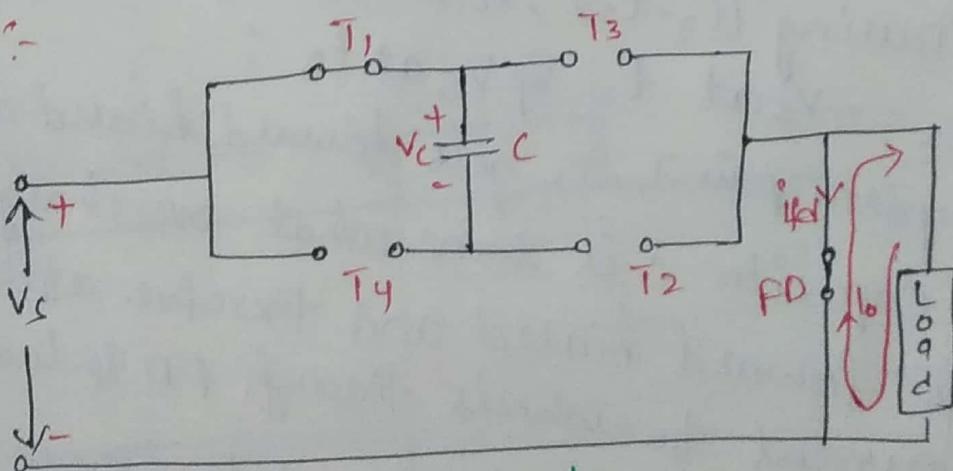

b) Mode II, $t_1 < t < t_2$


- At t_1 , capacitor C is slightly overcharged, as a result freewheeling diode gets forward biased and load current is transferred from T_1, T_2 to FD.
- From t_1 onwards, load current freewheels through FD.
- During $(t_2 - t_1)$, $V_c = -V_s$, $V_o = 0$, $i_c = 0$, if $i_d = I_o$, if $T_1 = T_2 = 0$, $V_{T3} = V_{T4} = V_s$ & $V_{T1} = V_{T2} = -DV_s$ as capacitor is overcharged by a small voltage DV_s .

Model III:

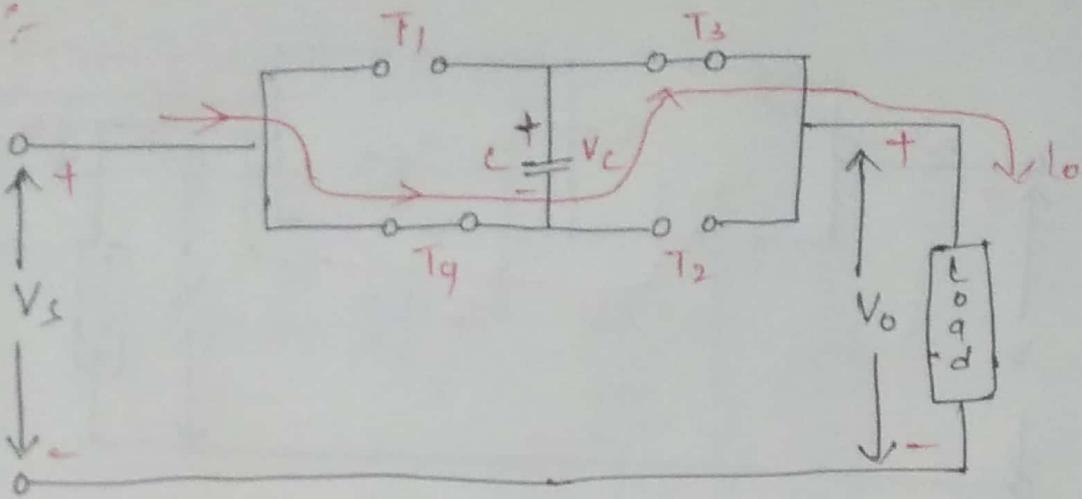

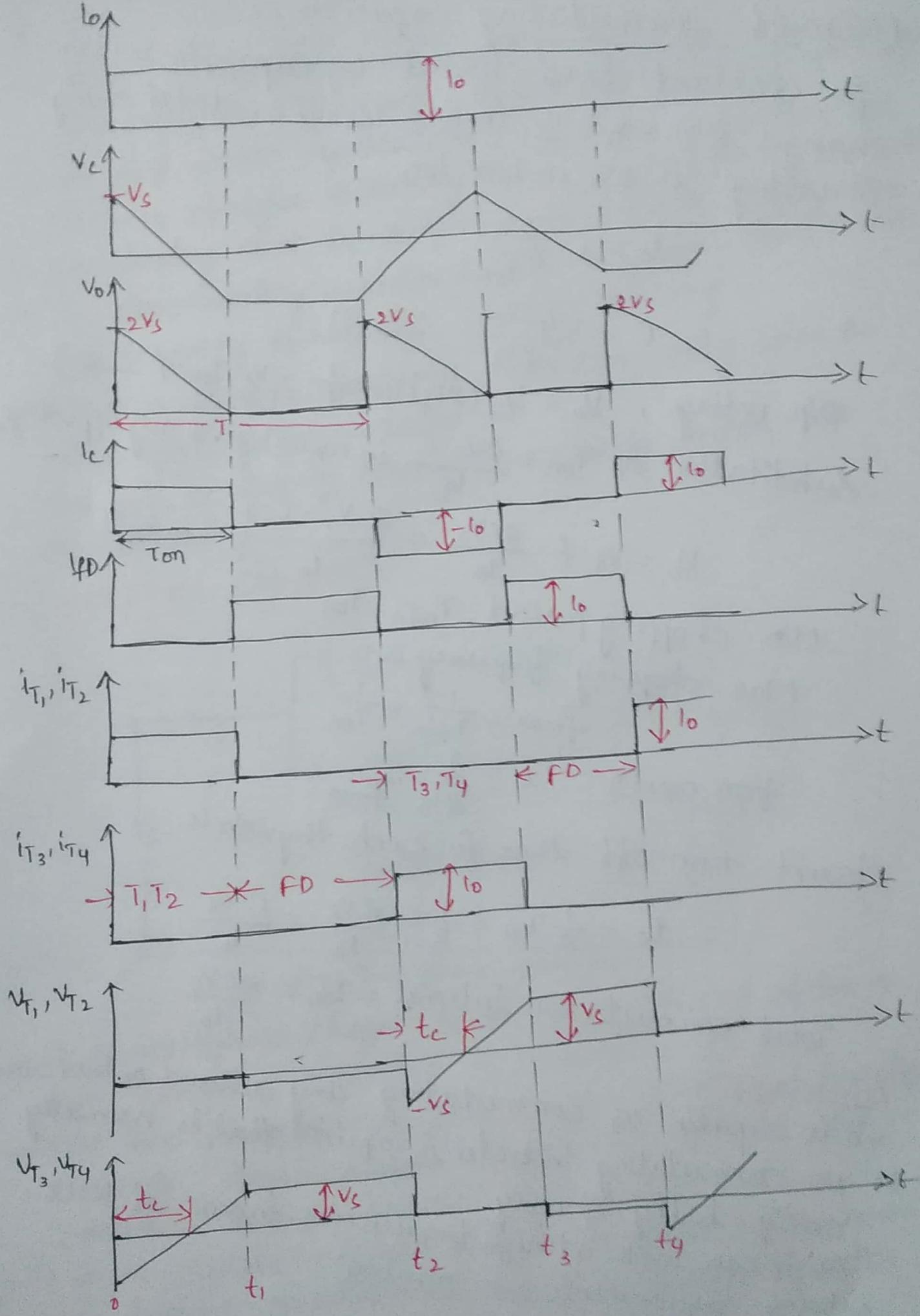c) Model III, $t_2 < t < t_3$

- At t_2 , thyristor pair T_3, T_4 is triggered, load voltage at once becomes, $V_0 = V_s + V_c = 2V_s$.
- Thyristor pair T_1, T_2 is reverse biased by V_c , this pair is therefore turned off at t_2 .
- The load current, now flowing through V_s, T_4, C, T_3 and load charges capacitor linearly from $(-V_s)$ at t_2 to V_s at t_3 .
- Load voltage accordingly falls from $2V_s$ at t_2 to $2V_s$ at t_3 . During $(t_3 - t_2)$; $i_C = -i_o$, $i_{T_3} = i_{T_4} = i_o$ but $U_{T_1} = U_{T_2} = -V_s$ at t_2 & V_s at t_3 .
i.e., thyristor pair T_1, T_2 gets forward biased at t_3 .
- At t_3 , capacitor C is somewhat overcharged, FD gets forward biased and therefore after t_3 , load current freewheels through FD & load. When T_1, T_2 are turned on at t_4 , model repeats.



Design of commutating capacitance:-

for constant load current I_o , capacitor voltage changes from $-V_s$ to V_s in time T_{on} , i.e., total change in voltage is $2V_s$ in Time T_{on} .

$$I_o = C \cdot \frac{2V_s}{T_{on}}$$

$$C = \frac{I_o \cdot T_{on}}{2V_s} \rightarrow ①$$

$$\text{O/p voltage, } V_o = \frac{1}{2} (2V_s) T_{on} \cdot \frac{1}{T} = V_s \cdot T_{on} \cdot f \rightarrow ②$$

Substitution of $T_{on} = \frac{2V_s \cdot C}{I_o}$ in equ ② gives output voltage

$$V_o = V_s \cdot f \cdot \frac{2CV_s}{I_o} = \frac{2 \cdot V_s^2 \cdot C \cdot f}{I_o} \rightarrow ③$$

Min. chopping period, $T_{min} = T_{on}$

Max. chopping frequency,

$$f_{max} = \frac{1}{T_{min}} = \frac{1}{T_{on}}$$

$$\text{from equ ①, } C = \frac{I_o}{2V_s} \cdot \frac{1}{f_{max}}$$

Circuit turn-off time for each thyristor's

$$t_c = \frac{1}{2} T_{on} = \frac{1}{2} C \cdot \frac{2V_s}{I_o} = \frac{C \cdot V_s}{I_o}$$

$$\text{Total commutation interval} = T_{on} = \frac{2CV_s}{I_o}$$

Advantages:-

- 1) It is capable of commutating any amount of load current.
- 2) No commutating inductor is required that is normally costly, bulky & noisy.
- 3) As it can work at high frequencies in order of $k\text{Hz}$, filtering requirements are minimal.

Disadvantages:

- 1) peak load voltage is equal to twice the supply voltage.
This peak can however be reduced by filtering
- 2) for high-power applications, efficiency may become low because of higher switching losses at high operating frequencies.
- 3) freewheeling diode is subjected to twice the supply voltage load current
- 4) The commutating capacitor has to carry full load current at a frequency of half the chopping frequency
- 5) one pair of SCRs should be turned on only when the other pair is commutated.
This can be done by sensing the capacitor current that is alternating.

Multiphase choppers:


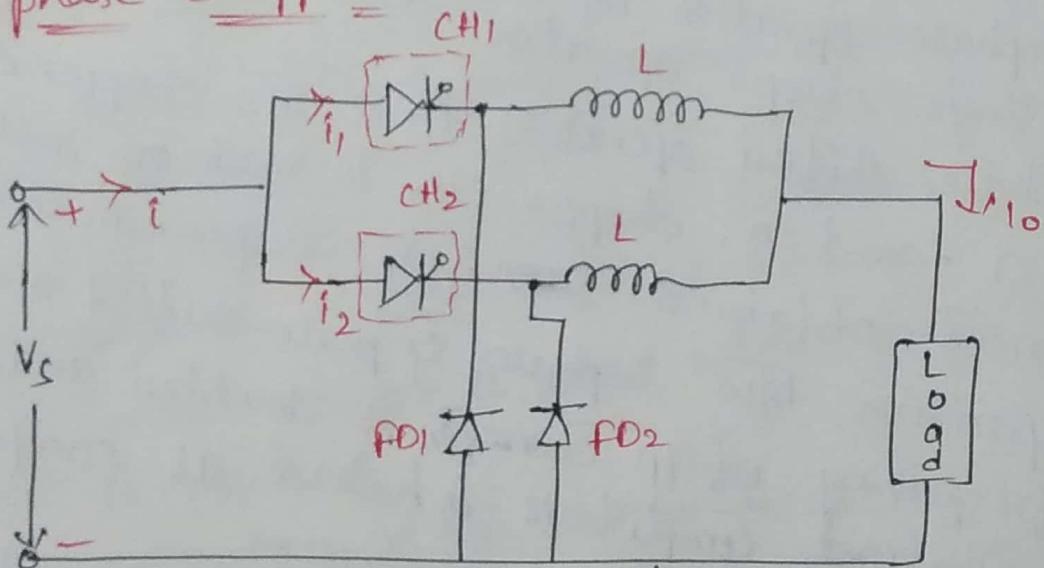



fig: Two phase chopper.

- A multiphase chopper is one that consists of two or more choppers connected in parallel
- The two choppers configuration is called a two-phase chopper
Similarly, three choppers connected in parallel will constitute a 3-φ chopper
- A multiphase chopper maybe operated in two modes i.e., inphase operation mode & phase shifted operation mode.

- In the in-phase operation mode, all the parallel connected choppers are on & off at the same instant.
- In phase shifted mode operation, different choppers are on & off at different instants of time
- In fig. consists of inductance L in series with each chopper is assumed to be sufficiently large so that each chopper operates independent of each other.
- Let the load current be to be ripple free.
- For a duty cycle of $\alpha = 30\%$, inphase operation of this chopper when both the choppers are on & off at the same instant.
- The i/p current i , obtained by the addition of i_1 , i_2 .
- The i/p current i , obtained by the addition of i_1 , i_2 is seen to be doubled.
- The inphase operation of multiphase chopper is equivalent to a single chopper operation.
- The phase shifted operation for $\alpha = 30$, chopper CT₁ is on for $0.3T$ from $t=0$. Chopper CT₂ is made on, such that i/p current obtained from $i_1 + i_2$ is periodic in nature.
- Comparison b/w inphase & phase-shifted operation the frequency of i/p current is doubled and its ripple current amplitude is halved as compared to the inphase operation of chopper.
- In the inphase operation mode frequency of harmonics in the i/p current is equal to switching frequency ($= 1/T$) of each chopper.
- In phase shift operating mode, frequency of harmonics in the i/p current is twice the switching frequency of each chopper.
- As the frequency of harmonics in the i/p current is twice the switching frequency, the size of filter is reduced in the phase shifted chopper.

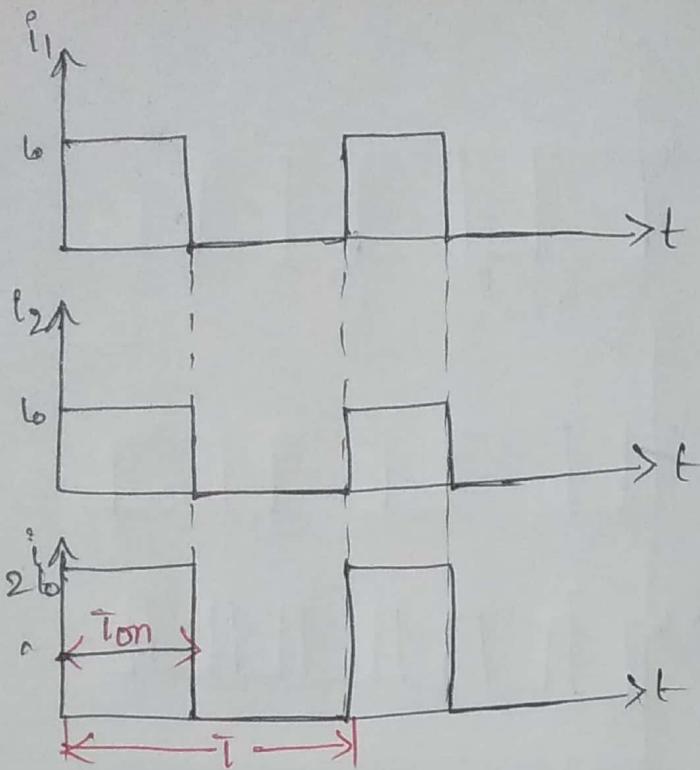


a) in phase operation

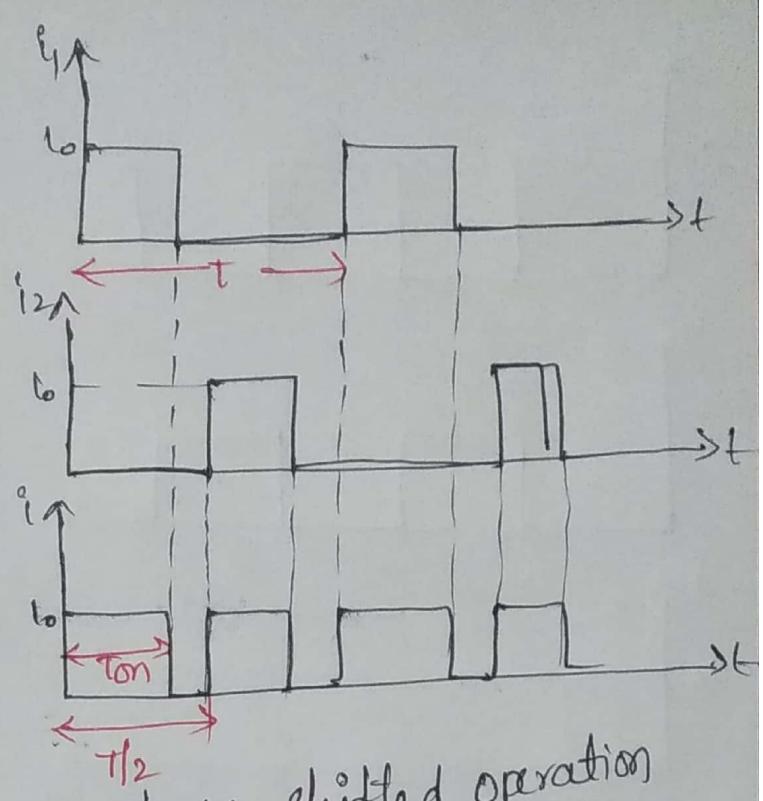


b) phase shifted operation

fig:- ilp waveforms for $\alpha = 0.30$.

- for $\alpha = 50\%$, the ilp supply current of phase-shifted operation is continuous & without any ripples
- for $\alpha = 60\%$, the supply current is continuous but with a pedestal of half the load current
- A multiphase chopper is used where large load current is required.
- The main advantage of this chopper over a single chopper is that its ilp current has reduced ripple amplitude & increased ripple frequency.
As a consequence of it, size of filter for a multiphase chopper is reduced.
- disadvantages of a multiphase chopper are
 - 1) extra commutation circuits
 - 2) additional external inductors &
 - 3) complexity in the control logic.

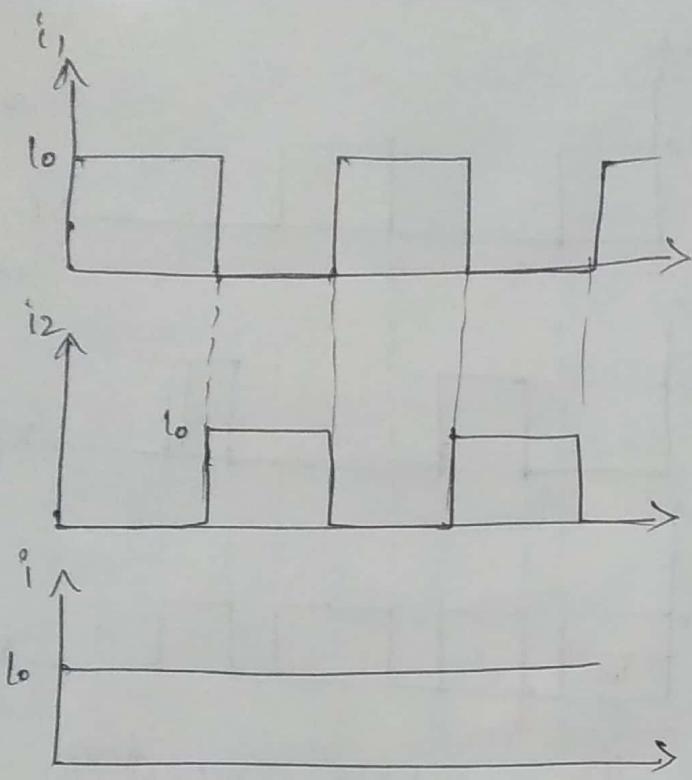

(c)

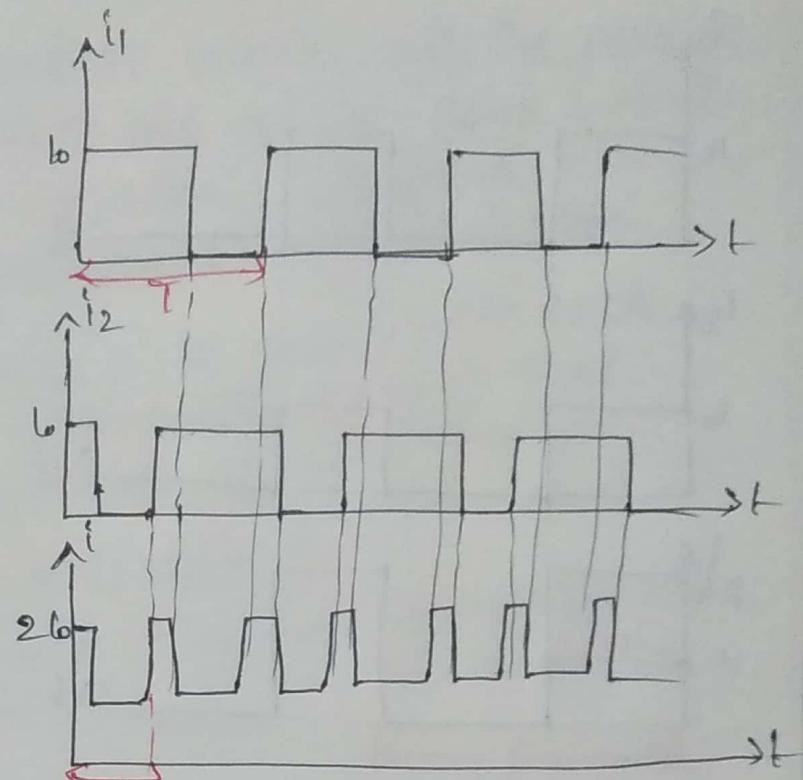

(d)

current waveforms for phase shifted operation

for (c) $\alpha = 0.50$, & (d) $\alpha = 0.60$.